

An electric circuit is said to be a **coupled circuit**, when there exists a mutual inductance between the coils (or inductors) present in that circuit. Coil is nothing but the series combination of resistor and inductor. In the absence of resistor, coil becomes inductor. Sometimes, the terms coil and inductor are interchangeably used.

In this chapter, first let us discuss about the dot convention and then will discuss about classification of coupling.

Dot Convention

Dot convention is a technique, which gives the details about voltage polarity at the dotted terminal. This information is useful, while writing KVL equations.

- If the current enters at the dotted terminal of one coil (or inductor), then it induces a voltage at another coil (or inductor), which is having **positive polarity** at the dotted terminal.
- If the current leaves from the dotted terminal of one coil (or inductor), then it induces a voltage at another coil (or inductor), which is having **negative polarity** at the dotted terminal.

Classification of Coupling

We can classify **coupling** into the following two categories.

- Electrical Coupling
- Magnetic Coupling


Now, let us discuss about each type of coupling one by one.

Electrical Coupling

Electrical coupling occurs, when there exists a **physical connection** between two coils (or inductors). This coupling can be of either aiding type or opposing type. It is based on whether the current enters at the dotted terminal or leaves from the dotted terminal.

Coupling of Aiding type

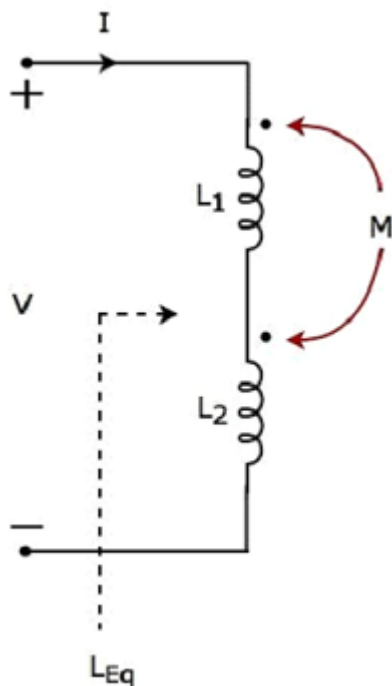Consider the following electric circuit, which is having two inductors that are connected in **series**.



Since the two inductors are connected in series, the **same current I** flow through both inductors having self-inductances L_1 and L_2 .

In this case, the current, I enter at the dotted terminal of each inductor. Hence, the induced voltage in each inductor will be having **positive polarity** at the dotted terminal due to the current flowing in another coil.

Apply **KVL** around the loop of the above electric circuit or network.

$$V - L_1 \frac{dI}{dt} - M \frac{dI}{dt} - L_2 \frac{dI}{dt} - M \frac{dI}{dt} = 0$$

$$V = L_1 \frac{dI}{dt} + L_2 \frac{dI}{dt} + 2M \frac{dI}{dt}$$


$$V = (L_1 + L_2 + 2M) \frac{dI}{dt}$$

The above equation is in the form of $V = L_{Eq} \frac{dI}{dt}$

In this case, the equivalent inductance has been increased by $2M$. Hence, the above electrical circuit is an example of **electrical** coupling which is of **aiding** type.

Coupling of Opposing type

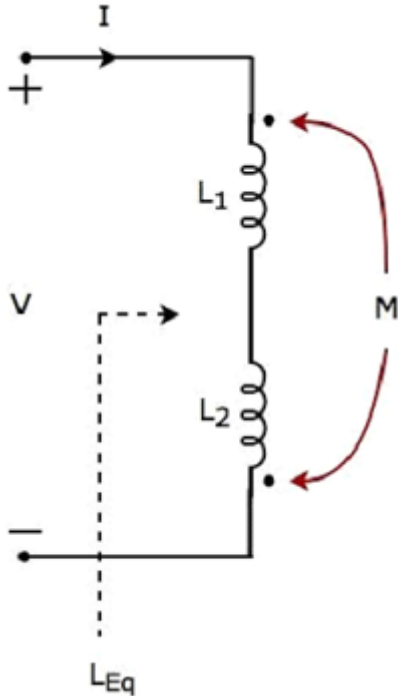Consider the following electric circuit, which is having two inductors that are connected in **series**.



In the above circuit, the current I enters at the dotted terminal of the inductor having an inductance of L_1 . Hence, it induces a voltage in the other inductor having an inductance of L_2 . So, **positive polarity** of the induced voltage is present at the dotted terminal of this inductor.

In the above circuit, the current I leaves from the dotted terminal of the inductor having an inductance of L_2 . Hence, it induces a voltage in the other inductor having an inductance of L_1 . So, **negative polarity** of the induced voltage is present at the dotted terminal of this inductor.

Apply **KVL** around the loop of the above electric circuit or network.

$$V - L_1 \frac{dI}{dt} + M \frac{dI}{dt} - L_2 \frac{dI}{dt} + M \frac{dI}{dt} = 0$$

$$\Rightarrow V = L_1 \frac{dI}{dt} + L_2 \frac{dI}{dt} - 2M \frac{dI}{dt}$$

$$\Rightarrow V = (L_1 + L_2 - 2M) \frac{dI}{dt}$$

The above equation is in the form of $V = L_{Eq} \frac{dI}{dt}$

Therefore, the **equivalent inductance** of series combination of inductors shown in the above figure is

$$L_{Eq} = L_1 + L_2 - 2M$$


In this case, the equivalent inductance has been decreased by $2M$. Hence, the above electrical circuit is an example of **electrical** coupling which is of **opposing** type.

Magnetic Coupling

Magnetic coupling occurs, when there is **no physical connection** between two coils (or inductors). This coupling can be of either aiding type or opposing type. It is based on whether the current enters at the dotted terminal or leaves from the dotted terminal.

Coupling of Aiding type

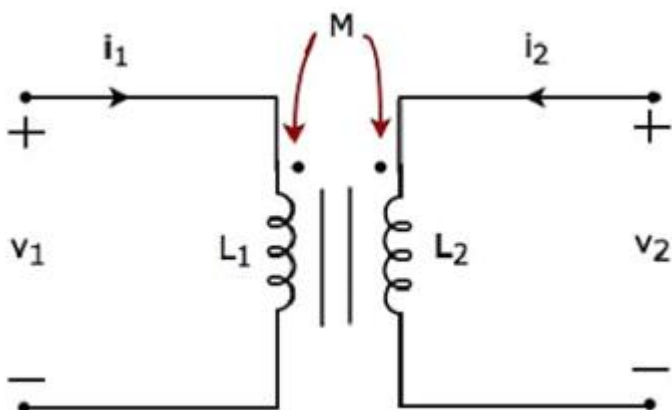Consider the following electrical equivalent **circuit of transformer**. It is having two coils and these are called as primary and secondary coils.



The currents flowing through primary and secondary coils are i_1 and i_2 respectively. In this case, these currents **enter** at the dotted terminal of respective coil. Hence, the induced voltage in each coil will be having positive polarity at the dotted terminal due to the current flowing in another coil.

Apply **KVL** around primary coil.

$$v_1 - L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} = 0$$

$$\Rightarrow v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

Equation 1

Apply **KVL** around secondary coil.

$$v_2 - L_2 \frac{di_2}{dt} - M \frac{di_1}{dt} = 0$$


$$\Rightarrow v_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

Equation 2

In Equation 1 and Equation 2, the self-induced voltage and mutually induced voltage have the same polarity. Hence, the above transformer circuit is an example of **magnetic coupling**, which is of **aiding** type.

Coupling of Opposing Type

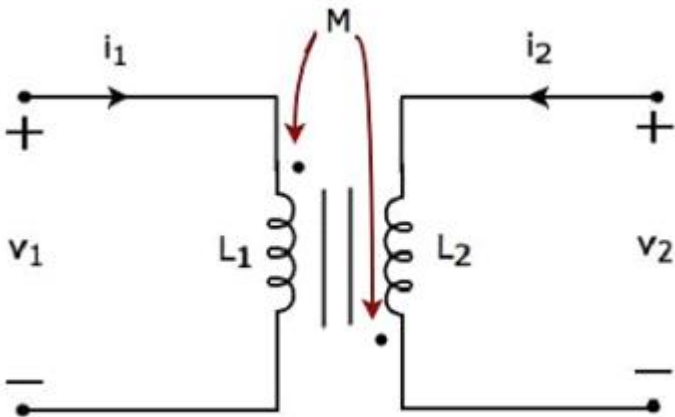Consider the following electrical equivalent **circuit of transformer**.



The currents flowing through primary and secondary coils are i_1 and i_2 respectively. In this case, the current, i_1 enters at the dotted terminal of primary coil. Hence, it induces a voltage in secondary coil. So, **positive polarity** of the induced voltage is present at the dotted terminal of this secondary coil.

In the above circuit, the current, i_2 leaves from the dotted terminal of secondary coil. Hence, it induces a voltage in primary coil. So, **negative polarity** of the induced voltage is present at the dotted terminal of this primary coil.

$$v_1 - L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} = 0$$

$$\Rightarrow v_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

Equation 3

Apply **KVL** around secondary coil.

$$v_2 - L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} = 0$$

$$\Rightarrow v_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

Equation 4

In Equation 3 and Equation 4, self-induced voltage and mutually induced voltage are having opposite polarity. Hence, the above transformer circuit is an example of **magnetic coupling**, which is of **opposing** type.