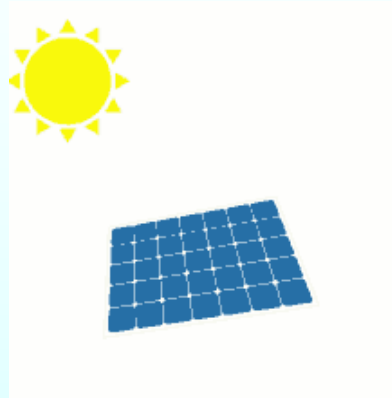


# Two Branch Parallel RLC circuits



**Mr.Ebbie Selva Kumar C**


Assistant Professor/ EEE

*Rohini College of Engineering and Technology*



## Two Branch Parallel Circuit :

Fig. 5.11(a) shows two branch parallel RLC circuit in which one branch contains resistor & inductor and the other branch contains resistor & capacitor.

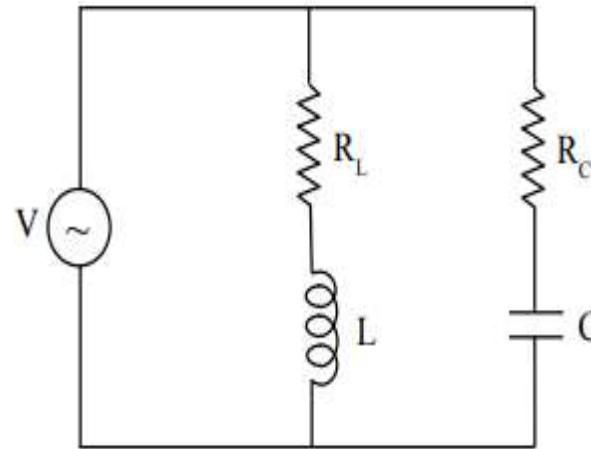

*Fig. 5.11 (a) Two branch parallel circuit*

The total admittance is, 
$$Y = \frac{1}{R_L + jX_L} + \frac{1}{R_C - jX_C}$$



Multiplying the numerator & denominator of each term by conjugate of the denominator we get,

$$\begin{aligned}
 Y &= \frac{R_L - jX_L}{(R_L + jX_L)(R_L - jX_L)} + \frac{R_C + jX_C}{(R_C + jX_C)(R_C - jX_C)} \\
 &= \frac{R_L - jX_L}{R_L^2 + X_L^2} + \frac{R_C + jX_C}{R_C^2 + X_C^2} \quad (\because (a + jb)(a - jb) = a^2 + b^2) \\
 &= \frac{R_L}{R_L^2 + X_L^2} + \frac{R_C}{R_C^2 + X_C^2} + j \left[ \frac{X_C}{R_C^2 + X_C^2} - \frac{X_L}{R_L^2 + X_L^2} \right]
 \end{aligned}$$


At resonance, susceptance  $B = 0$

$$\Rightarrow \frac{X_C}{R_C^2 + X_C^2} - \frac{X_L}{R_L^2 + X_L^2} = 0 \Rightarrow \frac{X_C}{R_C^2 + X_C^2} = \frac{X_L}{R_L^2 + X_L^2}$$

$$X_C(R_L^2 + X_L^2) = X_L(R_C^2 + X_C^2)$$

Substituting,  $X_C = \frac{1}{\omega_0 C}$ ;  $X_L = \omega_0 L$  we get

$$\frac{R_L^2 + \omega_0^2 L^2}{\omega_0 C} = \omega_0 L \left( R_C^2 + \frac{1}{\omega_0^2 C^2} \right)$$

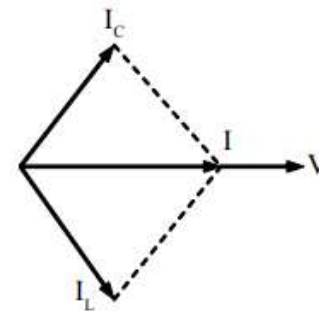

**Fig. 5.11 (b) Vector diagram**



$$R_L^2 + \omega_0^2 L^2 = \omega_0^2 L_c \left( \frac{\omega_0^2 R_c^2 C^2 + 1}{\omega_0^2 C^2} \right) \Rightarrow R_L^2 + \omega_0^2 L^2 = \frac{L}{C} (\omega_0^2 R_c^2 C^2 + 1)$$

$$R_L^2 + \omega_0^2 L^2 = \omega_0^2 R_c^2 LC + \frac{L}{C}$$

$$\omega_0^2 L^2 - \omega_0^2 R_c^2 LC = \frac{L}{C} - R_L^2$$

$$LC \omega_0^2 \left( \frac{L}{C} - R_c^2 \right) = \frac{L}{C} - R_L^2$$

$$\omega_0^2 = \frac{1}{LC} \left( \frac{\frac{L}{C} - R_L^2}{\frac{L}{C} - R_c^2} \right) = \frac{1}{LC} \left( \frac{R_L^2 - \frac{L}{C}}{R_c^2 - \frac{L}{C}} \right)$$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \sqrt{\frac{R_L^2 - \frac{L}{C}}{R_c^2 - \frac{L}{C}}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

**Thank You**

