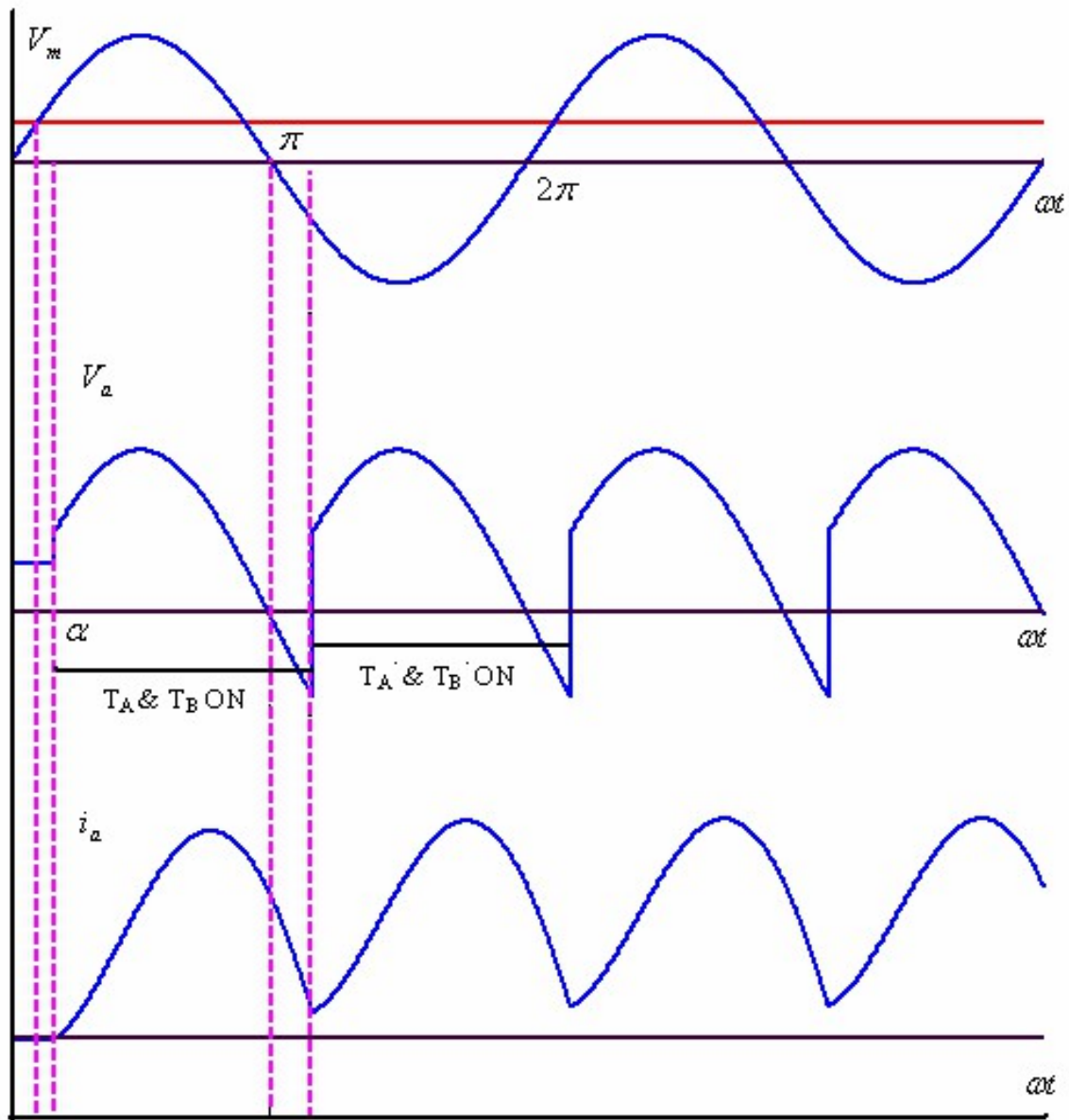


## 2.3 Continuous conduction

Let us assume that the armature current is continuous over the whole range of operation. Typical voltage and current waveforms are shown in Fig for semi-converter and full-converter systems, respectively. The thyristors are symmetrically triggered. In the semi-converter system shown in Fig. thyristor  $S_1$  is triggered at an angle  $\alpha$  and  $S_2$  at an angle  $\alpha + \pi$  with respect to the supply voltage  $v$ . In the full-converter system shown in Fig. thyristors  $S_1$  and  $S_3$  are simultaneously triggered at  $\alpha$ , thyristors  $S_2$  and  $S_4$  are triggered at  $\pi + \alpha$ .

In Fig. the motor is connected to the input supply for the period  $\alpha < \omega t < \pi$  through  $S_1$  and  $D_2$ , and the motor terminal voltage  $e_a$  is the same as the supply input voltage  $v$ . Beyond  $\pi$ ,  $e_a$  tends to reverse as the input voltage changes polarity. This will forward-bias the free-wheeling diode and DFW will start conducting. The motor current  $i_a$ , which was flowing from the supply through  $S_1$  is transferred to DFW (i.e.,  $S_1$  commutates). The motor terminals are shorted through the free-wheeling diode during  $\pi < \omega t < (\pi + \alpha)$ , making  $e_o$  zero. Energy from the supply is therefore delivered to the armature

Circuit when the thyristor conducts ( $\alpha$  to  $\pi$ ). This energy is partially stored in the inductance, partially stored in the kinetic energy (K.E.) of the moving system, and partially used to supply the mechanical load. During the free-wheeling period,  $\pi$  to  $\pi + \alpha$ , energy is recovered from the inductance and is converted to mechanical form to supplement the K.E. in supplying the mechanical load. The free-wheeling armature current continues to produce electromagnetic torque in the motor. No energy is feedback to the supply during this period.



**Figure 2.3.1 Continuous conduction waveform**

(Source: "Fundamentals of Electrical Drives" by G.K.Dubey, page-108)

In Fig. the motor is always connected to the input supply through the thyristors. Thyristors S1 and S3 conduct during the interval  $\alpha < \omega t < (\pi + \alpha)$  and connect the motor to the supply. At  $\pi + \alpha$ , thyristors S2 and S4 are triggered. Immediately the supply voltage appears across the thyristors S1 and S3 as a reverse-bias voltage and turns them off. This is called natural or line commutation. The motor current  $i_a$ , which was flowing from the supply through S1 and S3 is transferred to S2 and S4. During  $\alpha$  to  $\pi$ , energy flows from the input supply to the motor (both  $v$  and  $i_a$

are positive, and  $e_o$  and  $i_o$  are positive, signifying positive power flow). However, during  $7T$  to  $7T + a$ , some of the motor system energy is feedback to the input supply ( $v$  and  $I$  have opposite polarities and likewise  $e_a$  and  $i_o'$  signifying reverse power flow). Voltage and current waveforms are shown for a firing angle greater than  $90^\circ$ . The average motor terminal voltage  $E_o$  is negative. If the motor back emf  $E_g$  is reversed, it will behave as a de-generator and will feed power back to the ac supply. This is known as the inversion operation of the converter, and this mode of operation is used in the regenerative braking of the motor.

