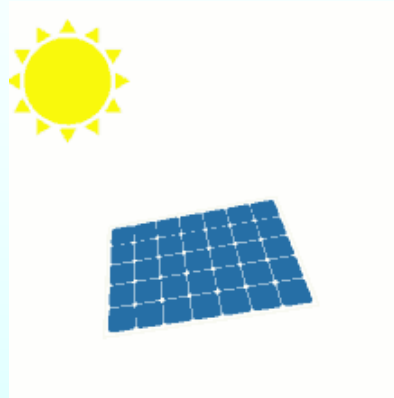


DC – Transient Response of RL Series Circuit



Mr.Ebbie Selva Kumar C

Assistant Professor/ EEE

Rohini College of Engineering and Technology



DC - Response of RL Series Circuit

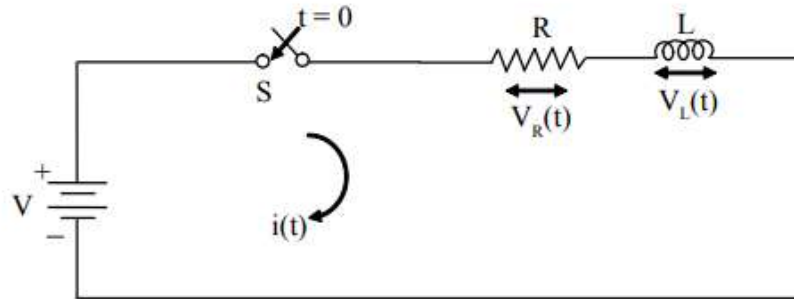


Fig. RL Series Circuit

Consider the RL series circuit excited by a DC source as shown in above fig. . At $t = 0$, switch s is closed. It is assumed that at the time of switching, the current is zero.

By applying kVL, $V = V_R(t) + V_L(t)$

$$V = Ri(t) + L \frac{di(t)}{dt} \quad \text{-----(5)}$$

Taking Laplace transform to equation (5), we get

$$\frac{V}{S} = RI(S) + L[SI(S) - i(0)]$$



Since $i(0) = 0$, the above equation becomes,

$$\frac{V}{S} = RI(S) + LSI(S)$$

$$\frac{V}{S} = I(S)[R + LS]$$

$$I(S) = \frac{V}{S(LS + R)} \text{-----(6)}$$

$$I(S) = \frac{V}{LS\left(S + \frac{R}{L}\right)}$$

By taking partial fraction to equation (6)

$$I(S) = \frac{V/L}{S\left(S + \frac{R}{L}\right)} = \frac{A}{S} + \frac{B}{S + R/L} \text{-----(7)}$$

$$A = \frac{V}{R}$$

$$\therefore B = -\frac{V}{R}$$



Substitute the value of A & B in equation (7), we get

$$I(S) = \frac{V/R}{S} - \frac{V/R}{S + R/L}$$

Applying Inverse laplace transform,

$$i(t) = \frac{V}{R}(1) - \frac{V}{R}e^{-R/L t} = \frac{V}{R}(1 - e^{-R/L t})$$

$$\text{Let } \frac{R}{L} = a$$

$$\therefore i(t) = \frac{V}{R}(1 - e^{-at}) \quad \text{-----(9)}$$

The current response of RL series circuit is shown in fig. 4.2.

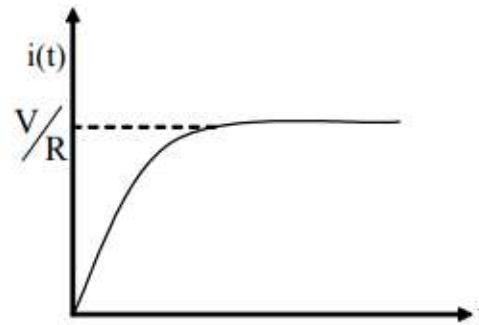


Fig. 3.2 Current response of RL series circuit



The transient voltages across the element of the circuit are obtained from the current.
The voltage across the resistor is,

$$\begin{aligned}V_R = Ri &= R \frac{V}{R} \left(1 - e^{-\frac{R}{L}t} \right) \\ &= V \left(1 - e^{-\frac{R}{L}t} \right)\end{aligned}$$

The voltage across the inductor is,

$$\begin{aligned}V_L = L \frac{di}{dt} &= L \frac{d}{dt} \left[\frac{V}{R} \left(1 - e^{-\frac{R}{L}t} \right) \right] \\ &= V e^{-\frac{R}{L}t}\end{aligned}$$



Thank You

