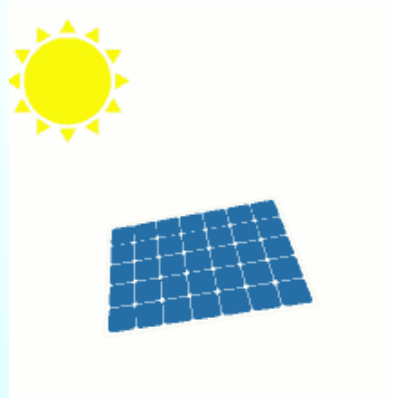


Norton's Theorem




Mr.Ebbie Selva Kumar C

Assistant Professor/ EEE

Rohini College of Engineering and Technology



Norton's Theorem

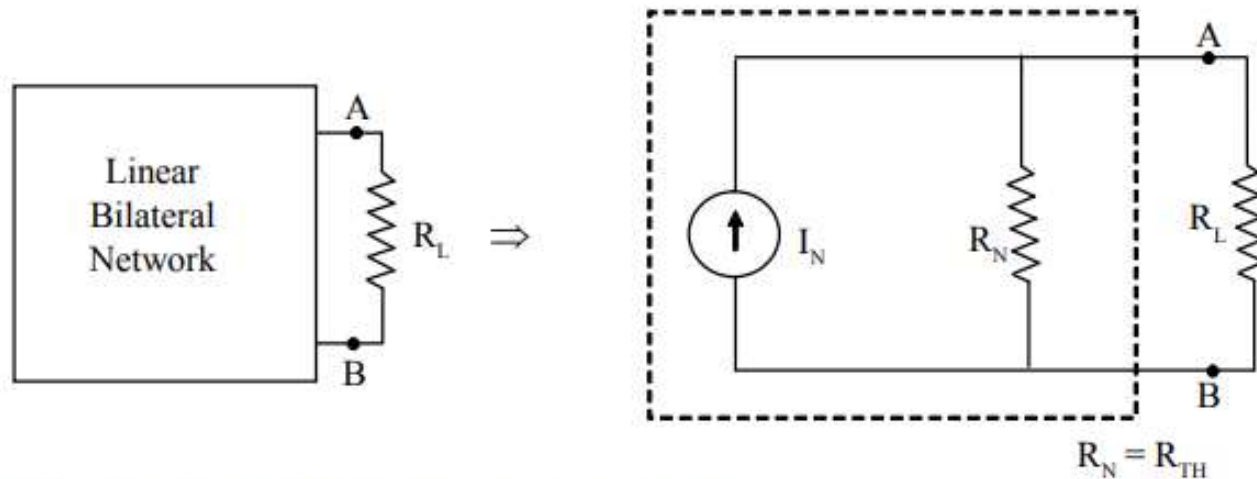

Norton's theorem is the duality of thevenin's theorem.

Statement :

“Any two terminal linear bilateral network having active and passive elements can be represented as a practical current source with I_N and R_N . I_N is the current flowing through the short circuit placed between A and B. R_N is same as R_{TH} . i.e., The resistance measured between A and B by reducing the energy sources to zero”.



Steps for solving a network using Norton's Theorem :


1. Replace load resistance (R_L) with a shortcircuit.
2. Calculate current through the short circuit using loop analysis or ohm's law or current division rule.
3. Calculate Norton's resistance looking from A & B.
4. Calculate I_L using current division rule.

$$I_L = I_N \frac{R_N}{R_N + R_L}$$




Proof :


Consider the circuit shown below

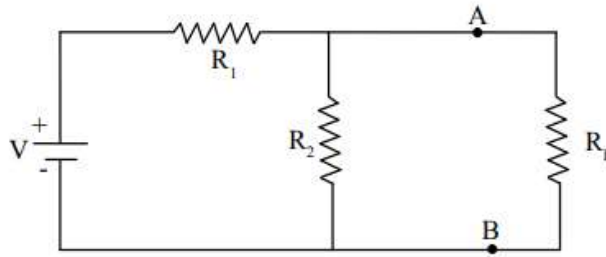

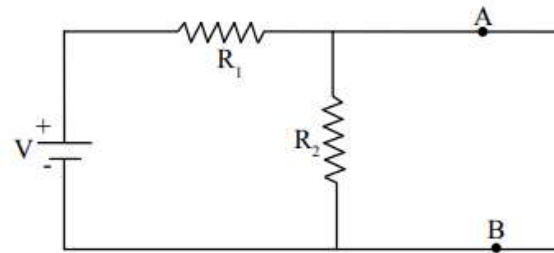1. Replace R_L with a short circuit as in below figure



2. Calculate the current I_N .

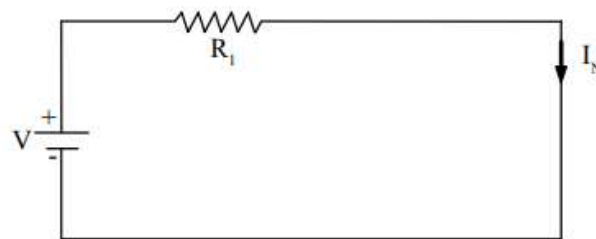


$$I_N = \frac{V}{R_1}$$

-----(6)




3. Calculate R_N .

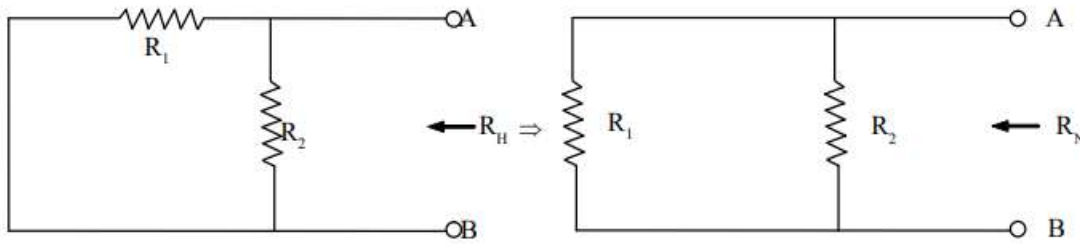

$$\therefore R_N = \frac{R_1 R_2}{R_1 + R_2}$$

-----(7)

4. Calculate I_L .

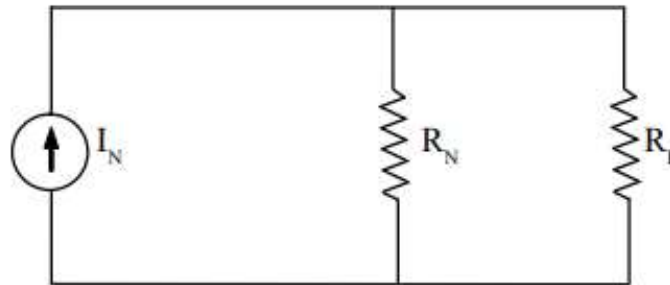

$$I_L = I_N \frac{R_N}{R_N + R_L}$$

-----(8)



Thank You

