

## Rectification

**The process of converting alternating current into direct current is called rectification.** In this section, we will discuss two types of rectifiers namely, half wave rectifier and full wave rectifier.

### 1. Half wave rectifier circuit


The half wave rectifier circuit is shown in Figure 9.17(a). The circuit consists of a transformer, a p-n junction diode and a resistor. In a half wave rectifier circuit, either a positive half or the negative half of the AC input is passed through while the other half is blocked. Only one half of the input wave reaches the output. Therefore, it is called half wave rectifier. Here, a p-n junction diode acts as a rectifier diode.

#### *During the positive half cycle*

When the positive half cycle of the ac input signal passes through the circuit, terminal A becomes positive with respect to terminal B. The diode is forward biased and hence it conducts. The current flows through the load resistor  $R_L$  and the AC voltage developed across  $R_L$  constitutes the output voltage  $V_0$  and the waveform of the diode current is shown in Figure 9.17(b).

#### *During the negative half cycle*

When the negative half cycle of the ac input signal passes through the circuit, terminal A is negative with respect to terminal B. Now the diode is reverse biased and does not conduct and hence no current passes through  $R_L$ . The reverse saturation current in a diode is negligible. Since there is no voltage drop across  $R_L$ , the negative half cycle of ac supply is suppressed at the output. The output waveform is shown in Fig.

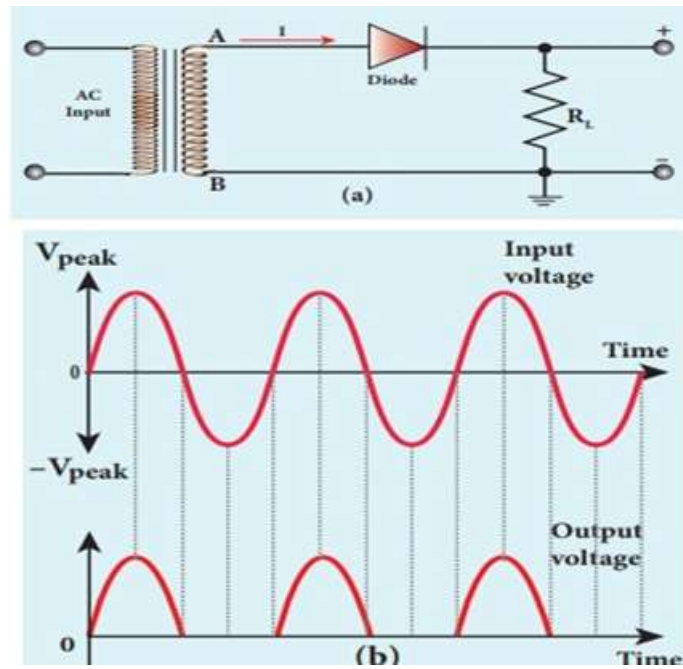

**Figure 1.4.1 Half wave rectifier**

Diagram Source Brain Kart



The output of the half wave rectifier is not a steady dc voltage but a pulsating wave. This pulsating voltage can not be used for electronic equipments. A constant or a steady voltage is required which can be obtained with the help of filter circuits and voltage regulator circuits.

**Efficiency ( $\eta$ ) is the ratio of the output dc power to the ac input power supplied to the circuit.**

Its value for half wave rectifier is 40.6 %

### **Full wave rectifier**

The positive and negative half cycles of the AC input signal pass through the full wave rectifier circuit and hence it is called the full wave rectifier. The circuit is shown in Figure 9.18(a). It consists of two p-n junction diodes, a center tapped transformer, and a load resistor ( $RL$ ) .

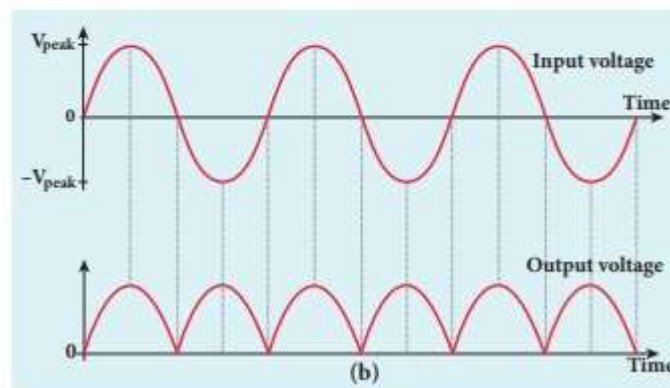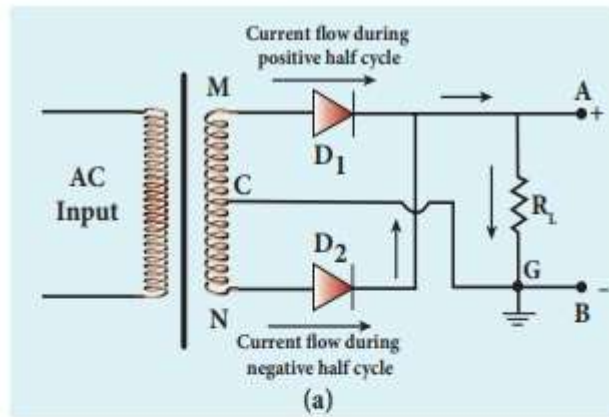

**Figure 9.18** (a) Full wave rectifier circuit  
(b) Input and output waveforms

### Figure 1.4.2 Full Wave rectifier

Diagram Source Brain Kart

The centre is usually taken as the ground or zero voltage reference point. Due to the centre tap transformer, the output voltage rectified by each diode is only one half of the total secondary voltage.

#### *During positive half cycle*

When the positive half cycle of the ac input signal passes through the circuit, terminal M is positive, G is at zero potential and N is at negative potential. This forward biases diode  $D_1$  and reverse biases diode  $D_2$ . Hence, being forward biased, diode  $D_1$  conducts and current flows along the path  $MD_1AGC$ . As a result, positive half cycle of the voltage appears across  $R_L$  in the direction G to C

***During negative half cycle***

When the negative half cycle of the ac input signal passes through the circuit, terminal N is positive, G is at zero potential and M is at negative potential. This forward biases diode  $D_2$  and reverse biases diode  $D_1$ . Hence, being forward biased, diode  $D_2$  conducts and current flows along the path  $ND_2 BGC$ . As a result, negative half cycle of the voltage appears across  $R_L$  in the same direction from G to C.



Hence in a full wave rectifier both positive and negative half cycles of the input signal pass through the load in the same direction as shown in Figure 9.18(b). Though both positive and negative half cycles of ac input are rectified, the output is still pulsating in nature.

The efficiency ( $\eta$ ) of full wave rectifier is twice that of a half wave rectifier and is found to be 81.2%. It is because both the positive and negative half cycles of the ac input source are rectified.

***Bridge rectifier***

A bridge rectifier is shown in Fig. There are four diodes  $D_1$ ,  $D_2$ ,  $D_3$  and  $D_4$  used in the circuit, which are connected to form a network. The input ends A and C of the network are connected to the secondary ends  $S_1$  and  $S_2$  of the transformer. The output ends B and D are connected to the load resistance  $R_L$ .



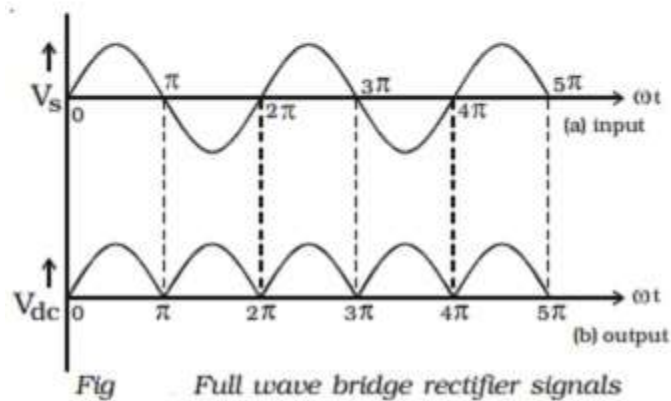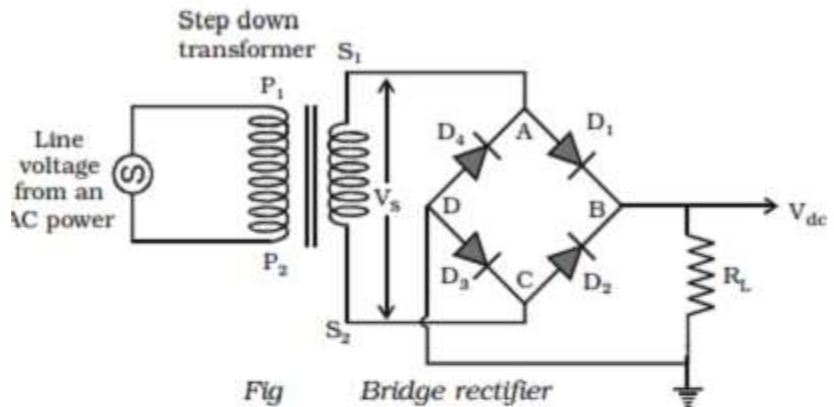

**Figure 1.4.3 Bridge rectifier**

Diagram Source Brain Kart

During positive input half cycle of the a.c. voltage, the point A is positive with respect to C. The diodes  $D_1$  and  $D_3$  are forward biased and conduct, whereas the diodes  $D_2$  and  $D_4$  are reverse biased and do not conduct. Hence current flows along  $S_1ABDCS_2$  through  $R_L$ . During negative half cycle, the point C is positive with respect to A. The diodes  $D_2$  and  $D_4$  are forward biased and conduct, whereas the diodes  $D_1$  and  $D_3$  are reverse biased and they do not conduct. Hence current flows along  $S_2CBDAS_1$  through  $R_L$ . The same process is repeated for subsequent half cycles. It can be seen that, current flows through  $R_L$  in the same direction, during both half cycles of the input a.c. signals. The output signal corresponding to the input signal is shown in Fig. The efficiency of the bridge rectifier is approximately 81.2%.

