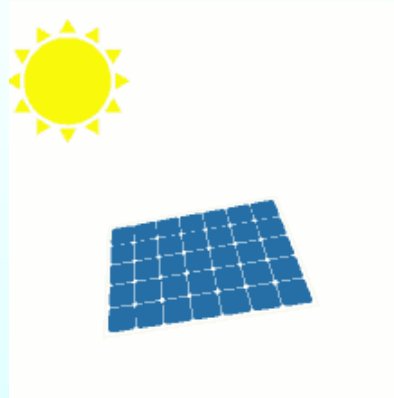


Three Branch Parallel RLC circuits



Mr.Ebbie Selva Kumar C

Assistant Professor/ EEE

Rohini College of Engineering and Technology



Three Branch Parallel RLC circuits :

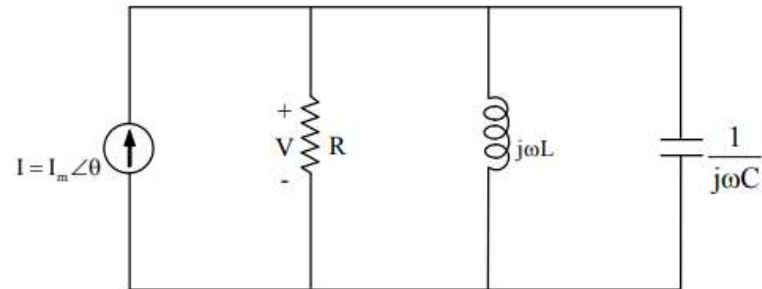


Fig. 5.9 Parallel RLC Circuit

Parallel RLC is the dual of series RLC. Fig. 5.9 shows the three branch parallel RLC circuit.

$$\text{The circuit admittance is, } Y = \frac{I}{V} = \frac{1}{R} + j\omega C + \frac{1}{j\omega L}$$

$$\text{(or) } Y = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$

Resonance occurs when imaginary part of Y is zero,

$$\omega C - \frac{1}{\omega L} = 0 \Rightarrow \frac{1}{X_C} - \frac{1}{X_L} = 0 \Rightarrow X_L = X_C$$

(or)

$$\Rightarrow \omega_0 L = \frac{1}{\omega_0 C} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \text{ sec.}$$

$$\text{The resonant frequency in Hz is } f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$



The voltage V vs frequency curve is shown in fig. 5.10. At resonance, parallel LC acts like open circuit. So, the entire current flows through R . Also, I_C & I_L can be much more than source current at resonance.

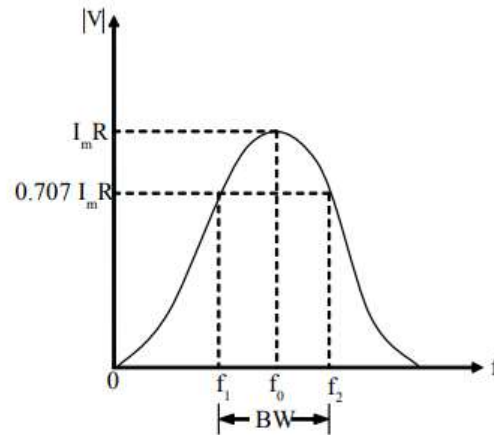


Fig. 5.10 Voltage V vs frequency curve

By comparing Z in series RLC and Y in parallel RLC & replacing R, L, C with $1/R, 1/L, 1/C$,

$$\therefore \omega_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}; \quad \omega_2 = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\text{Bandwidth, } BW = \omega_2 - \omega_1 = \frac{1}{RC}$$

$$\text{Quality factor, } Q = \frac{\omega_0}{B} = \omega_0 R C = \frac{R}{\omega_0 L}$$

For high Q -circuits, ($Q \geq 10$)

$$\omega_1 \approx \omega_0 - \frac{BW}{2}; \quad \omega_2 \approx \omega_0 + \frac{BW}{2}$$



Thank You

