

## D.C & A.C Bridges

Bridge circuits are used very commonly as a variable conversion element in measurement systems and produce an output in the form of a voltage level that changes as the measured physical quantity changes. They provide an accurate method of measuring resistance, inductance and capacitance values, and enable the detection of very small changes in these quantities about a nominal value. They are of immense importance in measurement system technology because so many transducers measuring physical quantities have an output that is expressed as a change in resistance, inductance or capacitance. The displacement-measuring strain gauge, which has a varying resistance output, is but one example of this class of transducers. Normally, excitation of the bridge is by a d.c. voltage for resistance measurement and by an a.c. voltage for inductance or capacitance measurement. Both null and deflection types of bridge exist, and, in a like manner to instruments in general, null types are mainly employed for calibration purposes and deflection types are used within closed-loop automatic control schemes.

### Null-type, d.c. bridge (Wheatstone bridge)

A null-type bridge with d.c. excitation, commonly known as a Wheatstone bridge, has the form shown in Figure 7.1. The four arms of the bridge consist of the unknown resistance  $R_u$ , two equal value resistors  $R_2$  and  $R_3$  and a variable resistor  $R_v$  (usually a decade resistance box). A d.c. voltage  $V_i$  is applied across the points AC and the resistance  $R_v$  is varied until the voltage measured across points BD is zero. This null point is usually measured with a high sensitivity galvanometer.

To analyse the Wheatstone bridge, define the current flowing in each arm to be  $I_1 \dots I_4$  as shown in Figure 3.1. Normally, if a high impedance voltage-measuring instrument is used, the current  $I_m$  drawn by the measuring instrument will be very small and can be approximated to zero. If this assumption is made, then, for  $I_m \approx 0$ :

$$I_1 = I_3 \text{ and } I_2 = I_4 \quad 3.1$$


$$I_1 = I_3 \quad \text{and} \quad I_2 = I_4$$

Looking at path ADC, we have a voltage  $V_i$  applied across a resistance  $R_u + R_3$  and by Ohm's law:

$$I_1 = \frac{V_i}{R_u + R_3}$$

Similarly for path ABC:

$$I_2 = \frac{V_i}{R_v + R_2}$$

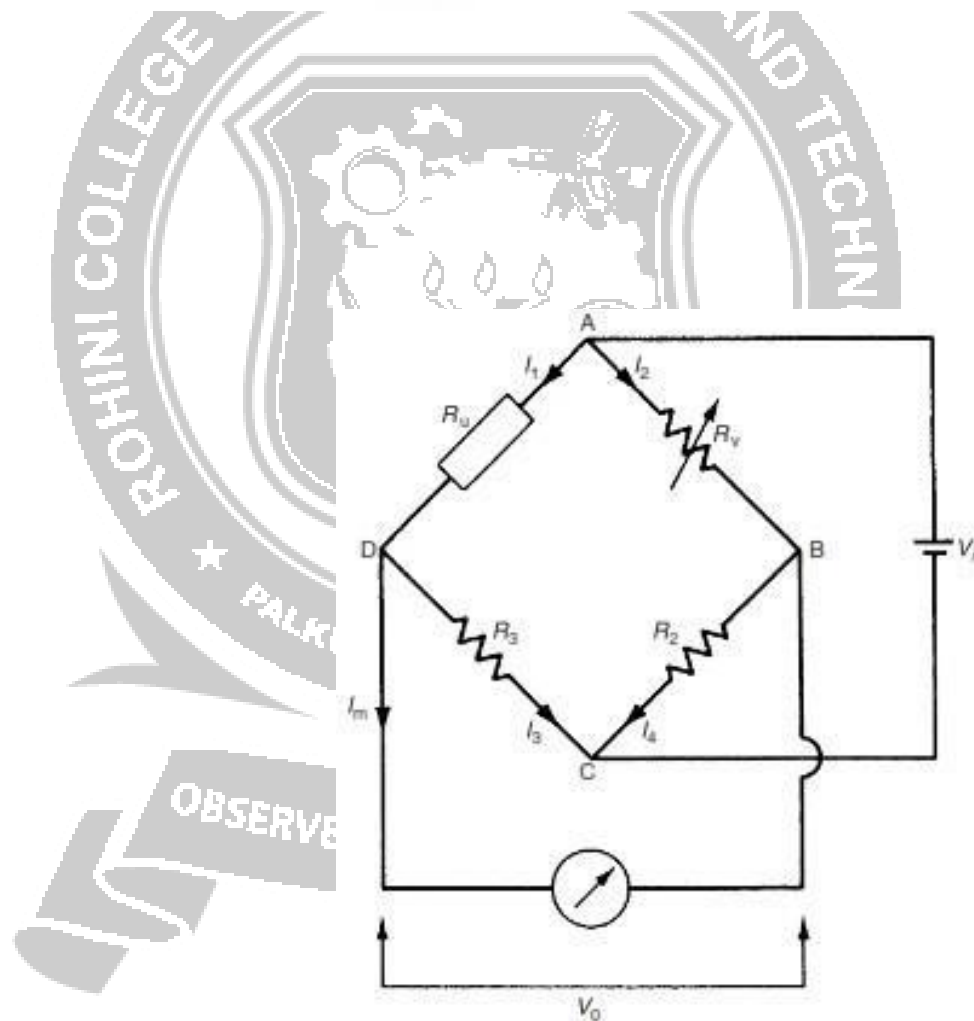

Now we can calculate the voltage drop across AD and AB:

$$V_{AD} = I_1 R_v = \frac{V_i R_u}{R_u + R_3}; \quad V_{AB} = I_2 R_v = \frac{V_i R_v}{R_v + R_2}$$

By the principle of superposition,

$$V_0 = V_{BD} = V_{BA} + V_{AD} = -V_{AB} + V_{AD}$$

Thus:

$$V_0 = -\frac{V_i R_v}{R_v + R_2} + \frac{V_i R_u}{R_u + R_3}$$

At the null point  $V_0 = 0$ , so:

$$\frac{R_u}{R_u + R_3} = \frac{R_v}{R_v + R_2}$$

Inverting both sides:

$$\frac{R_u + R_3}{R_u} = \frac{R_v + R_2}{R_v} \quad \text{i.e.} \quad \frac{R_3}{R_u} = \frac{R_2}{R_v} \quad \text{or} \quad R_u = \frac{R_3 R_v}{R_2}$$

Thus, if  $R_2 = R_3$ , then  $R_u = R_v$ . As  $R_v$  is an accurately known value because it is derived from a variable decade resistance box, this means that  $R_u$  is also accurately known.

### Deflection-type d.c. bridge

A deflection-type bridge with d.c. excitation is shown in Figure 3.2. This differs from the Wheatstone bridge mainly in that the variable resistance  $R_v$  is replaced by a fixed resistance  $R_1$  of the same value as the nominal value of the unknown resistance  $R_u$ . As the resistance  $R_u$  changes, so the output voltage  $V_0$  varies, and this relationship between  $V_0$  and  $R_u$  must be calculated.

This relationship is simplified if we again assume that a high impedance voltage measuring instrument is used and the current drawn by it,  $I_m$ , can be approximated to zero. (The case when this assumption does not hold is covered later in this section.). The analysis is then exactly the same as for the preceding example of the Wheatstone bridge, except that  $R_v$  is replaced by  $R_1$ . Thus, from equation (3.1),

$$V_0 = V_i * \left( \frac{R_u}{R_u + R_3} \right) - \left( \frac{R_1}{R_1 + R_2} \right) V_i$$

When  $R_u$  is at its nominal value, i.e. for  $R_u = R_1$ , it is clear that  $V_0 = 0$  (since  $R_2 = R_3$ ). For other values of  $R_u$ ,  $V_0$  has negative and positive values that vary in a non-linear way with  $R_u$ .

