
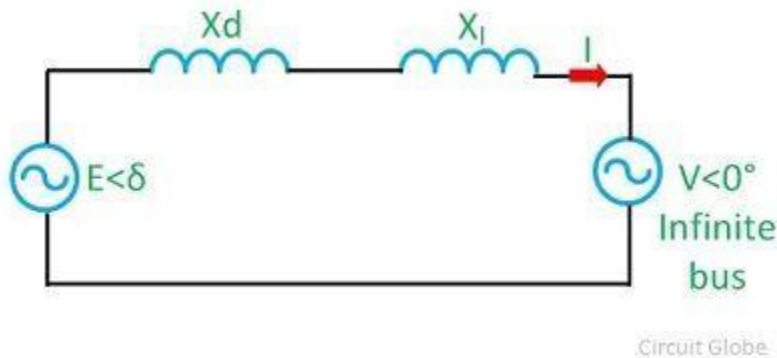


Power-Angle Curve

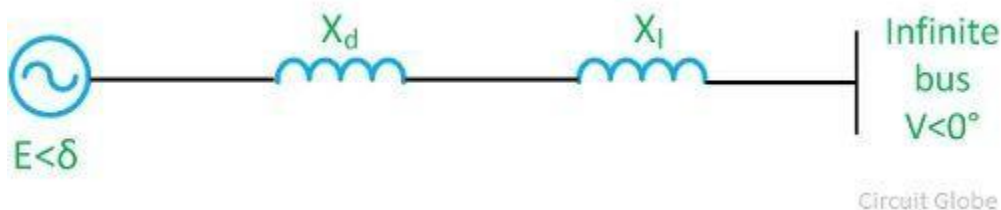Consider a synchronous machine connected to an infinite bus through a transmission line of reactance X_l shown in a figure below. Let us assume that the resistance and capacitance are neglected.



Equivalent diagram of synchronous machine connected to an infinite bus through a transmission line of series reactance X_l is shown below:



Let, $V = V \angle 0^\circ$ – voltage of infinite bus, $E = E \angle \delta$ – voltage behind the direct axis synchronous reactance of the machine, X_d = synchronous / transient reactance of the machine. The complex power delivered by the generator to the system is

$$S = VI$$

$$S = V \left[\frac{E \angle \delta - V \angle 0^\circ}{j(X_d + X_l)} \right]$$

$$X_d + X_l = X$$

Let,

$$S = V \left[\frac{E \angle \delta}{X \angle 90^\circ} + j \frac{V}{X} \right]$$

$$S = \frac{EV}{X} \angle (90^\circ - \delta) - j \frac{V^2}{X}$$

$$S = V \left[\frac{EV}{X} \sin \delta + j \frac{EV}{X} \cos \delta - j \frac{V^2}{X} \right]$$

$$P_e + jQ_e = \frac{EV}{X} \sin \delta + j \left(\frac{EV}{X} \cos \delta - \frac{V^2}{X} \right)$$

Active power transferred to the system

$$P_e = \frac{EV}{X} \sin \delta$$

The reactive power transferred to the system

$$Q_e = \frac{EV}{X} \cos \delta - \frac{V^2}{X}$$


The maximum steady-state power transfers occur when $\delta = 90^\circ$

$$P_e = \frac{EV}{X} \sin 90^\circ$$

$$(\sin 90^\circ = 1)$$

$$P = \frac{EV}{X} \quad P_e = P_{emax} \sin \delta$$

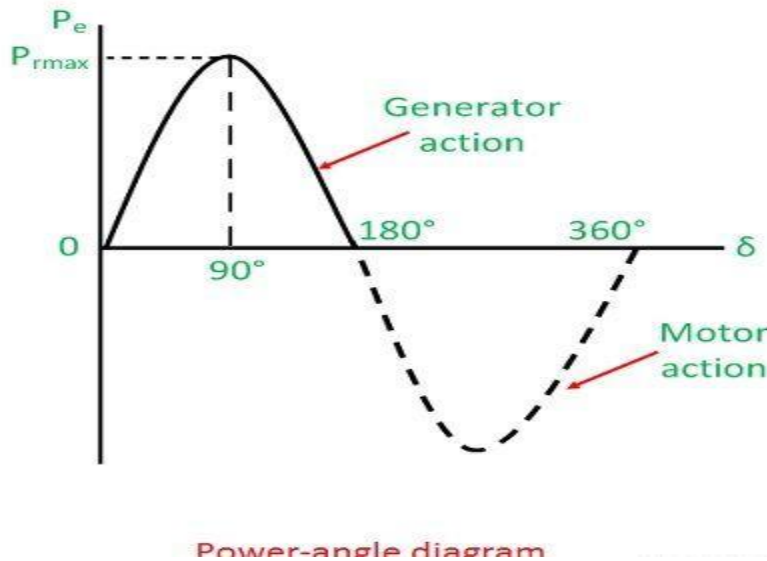The graphical representation of P_e and the load angle δ is called the power angle curve. It is widely used in power system stability studies. The power angle curve is shown below



Maximum power is transferred when $\delta = 90^\circ$. As the value of load angle δ is above 90° , P_e decrease and becomes zero at $\delta = 180^\circ$. Above 180° , P_e becomes negative, which show that the direction of power flow is reversed, and the power is supplied from infinite bus to the generator. The value of P_e is often called pull out power. It is also called the steady-state limit.

The total reactance between two voltage sources E and X is called the transfer reactance. The maximum power limit is inversely proportion to the transfer reactance.