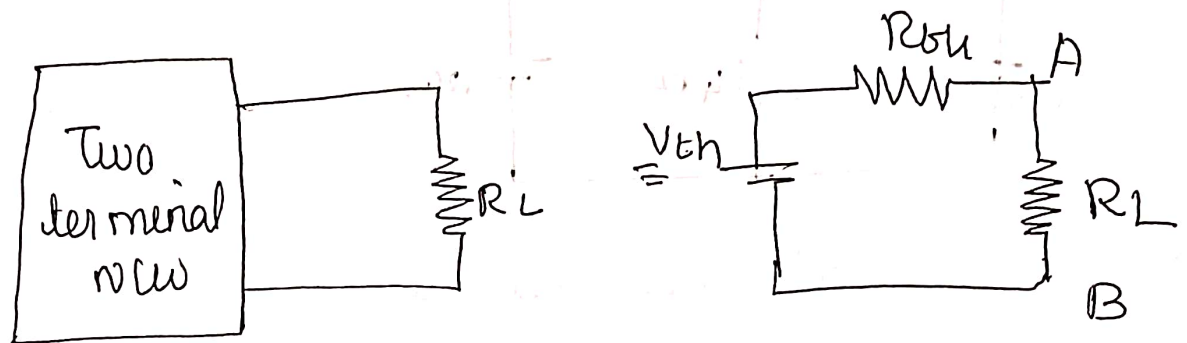


Thevenin's Theorem.


Any two terminal, bi-lateral linear network can be replaced by an equivalent circuit that consist of a single voltage source (V_{th}) connected in series with resistance R_{th} .




Procedure

- step 1 :- Remove the load resistor R_L and find the open circuit voltage V_{th} across the load terminal.
- step 2 :- short circuit all voltage sources and open circuit all current sources. find R_{th} looking through load terminal.
- step 3 :- obtain thevenine equivalent circuit by replacing V_{th} in series with R_{th} and adding the load resistance.

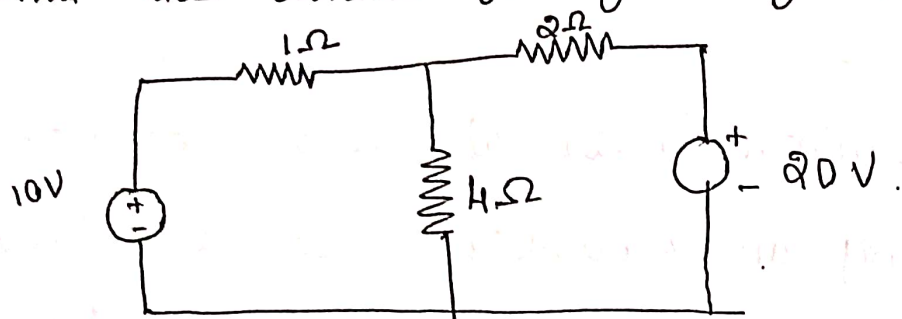(19)
1) Find the current flowing through the 2Ω resistor.



1) Remove the load to find V_{th} .

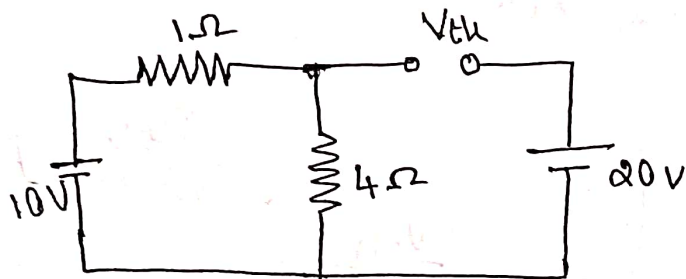

Apply KVL to loop 1

$$10V - (1+4)i = 0$$

$$5i = 10$$

$$i = \frac{10}{5} = 2A$$


∴ voltage across 4Ω is $4 \times 2 = 8V$

∴ V_{th} is difference b/w 8 and 20.

$$\therefore V_{th} = 20 - 8$$

$$\boxed{V_{th} = 12V}$$

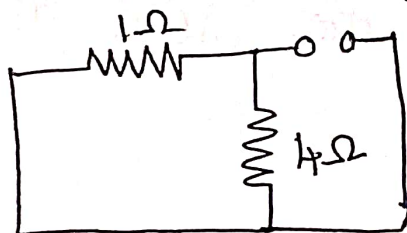
To find R_{th} . s.c vlg source, OC at source



$$R_{th} = 1\Omega \parallel 4\Omega$$

$$R_{th} = \frac{1 \times 4}{4+1} = \frac{4}{5}$$

(20)

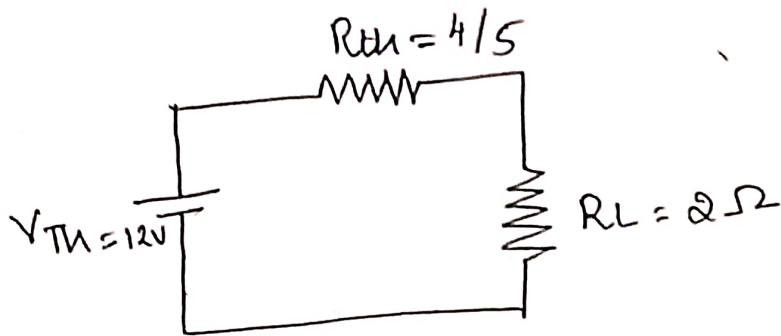


$$\hat{I} = \frac{V}{R} = \frac{12}{\frac{4}{5} + 2}$$

$$= \frac{12 \times 5}{4 + 10} = \frac{5 \times 12}{14} = \frac{30}{7}$$

$$\hat{I}_L = 4.28 \text{ A}$$


$\therefore$ it is series ckt.

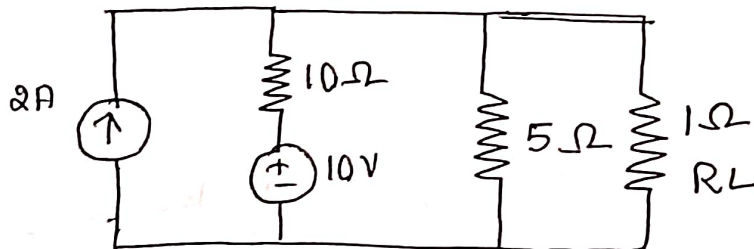2. Find the power loss in 1Ω resistor in given ckt using Thevenin's theorem.



Soln

1) To Find V_{TH} remove R_L

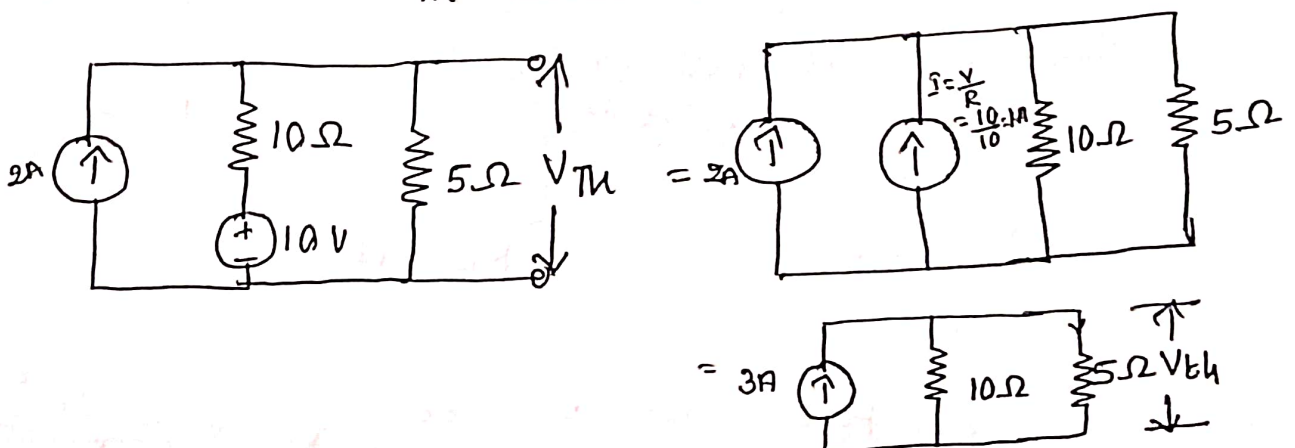

(21)

$$I \text{ through } 5\Omega = 3 \times \frac{10}{10+5}$$

[Ct. divider Rule]

$$= 3 \times \frac{10}{15}$$

$$I_{5\Omega} = 2A$$


$$V_{Th} = I_{5\Omega} \times 5$$

$$= 2 \times 5$$

$$V_{Th} = 10V$$

To find R_{Th}

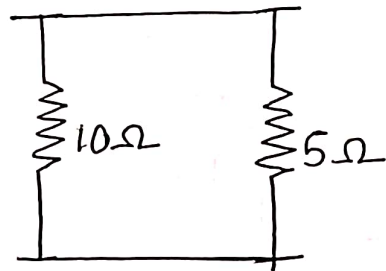
Remove R_L , s.c. v/dg source, o.c. ct source



$$R_{Th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{10 \times 5}{10 + 5} = \frac{10 \times 5}{15}$$

$$R_{Th} = 3.33\Omega$$

Thevenine equivalent ct is

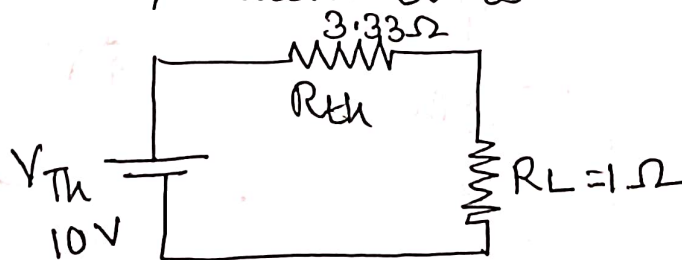

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

$$= \frac{10}{3.33 + 1} = \frac{10}{4.33}$$


$$I_L = 2.309$$

$$\therefore \text{Power loss across } R_L = \frac{I_L^2}{1} = \frac{(2.309)^2}{1} = 5.33W$$

(20)


(22)

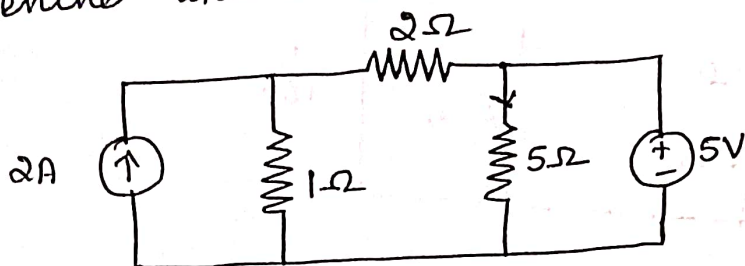3) Find the current through 5Ω resistor using Thevenine theorem.




Solu

Remove 5Ω and find V_{th} .

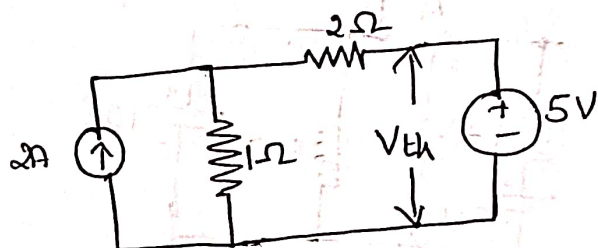

$$V_{th} = 5V$$

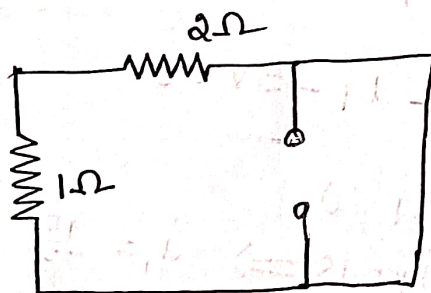To find R_{th} b.c. vltg source & o.c ct source. Remove R_L .




$$R_{th} = 2\Omega \parallel 3\Omega = \frac{2 \times 3}{2+3} = \frac{6}{5}$$

$$R_{th} = 3\Omega \parallel 0\Omega$$

$$R_{th} = 0$$


Thevenine ckt

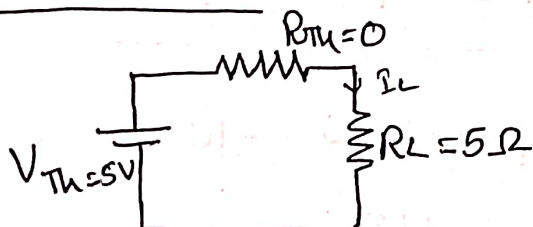


$$I_L = \frac{V_{th}}{R_L} = \frac{5}{5}$$

$$I_L = 1A$$

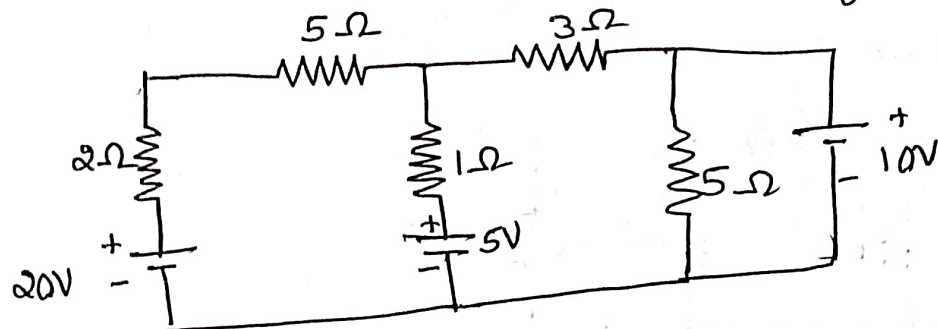23 Find the power across 3Ω using Thevenin's Theorem



To find V_{th} :- Remove 3Ω .

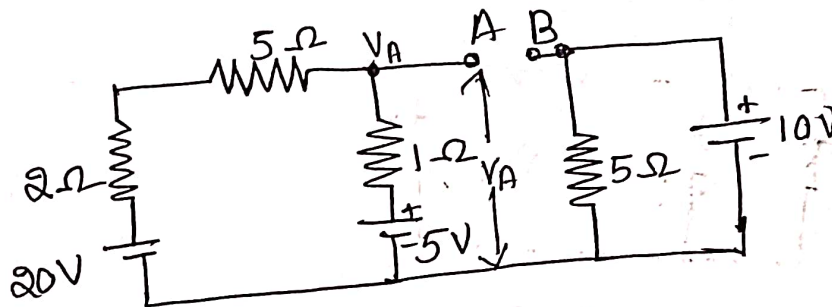

$$V_{th} = V_A - V_B.$$

Apply KVL to loop 1

By node vlg,

$$\frac{V_A - 20}{1} = \frac{V_A - 5}{1}$$

$$V_A - 20 = V_A - 5$$

$$6V_A = 15$$

$$V_A = \frac{15}{6}$$

=

$$V_{th} = +6.875 - 10$$

$$= -3.125V$$

To find R_{th}

Remove R_L , s.c vlg source, o.c at same

$$20V - 7i_1 - i_1 - 5V = 0$$


$$15 - 8i_1 = 0$$

$$8i_1 = 15 \Rightarrow i_1 = \frac{15}{8} \Rightarrow i_1 = 1.875A$$

$$V_A = +i_1 \times 1 + 5$$


$$= +1.875 + 5 = +6.875V$$

24 23

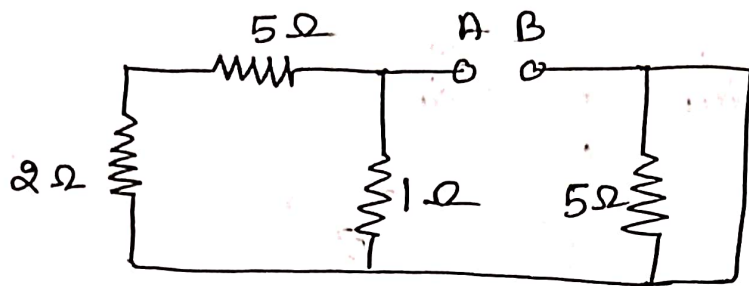

$$R_{th} = (2+5) \parallel 1 = \frac{7 \times 1}{7+1} = \frac{7}{8}$$

$$R_{th} = 0.875 \Omega$$

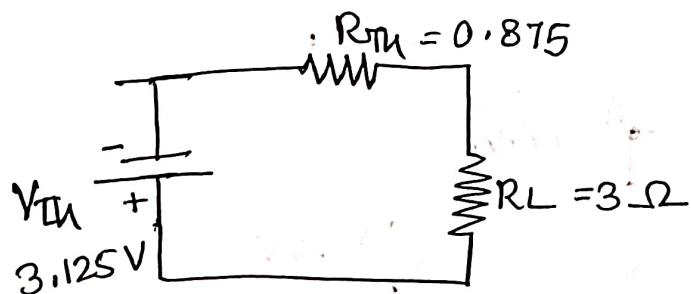


$$I_L = \frac{-3.125}{3.875} = -0.8065 A$$




$$\text{Power square} = I^2 R_L = (-0.806)^2 \times 3$$

$$P = 1.94 W$$

5) Find current through 1Ω .

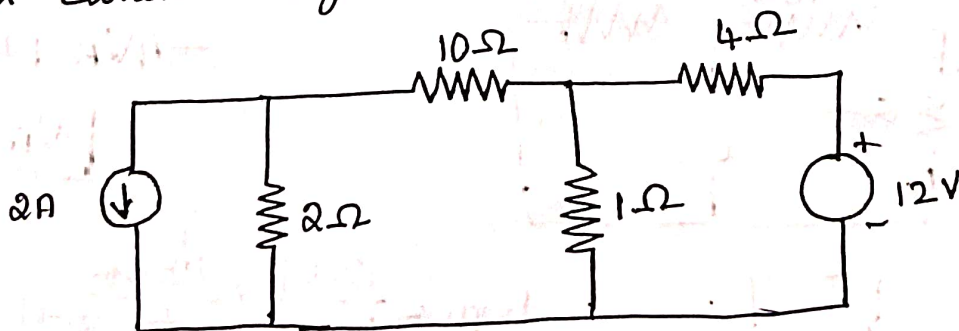

25 To Find V_{TH} remove 1Ω

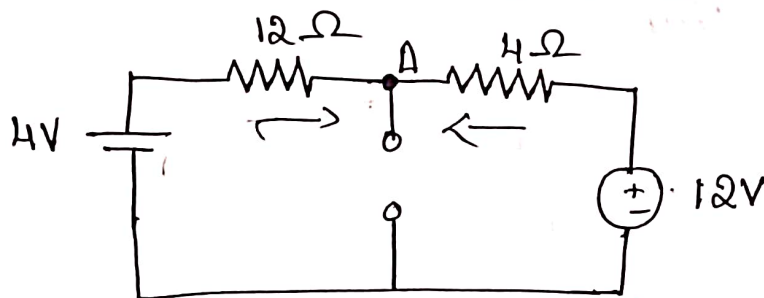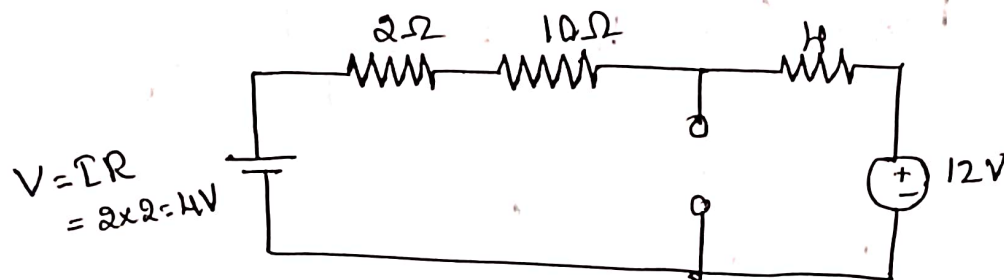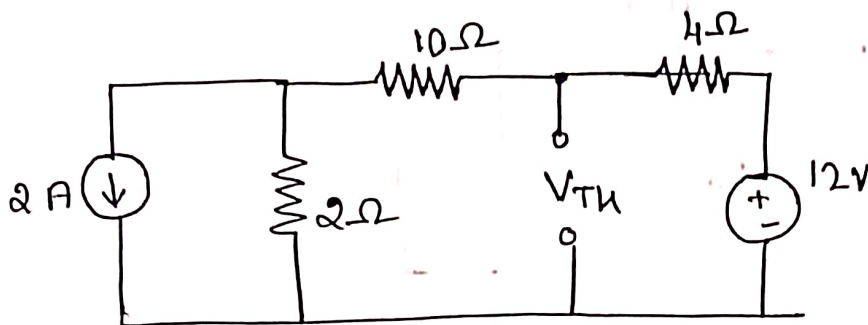

$$\frac{V_A - 4}{3 \times 2} = \frac{V_A - 12}{4}$$

$$V_A - 4 = 3V_A - 36$$

$$32 = 2V_A$$

$$V_A = 16$$

$$\frac{4 - V_A}{12} + \frac{12 - V_A}{4} = 0$$

$$\frac{4 - V_A}{3} + \frac{12 - V_A}{1} = 0$$



$$4 - V_A + 36 - 3V_A = 0$$

$$2V_A + 40 = 0$$

$$-4V_A + 40 = 0$$

$$V_A = 10$$

To Find R_{TH} .

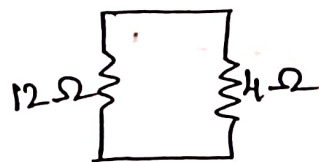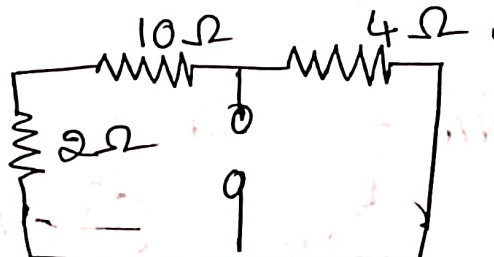

$$R_{TH} = \frac{12 \times 4}{12 + 4} = \frac{12 \times 4}{16} = 3\Omega$$

