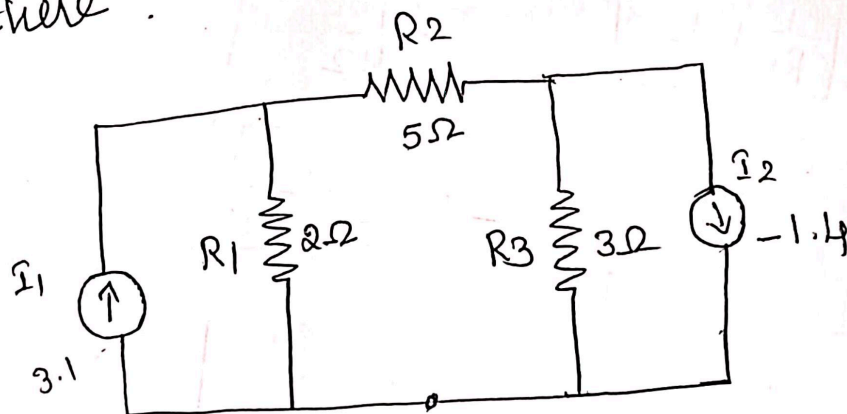


Node analysis (Branch current method) 34


This method is used to determine voltage b/w nodes. It has the following steps.

- 1) Convert vly source to current source
- 2) Identify the nodes & choose the reference node.
- 3) choose the reference node such that maximum number of components are connected.
- 4) Give number to other nodes and corresponding voltage $V_1, V_2, \dots$
- 5) if n nodes are there $(n-1)$ expressions will be there.

1)



The ckt can be re-drawn as.

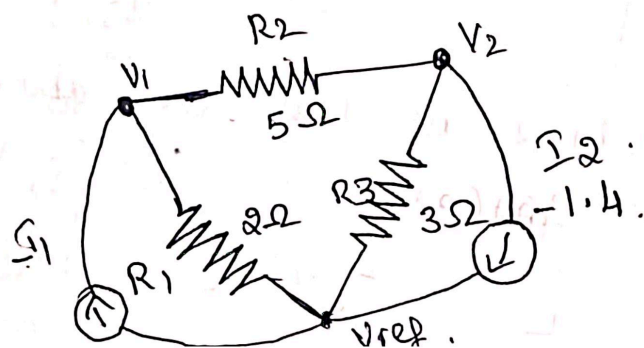

35) Apply KCL to node 1

$$I_1 = \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2}$$

$$I_1 = \frac{V_1}{R_1} + \frac{V_1}{R_2} - \frac{V_2}{R_2}$$

$$I = V_1 \left[\frac{1}{R_1} + \frac{1}{R_2} \right] - \frac{V_2}{R_2}$$

Apply KCL at N_2 .

$$I_2 + \frac{V_2}{R_3} + \frac{V_2 - V_1}{R_2} = 0$$

$$\frac{V_2}{R_3} + \frac{V_2}{R_2} - \frac{V_1}{R_2} = -I_2$$

$$-V_1 \left[\frac{1}{R_2} \right] + V_2 \left[\frac{1}{R_3} + \frac{1}{R_2} \right] = -I_2 \quad \text{--- (2)}$$

$$+V_1 \left(\frac{1}{R_2} \right) - V_2 \left[\frac{1}{R_3} + \frac{1}{R_2} \right] = (+) I_2$$

$$\begin{bmatrix} \left[\frac{1}{R_1} + \frac{1}{R_2} \right] & -\frac{1}{R_2} \\ +\frac{1}{R_2} & -\left[\frac{1}{R_2} + \frac{1}{R_3} \right] \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \begin{bmatrix} 3.1 \\ -1.4 \end{bmatrix}$$

$R_1 = 2, R_2 = 5$
 $R_3 = 3$
 $I_1 = 3.1, I_2 = -1.4$

conductance are given then above matrix become

$$\begin{bmatrix} (G_1 + G_2) & -G_2 \\ G_2 & -(G_2 + G_3) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\Delta = -0.371 + 0.071$$

$$V_1 = \frac{\Delta V_1}{\Delta} = \begin{bmatrix} 3.1 & -1/5 \\ -1.4 & -[1/5 + 1/3] \end{bmatrix}$$

$$= \begin{bmatrix} 3.1 & -0.2 \\ -1.4 & -0.53 \end{bmatrix}$$

$$0.297$$

$$V_1 = \frac{-1.643 - 0.28}{0.297 + 0.331} = 1.92$$


$$V_1 = 5.8V \quad (\text{should be } 5)$$

$$V_2 = \frac{\Delta V_2}{\Delta} = \begin{bmatrix} 0.7 & 3.1 \\ 0.2 & -1.4 \end{bmatrix} = \begin{bmatrix} 0.98 & 0.62 \\ 0.331 & 0.36 \end{bmatrix}$$


$$V_2 = 1.08$$

(should be 2)

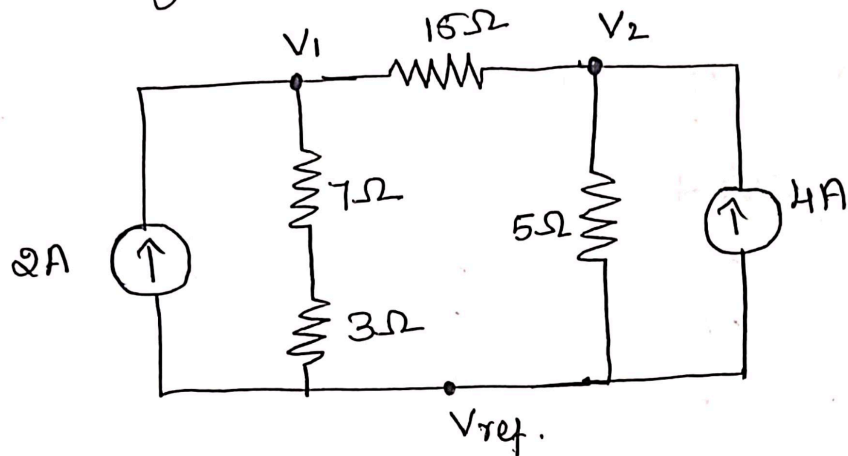2) Determine the current flowing left to right through the 15Ω resistor of fig 4.2a. (36)



soln The circuit can be redrawn as.

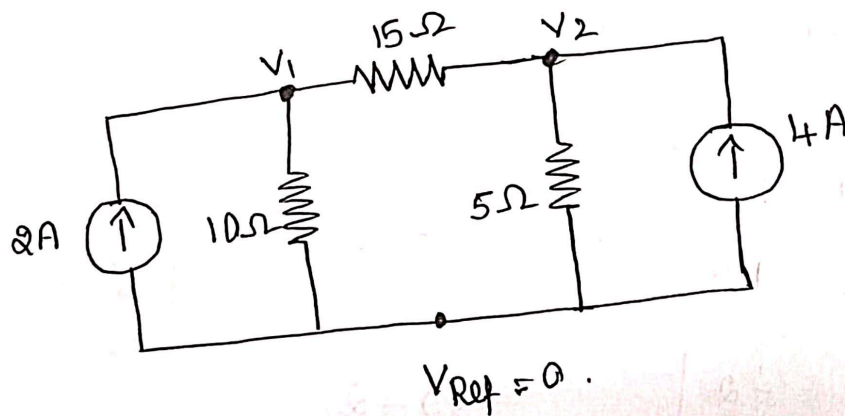

$$\frac{5 \times 15 \times 10}{3 \times 2}$$

KCL at Node 1

$$2A = \frac{V_1}{10} + \frac{V_1 - V_2}{15}$$

$$= \frac{V_1}{10} + \frac{V_1}{15} - \frac{V_2}{15}$$

$$2A = V_1 \left[\frac{1}{10} + \frac{1}{15} \right] - \frac{V_2}{15}$$

Rearranging

$$2 = \left[\frac{3+2}{30} \right] V_1 - \frac{2V_2}{30}$$

$$60 = 5V_1 - 2V_2 \quad \text{--- (2)}$$

$$\text{--- (1)}$$

KCL at node 2

$$0 = \frac{V_2 - V_1}{15} + \frac{V_2}{5} \quad \text{--- (3)}$$

(97)

$$4 = \frac{V_2 - V_1}{15} + \frac{3V_2}{15}$$

$$60 = V_2 - V_1 + 3V_2$$

$$60 = -V_1 + 4V_2 \quad \text{--- (2)}$$

$$5V_1 - 2V_2 = 60 \quad \text{--- (A)}$$

$$-V_1 + 4V_2 = 60 \quad \text{--- (B)}$$

$$\begin{bmatrix} 5 & -2 \\ -1 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 60 \\ 60 \end{bmatrix}$$

$$V_1 = \frac{\Delta V_1}{\Delta} = \frac{\begin{bmatrix} 60 & -2 \\ 60 & 4 \end{bmatrix}}{\begin{vmatrix} 5 & -2 \\ -1 & 4 \end{vmatrix}} = \frac{+240 + 120}{20 - 2} = \frac{360}{18} = 20V$$


$$\boxed{V_1 = 20V}$$

$$V_2 = \frac{\Delta V_2}{\Delta} = \frac{\begin{bmatrix} 5 & 60 \\ -1 & 60 \end{bmatrix}}{\begin{bmatrix} 5 & -2 \\ -1 & 4 \end{bmatrix}} = \frac{300 + 60}{20 - 2} = \frac{360}{18} = 20V$$

$$\boxed{V_2 = 20V}$$

ct through 15Ω is $\frac{V_1 - V_2}{15} = \frac{0}{15} = 0$, No current flow.

2)

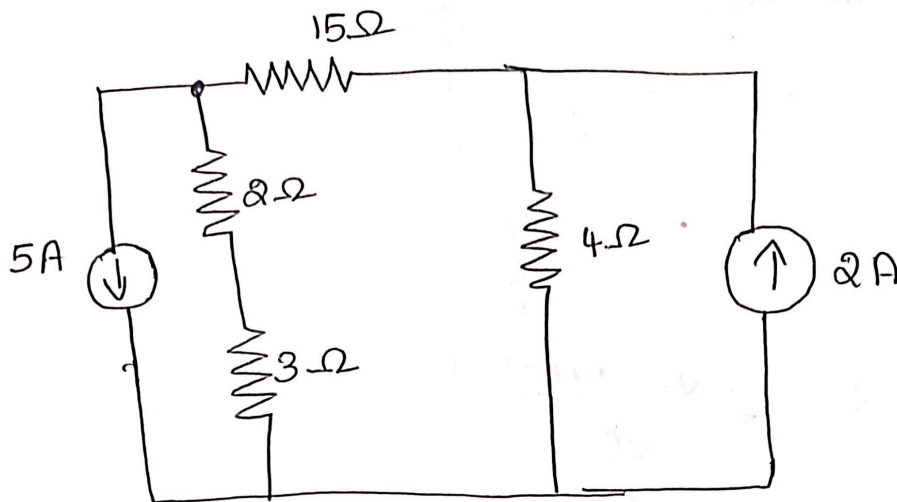Ans


$$V_1 = -\frac{145}{8} V$$

$$V_2 = \frac{5}{2} V$$

For the circuit shown determine V_1 and V_2 .

Soln

The circuit can be re-drawn as.

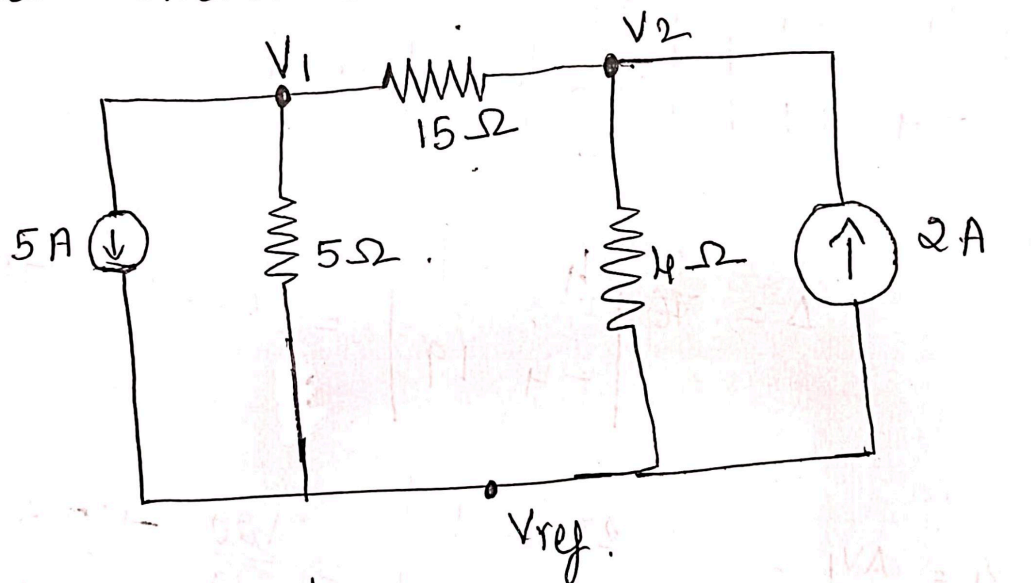

* Mark the nodes,

* Apply KCL to node 1,

$$5 + \frac{V_1}{5} + \frac{V_1 - V_2}{15} = 0$$

$$\frac{75 + 3V_1 + V_1 - V_2}{15} = 0 - 5$$

$$4V_1 - V_2 = -75 \quad \text{--- (1)}$$

(39) Apply KVL at N_2 .

$$Q = \frac{V_2}{4} + \frac{V_2 - V_1}{15}$$

$$= \frac{V_2}{4} + \frac{V_2}{15} - \frac{V_1}{15}$$

$$Q = \frac{15V_2 + 4V_2 - 4V_1}{60}$$

$$19V_2 - 4V_1 = 120 \quad \text{--- (1)}$$

$$-4V_1 + 19V_2 = 120 \quad \text{--- (2)}$$

$$\begin{bmatrix} 4 & -1 \\ -4 & 19 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -75 \\ 120 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 4 & -1 \\ -4 & 19 \end{vmatrix} = 76 - 4 = 72$$

$$V_1 = \frac{\Delta V_1}{\Delta} = \frac{\begin{vmatrix} -75 & -1 \\ 120 & 19 \end{vmatrix}}{72} = \frac{-1425 + 120}{72} = \frac{-1305}{72}$$


$V_1 = -18.125 \text{ V}$

$$V_Q = \frac{\Delta V_2}{\Delta}$$


$$= \frac{\begin{vmatrix} 4 & -75 \\ -4 & 120 \end{vmatrix}}{72} = \frac{480 - 300}{72} = \frac{180}{72}$$

$V_2 = 2.5 \text{ V}$

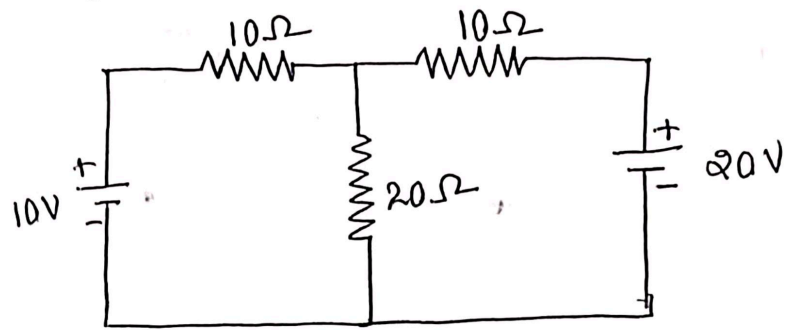- 4) using nodal analysis determine the current in the 20Ω resistor.



Convert vtg source to current source

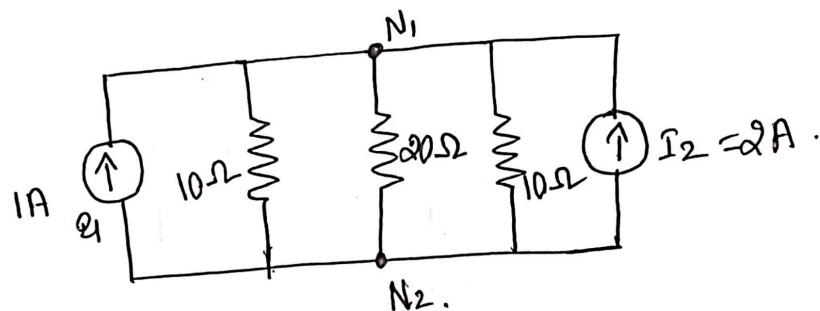

$$I_1 = V/R$$

$$= \frac{10V}{10\Omega} = 1A$$

$$I_2 = \frac{20V}{10\Omega} = 2A$$

Apply KVL to N_1

$$1 + 2 = \frac{V_1}{10} + \frac{V_1}{20} + \frac{V_1}{10}$$


$$3 = V_1 \left[\frac{1}{10} + \frac{1}{20} + \frac{1}{10} \right]$$

$$V_1 = \frac{3}{\frac{2+1+2}{20}}$$

$$V_1 = \frac{60}{8} = 12$$

$$I_{20\Omega} = \frac{12}{20} = 0.6A$$

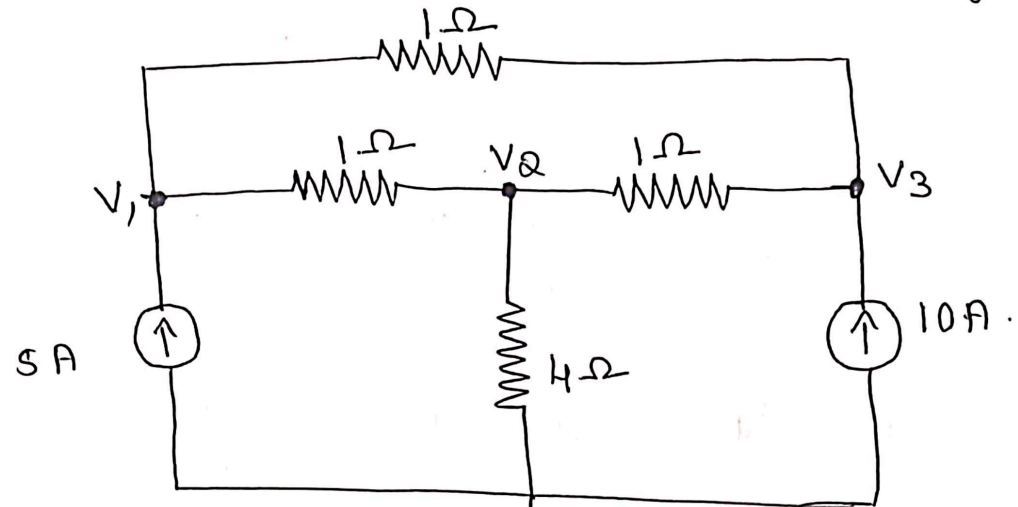- 5) Find V_1, V_2, V_3 by the nodal method for the given circuit.



KCL at N_1

$$5 = \frac{V_1 - V_2}{1} + \frac{V_1 - V_3}{1}$$

$$= V_1 - V_2 + V_1 - V_3 = 2V_1 - V_2 - V_3$$

$$2V_1 - V_2 - V_3 = 5 \quad \text{--- (1)}$$

KCL at N_2

$$\frac{V_2 - V_1}{1} + \frac{V_2}{4} + \frac{V_2 - V_3}{1}$$

$$0 = V_2 - V_1 + \frac{V_2}{4} + V_2 - V_3$$

$$= -V_1 + 2V_2 + \frac{V_2}{4} - V_3$$

$$= -V_1 + \frac{9}{4}V_2 - V_3 \quad \text{--- (2)}$$

KCL at N_3 .

$$10 = \frac{V_3 - V_1}{1} + \frac{V_3 - V_2}{1}$$

$$= V_3 - V_1 + V_3 - V_2 = -V_1 - V_2 + 2V_3 = 10 \quad \text{--- (3)}$$

(42)

$$\begin{bmatrix} 2 & -1 & -1 \\ -1 & 9/4 \\ & (2.25) & -1 \\ -1 & -1 & 2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 10 \end{bmatrix}$$

$$\Delta = 2 \begin{bmatrix} 4.5 & -1 \\ -2 & -1 \end{bmatrix} - (-1) \begin{bmatrix} -2 & -1 \end{bmatrix} + (-1) \begin{bmatrix} 1 & 2.25 \end{bmatrix}$$

$$= 7 - 3 - 3.25 \Rightarrow \boxed{\Delta = 0.75}$$

$$\Delta V_1 = \begin{bmatrix} 5 & -1 & -1 \\ 0 & 2.25 & -1 \\ 10 & -1 & 2 \end{bmatrix}$$

$$= 5 \begin{bmatrix} 4.5 & -1 \end{bmatrix} - (-1) (0 + 10) + (-1) (0 - 22.5)$$

$$= 17.5 + 10 + 22.5 = 50$$

$$V_1 = \frac{\Delta V_1}{\Delta} = \frac{50}{0.75} \Rightarrow \boxed{V_1 = 66.66 \text{ V}}$$

$$\Delta V_2 = \begin{bmatrix} 2 & 5 & -1 \\ -1 & 0 & -1 \\ -1 & 10 & 2 \end{bmatrix}$$

$$= 2 \begin{bmatrix} 10 \end{bmatrix} - 5 \begin{bmatrix} -2 & -1 \end{bmatrix} + (-1) (-10)$$

$$= 20 + 15 + 10 = 45 \Rightarrow V_2 = \frac{\Delta V_2}{\Delta} = \frac{45}{0.75} = 60$$

(43)

$$V_2 = 60$$

$$\Delta V_3 = \begin{bmatrix} 2 & -1 & 5 \\ -1 & 2.25 & 0 \\ -1 & -1 & 10 \end{bmatrix}$$


$$= 2[22.5] - (-1)(-10) + 5(1 + 2.25)$$

$$= 45 - 10 + 16.25$$


$$= 51.25$$

$$V_3 = \frac{\Delta V_3}{\Delta} = \frac{51.25}{0.75} = 68.33V.$$

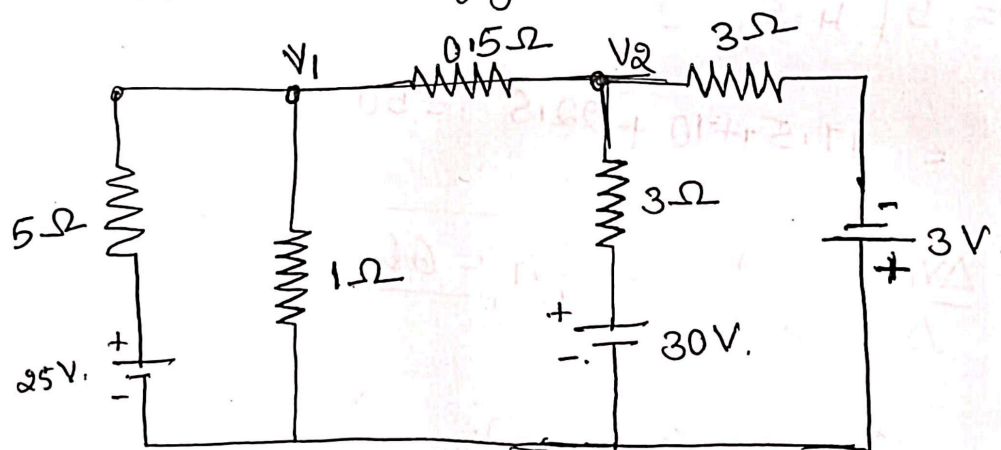
Find the voltage of the nodes 1 and 2 in the network shown in figure



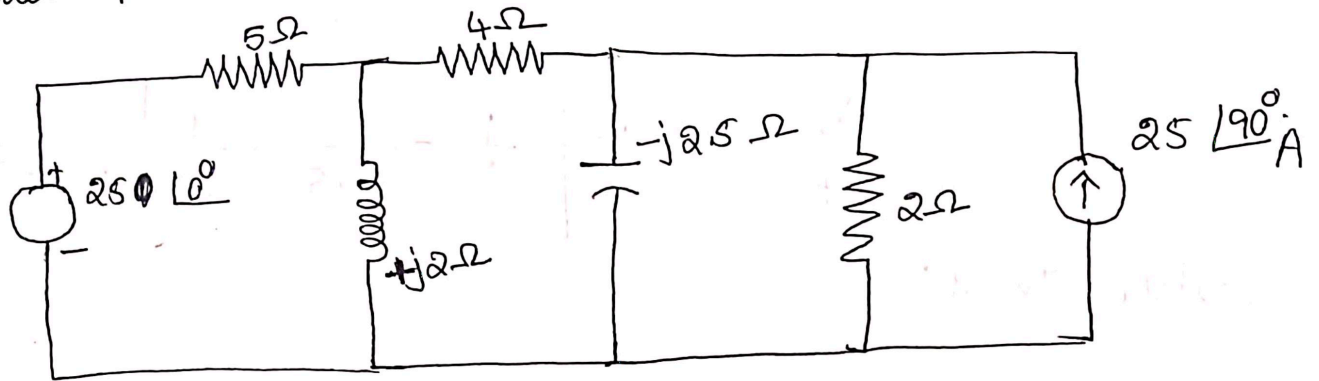using nodal analysis, find the current through 4Ω resistor in the circuit shown in figure. (44) (44)



1) Convert vtg source to ct source.

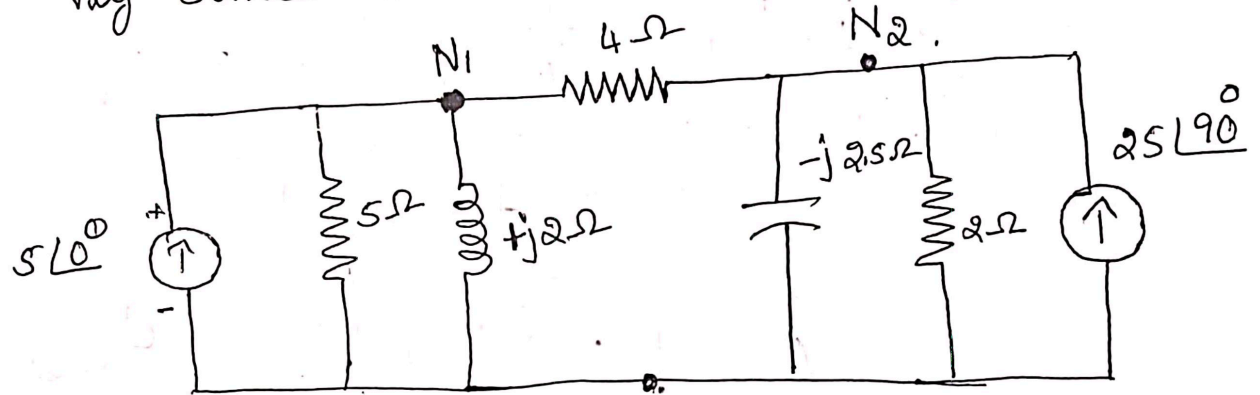

Apply KCL to node 1,

$$5 = \frac{V_1}{5} + \frac{V_1}{-j2} + \frac{V_1 - V_2}{4}$$

$$5 = \frac{V_1}{5} + \frac{V_1}{4} + \frac{V_1}{-2j} - \frac{V_2}{4}$$

$$5\angle 0^\circ = V_1 \left[\frac{1}{5} + \frac{1}{2j} + \frac{1}{4} \right] - \frac{1}{4} V_2 \quad \text{--- (1)}$$

Apply KCL to N2.

$$25\angle 90^\circ = \frac{V_2}{2} + \frac{V_2}{-j2.5} + \frac{V_2 - V_1}{4}$$

(48)

$$\frac{V_2}{2} - \frac{V_2}{j2.5} + \frac{V_2}{4} - \frac{V_1}{4} = 25 \angle 90^\circ$$

$$-\frac{V_1}{4} + V_2 \left[\frac{1}{2} - \frac{1}{j2.5} + \frac{1}{4} \right] = 25 \angle 90^\circ$$

matrix form:-

$$\begin{bmatrix} \frac{1}{5} + \frac{1}{j2} + \frac{1}{4} & -\frac{1}{4} \\ -\frac{1}{4} & \frac{1}{4} + \frac{1}{-j2.5} + \frac{1}{2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 5 \angle 0^\circ \\ 25 \angle 90^\circ \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 0.2 + 0.5j + 0.25 & -0.25 \\ -0.25 & 0.25 + 0.4j + 0.5 \end{bmatrix}$$

$$= \begin{bmatrix} 0.45 + 0.5j & -0.25 \\ -0.25 & 0.75 + 0.4j \end{bmatrix}$$

$$= 0.1375 + 0.555j - 0.0625$$

$$= (0.45 + 0.5j)(0.75 + 0.4j) - (0.25)^2$$

$$= 0.3375 + 0.18j + 0.375j + 0.2 - 0.0625$$

$$= 0.5375 - j0.195 - 0.0625 = 0.475 - j0.195$$

$$= \sqrt{x^2 + y^2} \angle \tan^{-1} \frac{0.195}{0.475}$$

$$\Delta = 0.513 \angle -22.3^\circ$$

$$\Delta_1 = \begin{vmatrix} 5 \angle 0^\circ & -0.25 \\ 25 \angle 90^\circ & 0.75 + j0.4j \end{vmatrix}$$

$$\sqrt{0.5625 + 0.14}$$

$$\sqrt{0.7225}$$

$$\text{mag} 0.85$$

$$= \begin{vmatrix} 5 \angle 0^\circ & 0.25 \angle 0^\circ \\ 25 \angle 90^\circ & 0.85 \angle 27.9^\circ \end{vmatrix}$$

$$= 4.25 \angle 27.9^\circ - 6.25 \angle 90^\circ$$

$$= 5(0.75 + j0.4j) + 0.25(25 \angle 90^\circ)$$

$$= 3.75 + j2 + 0.25(25j)$$

$$= 3.75 + j2 + j6.25$$

$$\Delta_1 = 3.75 + j8.25 = 9.06 \angle 65.5^\circ$$

$$\text{shift} = \text{Pol.}, \text{shift} =$$

$$\Delta_2 = \begin{vmatrix} 0.45 - j0.5 & 5 \angle 0^\circ \\ -0.25 & 25 \angle 90^\circ \end{vmatrix}$$

$$= 25 \angle 90^\circ (0.45 - j0.5) + 0.25 \times 5 \angle 0^\circ$$

$$= j25(0.45 - j0.5) + 1.25$$

$$= 11.25j + 12.5 + 1.25$$

$$= 13.75 + j11.25$$

$$\Delta_2 = 17.77 \angle 39.3^\circ$$

47

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{9.06 \angle 65.5^\circ}{0.513 \angle -22.3^\circ}$$

46

$$V_1 = 17.66 \angle 87.8^\circ \text{ volts} = 0.1677 + j17.6$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{17.77 \angle 39.3^\circ}{0.513 \angle -22.3^\circ} = 34.64 \angle 61.6^\circ \text{ volts}$$

$$= 16.47 + j30.47 \text{ V}$$

$$\text{voltage across } 4\Omega = V_2 - V_1$$

$$= 16.47 + j30.47 - 0.1677 - j17.6$$

$$= 15.793 + j12.87$$

$$= 20.37 \angle 39.17^\circ \text{ volts}$$

$$\text{current} = \frac{V}{R} = \frac{20.37 \angle 39.17^\circ}{4}$$


$$= 5.09 \angle 39.17^\circ \text{ A}$$

Time domain

Frequency domain

48


Resistor

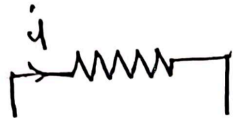

$$V = iR$$

$$V = IR$$


Inductor

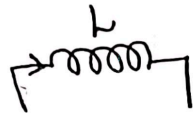

$$V = L \frac{di}{dt}$$

$$V = j\omega L I$$

Capacitor

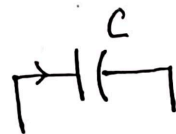

$$V = \frac{1}{C} \int i dt$$


$$V = \left(\frac{1}{j\omega C} \right) I$$

Impedance

$$Z_R = R, \quad Z_L = j\omega L, \quad Z_C = \frac{1}{j\omega C}$$

Find the equivalent impedance of the network shown.

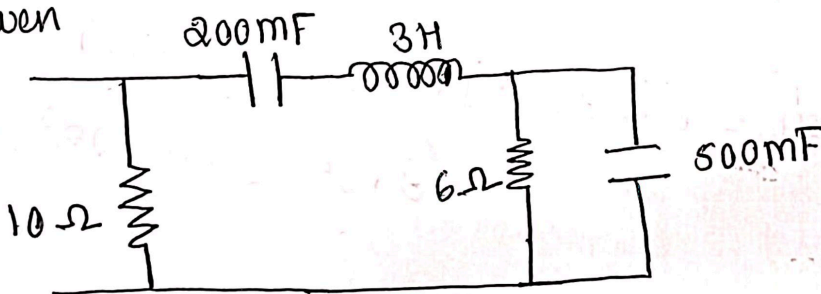for a given
operating
frequency of
5 rad/s




Soln

$$Z_R = 10 \Omega$$

$$Z_L = j\omega L = j \times 5 \times 3 = j15 \Omega$$

$$Z_R = 6 \Omega$$
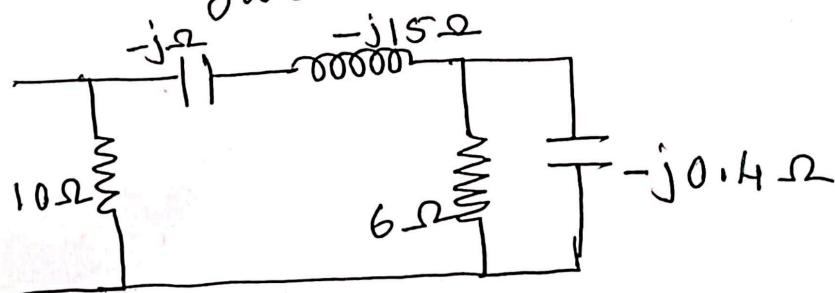
$$Z_C = \frac{1}{j\omega C} = \frac{-j}{\omega C} = \frac{-j}{5 \times 500 \times 10^{-3}} = -j0.4 \Omega$$



(19)

$$Z_{eq} = \frac{6(-j0.4)}{6-j0.4} =$$

$$Z_{eq} = 0.02655 - j0.3984 \Omega$$

series imp $Z_{eq} = Z_L + Z_C$

Parallel imp $Z_{eq} = \frac{Z_L Z_C}{Z_L + Z_C}$

$$Z_{eq} = -j\Omega \text{ and } j15 \Omega$$

$$Z_{eq} = 0.02655 - j0.3982 - j + j15 = 0.02655 + j13.6 \Omega$$

This Z_{eq} is now in parallel with 10Ω .

$$Z_{eq} = \frac{10(0.02655 + j13.6)}{10 + 0.02655 + j13.6}$$

$$= 6.488 + j4.763 \Omega$$

$$Z_{eq} = 6.488 + j4.763 \Omega \quad (or)$$

$$8.05 \angle 36.28^\circ \Omega$$

Admittance

$$Y = G + jB = \frac{1}{Z} = \frac{1}{R + jX} \quad \left[\because Y = \frac{1}{Z} \right]$$

mesh equation derivation.