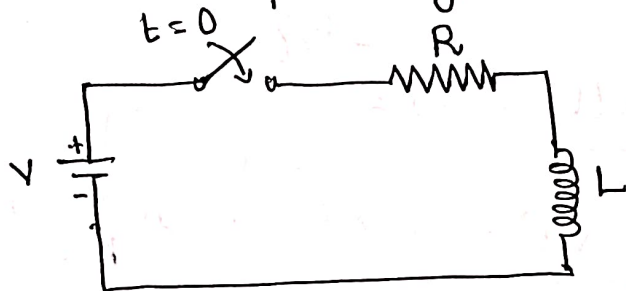


(14)

Forced Response of RL series circuit.

The circuit shows an RL circuit connected to a DC source of voltage V through a switch S . Assume switch is closed at time $t=0$ also assume the initial current flowing in the circuit is zero.



Apply KVL to ckt

$$V = V_R + V_L$$

$$V = iR + L \cdot \frac{di}{dt}$$

Taking Laplace transform on both side

$$\frac{V}{s} = R I(s) + L [s I(s) - i(0)] \quad \left| \quad L[1] = \frac{1}{s} \right.$$

where $i(0)$ is the initial current
let it be 0.

$$L\left(\frac{di}{dt}\right) = s I(s) - i(0)$$

$$\therefore \frac{V}{s} = R I(s) + L s I(s)$$

$$\frac{V}{s} = I(s) (R + Ls)$$

$$I(s) = \frac{V}{s(R + Ls)}$$

By using partial Fraction method

(5)

$$I(s) = \frac{V}{s(R+SL)} = \frac{A}{s} + \frac{B}{R+SL} \quad \text{--- (1)}$$

$$V = A(R+SL) + BS$$

At $s=0$

$$V = AR$$

$$\boxed{A = \frac{V}{R}}$$

At $s = -\frac{R}{L}$

$$V = A\left(R - \frac{R}{L} \times L\right) + B\left(-\frac{R}{L}\right)$$

$$V = A(R-R) - B \cdot \frac{R}{L}$$

$$\therefore \boxed{B = -V\left(\frac{L}{R}\right)}$$

substituting the value of A and B in (1)

$$I(s) = \frac{V/R}{s} - \frac{V \cdot L/R}{R+SL}$$

$$= \frac{V}{Rs} - \frac{VL}{R(R+SL)}$$

$$= \frac{V}{R} \left(\frac{1}{s}\right) - \frac{V}{R} \left[\frac{1}{\frac{R}{L} + \frac{SL}{L}}\right]$$

$$= \frac{V}{R} \left(\frac{1}{s}\right) - \frac{V}{R} \left(\frac{1}{s + R/L}\right)$$

Taking inverse Laplace transform on both sides

(16)


$$i(t) = \frac{V}{R} \cdot 1 - \frac{V}{R} e^{-(R/L)t}$$

$$i(t) = \frac{V}{R} \left[1 - e^{-(R/L)t} \right]$$

$$i(t) = \frac{V}{R} \left[1 - e^{-t/\tau} \right]$$

where time constant
 $\tau = L/R$

The above equation can be drawn as.

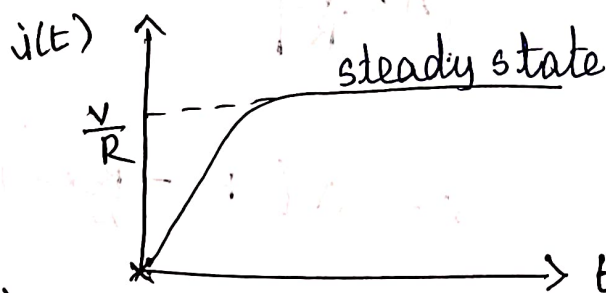

When $t=0$ $i(0)=0$

Final value at can be found by substituting $t=\infty$

$$i(t) \Big|_{t=\infty} = \frac{V}{R} \left[1 - e^{-\infty} \right]$$

$$= \frac{V}{R} \quad [\because e^{-\infty} = 0]$$

Note, At $t = \frac{L}{R}$

$$i(t) = \frac{V}{R} \left[1 - e^{-\frac{L}{R} \cdot \frac{R}{L}} \right]$$

$$= \frac{V}{R} \left[1 - e^{-1} \right]$$

$$= \frac{V}{R} \left[1 - 0.368 \right]$$

$$i(t) = 0.632 \frac{V}{R}$$

$i(t)$ is 63.2% of steady state (or) final value

voltage across inductor V_L

(17)

$$V_L = L \cdot \frac{di}{dt}$$

$$= L \cdot \frac{d}{dt} \frac{V}{R} (1 - e^{-t/\tau})$$

$$= \frac{VL}{R} - e^{-t/\tau} \cdot \left(-\frac{1}{\tau}\right)$$

$$= \frac{VL}{R} \left(-\frac{R}{L}\right) (-e^{-t/\tau})$$

$$V_L = + V e^{-t/\tau}$$

$$V_R = iR$$

$$= \frac{V}{R} \times R [1 - e^{-t/\tau}]$$

$$V_R = V [1 - e^{-t/\tau}]$$

Power across resistor is,

$$P_R = I^2 R$$

$$= \frac{V^2}{R} (1 - e^{-t/\tau})^2$$

$$P_R = \frac{V^2}{R} (1 - e^{-t/\tau})^2$$

Power across inductor,

$$P_L = I V_L$$

$$= \frac{V}{R} (1 - e^{-t/\tau}) \cdot V e^{-t/\tau}$$

$$P_L = \frac{V^2}{R} (e^{-t/\tau} - e^{-2t/\tau})$$

18

$$E_L = \int_0^{\infty} P dt = \frac{V^2}{R} \int_0^{\infty} e^{-t/\tau} - e^{-2t/\tau} dt$$

$$= \frac{V^2}{R} \left[\frac{e^{-t/\tau}}{-1/\tau} - \frac{e^{-2t/\tau}}{-2/\tau} \right]_0^{\infty}$$

$$= \frac{V^2}{R} \left[0 - \left[-\tau + \frac{\tau}{2} \right] \right]$$

$$= \frac{V^2}{R} \left[- \left[-\frac{L}{R} + \frac{L}{2R} \right] \right]$$

$$= \frac{V^2}{R} \left[- \frac{-2L+L}{2R} \right]$$

Energy

$$E_L = \frac{V^2}{R} \left(\frac{L}{2R} \right) = \left(\frac{V}{R} \right)^2 \cdot \frac{L}{2}$$

$$E_R = \int_0^{\infty} \frac{V^2}{R} (1 - e^{-t/\tau})^2 dt = \infty$$


$$\eta = \frac{E_L}{E_L + E_R}$$

$$\boxed{\eta = 0}$$

Forced Response of RC circuit

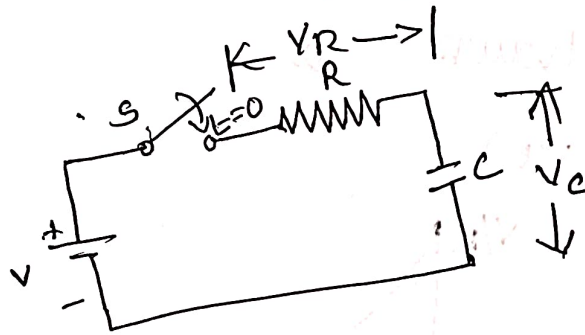(19)

An RC circuit is connected to a DC supply voltage of 'V' volts through a switch. Assume the switch is closed at $t=0$. Also assume initial charge and voltage in the capacitor is zero.



Applying KVL to above circuit,

$$V = V_R + V_C$$

$$V = iR + \frac{1}{C} \int i dt$$

Taking Laplace transform on both sides.

$$\frac{V(s)}{s} = R \bar{i}(s) + \frac{1}{C} \cdot \frac{\bar{i}(s)}{s}$$

$$= \bar{i}(s) \left[R + \frac{1}{Cs} \right]$$

$$\bar{i}(s) = \frac{V}{s \left(R + \frac{1}{Cs} \right)}$$

$$= \frac{V}{\left[Rs + \frac{1}{C} \right]} = \frac{V}{\left[Rs + \frac{R}{RC} \right]}$$

$$\bar{i}(s) = \frac{V}{R \left[s + \frac{1}{RC} \right]}$$

20


Taking inverse Laplace transform.

$$i(t) = \frac{V}{R} e^{-t/RC}$$

At $t=0$ $i(t) = V/R$.

At $t=\infty$ $i(t) = 0$

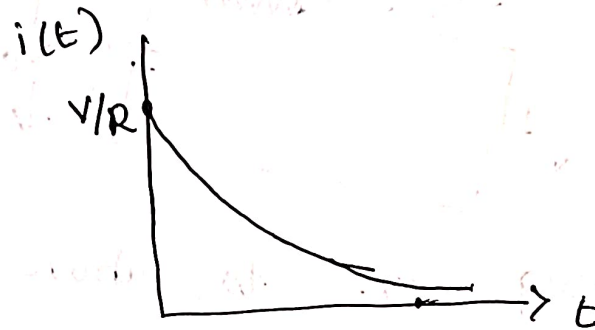The transient response of RC circuit can be drawn as



voltage across resistor,

$$V_R = iR$$

$$= \frac{V}{R} \cdot e^{-t/RC}$$

$$V_R = V e^{-t/RC}$$

voltage across capacitor,

$$V_C = \frac{1}{C} \int_0^t i \, dt$$

$$= \frac{1}{C} \int_0^t \frac{V}{R} e^{-t/RC} \, dt$$

$$= \frac{V}{RC} \left[\frac{e^{-t/RC}}{-1/RC} \right]_0^t$$

(21)

$$= \frac{-V \times RC}{RC} \begin{bmatrix} e^{-t/RC} & 0 \\ e & -e \end{bmatrix}$$

$$= V \left[-e^{-t/RC} + 1 \right]$$

$$= V \left[1 - e^{-t/RC} \right]$$

$$\boxed{V_C = V \left[1 - e^{-t/\tau} \right]}$$

Time constant

$$\tau = RC$$

Power

$$P_C = VI = V \left[1 - e^{-t/\tau} \right] \frac{V}{R} e^{-t/RC}$$

$$= \frac{V^2}{R} \left[e^{-t/\tau} - e^{-2t/\tau} \right] \quad [\because RC = \tau]$$

$$P_R = I^2 R$$

$$= \frac{V^2}{R^2} \left(e^{-t/\tau} \right)^2 R$$

$$\boxed{P_R = \frac{V^2}{R} e^{-2t/\tau}}$$

Energy

$$E_R = \int_0^{\infty} P_R dt = \frac{V^2}{R} \int_0^{\infty} e^{-2t/\tau} dt = \frac{V^2}{R} \left[\frac{e^{-2t/\tau}}{-2/\tau} \right]_0^{\infty}$$

$$= \frac{-V^2 \tau}{2R} \left[e^{-\infty} - e^0 \right]$$

$$= \frac{V^2 \tau}{2R} (-0 + 1) = \frac{V^2 RC}{2R}$$

22

$$E_R = \frac{V^2 C}{2}$$

$$E_C = \int_0^{\infty} P_C dt$$

$$= \frac{V^2}{R} \int_0^{\infty} (e^{-t/\tau} - e^{-2t/\tau}) dt$$

$$= \frac{V^2}{R} \left[\frac{e^{-t/\tau}}{-1/\tau} - \frac{e^{-2t/\tau}}{-2/\tau} \right]_0^{\infty}$$

$$= \frac{V^2}{R} \left[0 - \left(\frac{1}{-1/\tau} - \frac{1}{-2/\tau} \right) \right]$$

$$= \frac{V^2}{R} \left[\tau - \frac{\tau}{2} \right] = \frac{V^2}{R} \frac{\tau}{2} = \frac{V^2 RC}{2R}$$

$$E_C = \frac{V^2 C}{2}$$

Efficiency

$$\eta = \frac{E_C}{E_C + E_R}$$
$$= \frac{V^2 C / 2}{V^2 C} = 1/2$$

$$\eta = 50\%$$