

Superposition theorem.

Superposition theorem allow us to analyze a circuit with multiple sources by considering the effect of each source separately.


steps:- Find the number of independent sources

2:- Consider one source at a time, deactivate other sources. Find current & voltage across each element.

3. Repeat this for all the sources.


4. Add the current & voltages.

1)

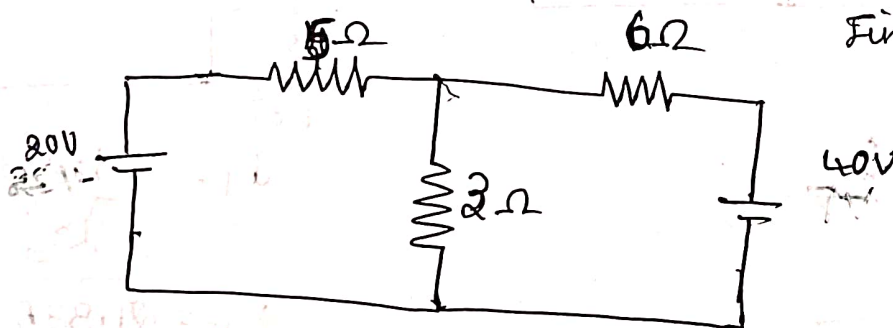

Find i_2 through 3Ω resistor.

Let 20V is active

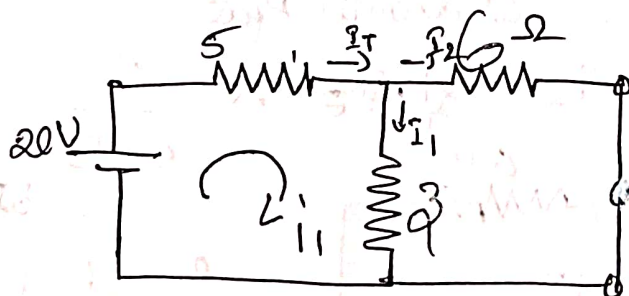

$$2 \times 6 =$$

$$6i_1 - 12i_2 = 0 \quad \text{--- (3)}$$

$$-10i_2 = -28$$

$$i_2 = 2.8 \text{ A}$$

$$1 + 3$$

$$28 - 4i_1 + 2(i_1 - i_2) = 0$$

$$28 - 6i_1 + 2i_2 = 0$$


$$-6i_1 + 2i_2 = -28 \quad \text{--- (1)}$$

$$-2(i_2 - i_1) - i_1 = 0$$

$$-2i_2 + i_1 = 0$$


$$i_1 - 2i_2 = 0 \quad \text{--- (2)}$$

43

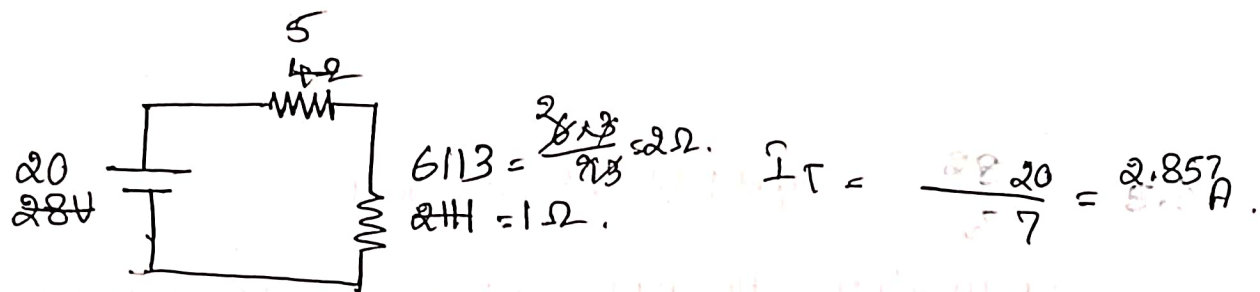

$$6 \parallel 3 = \frac{6 \times 3}{6 + 3} = 2\Omega$$

$$I_T = \frac{20}{5 + 2} = 2.857 A$$

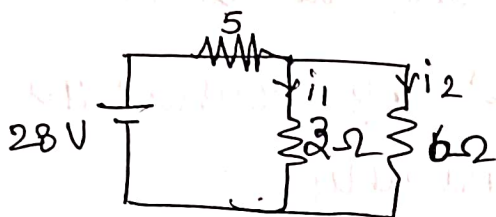



$$i_2 = \frac{5.06}{2} \times \frac{2}{2+1} = 3.73 A$$

$$i_1 = 2.85 \times \frac{6}{2+6} = 1.86 A$$

$$= 2.85 \times \frac{6}{8}$$

2) To find i_2 .

$$I_1 = 1.904 A$$

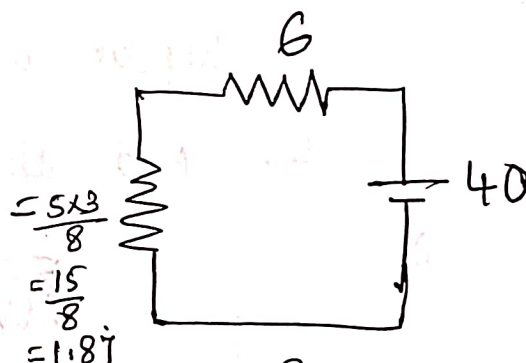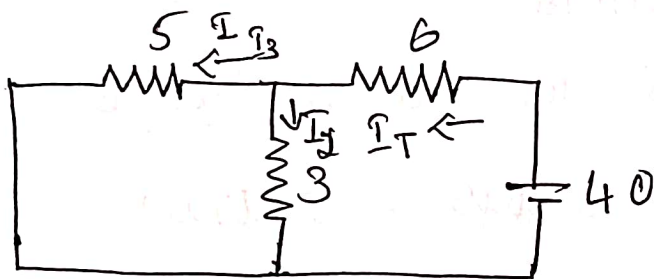


$$= \frac{5 \times 3}{8}$$

$$= \frac{15}{8}$$

$$= 1.87$$

$$I_T = \frac{40}{1.87 + 6}$$


$$I_T = 5.08 A$$

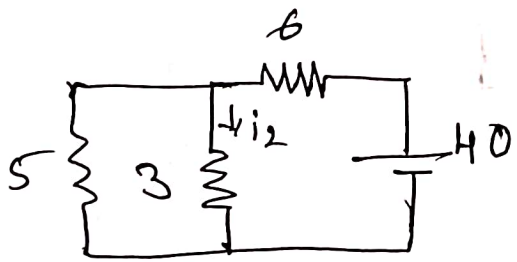

current divider rule

$$i_2 = 5.08 \times \frac{5}{5+3} = 3.17 A$$


3)

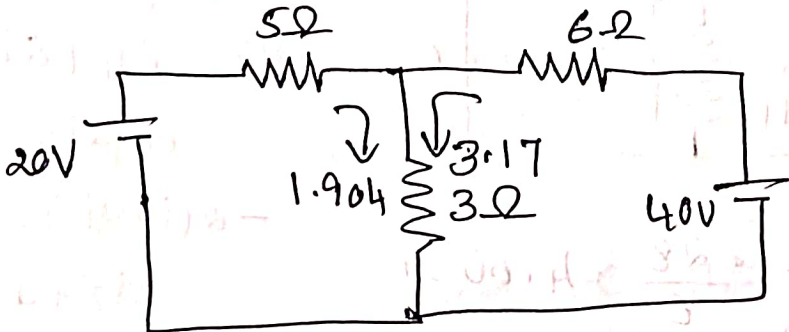


$$I_T = 1.904 + 3.17 = 5.074 A$$

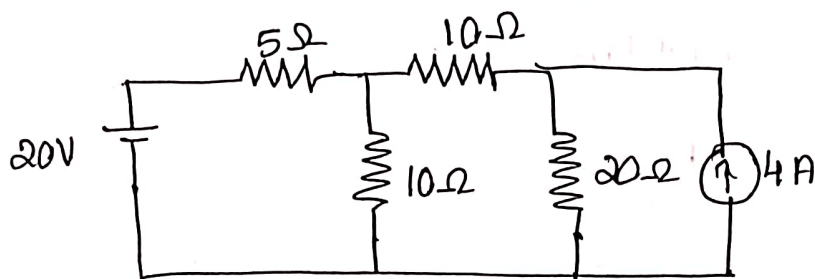(44)

Find the current flowing through 20Ω resistor.



Step 1:- deactivate 4A.

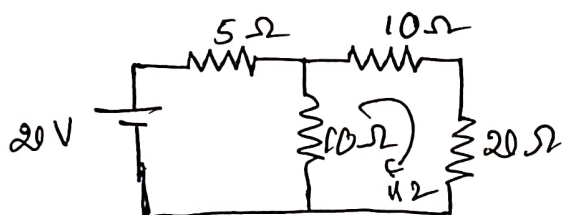

$$20 - 5i_1 - 10(i_1 - i_2) = 0$$

$$20 - 5i_1 - 10i_1 + 10i_2 = 0$$

$$20 - 15i_1 + 10i_2 = 0$$

$$-15i_1 + 10i_2 = -20 \quad (1)$$

$$-10(i_2 - i_1) - 10i_2 - 20i_2 = 0$$

$$-10i_2 + 10i_1 - 10i_2 - 20i_2 = 0$$

$$10i_1 - 40i_2 = 0 \quad (2)$$

$$(1) \times 4 = -60i_1 + 40i_2 = -80 \quad (3)$$


$$(2) + (3) = 50i_1 = -80 \Rightarrow i_1 = -1.6$$

$$(10)(-1.6) - 40i_2 = 0$$


$$-16 = 40i_2$$

$$i_2 = -0.4A$$

ct through 20Ω is $0.4A$.

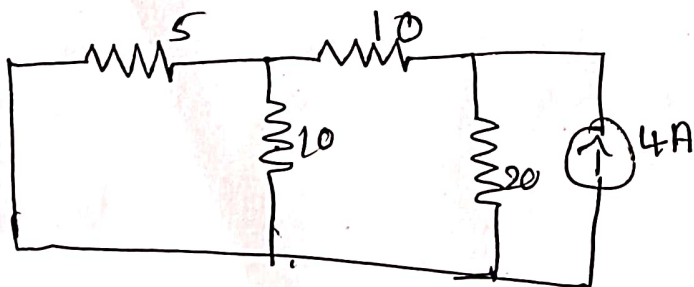
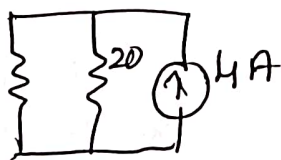
$$\begin{aligned} & \frac{10 \times 5}{15} + 10 \\ &= \frac{50}{15} + 10 \\ &= 13.33 \end{aligned}$$



$$I_{20\Omega} = 4 \times \frac{13.33}{13.3 + 20} = 1.6A$$


Q3

Total ct flowing through 2Ω is

$$0.4 + 1.6$$

$$I_{2\Omega} = 2A$$

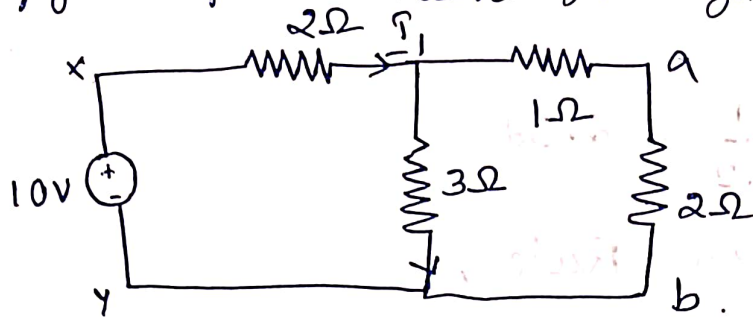46) verify Reciprocity Theorem for the gndt Reciprocity Theorem



$$R_{eq} = (2 \parallel 1) = \frac{2 \times 1}{2 + 1} = \frac{2}{3}$$

$$= (2 + 1) \parallel 3 = \frac{3 \times 3}{3 + 3} = \frac{9}{6} = \frac{3}{2}$$

$$= \frac{3}{2} + 2 = \frac{7}{2} = 3.5 \Omega$$


$$I_T = \frac{V}{R_{eq}} = \frac{10}{3.5}$$

$$I_T = 2.86 \text{ A}$$

$$I_2 = I_T \times \frac{3}{(2+1)+3}$$

$$= I_T \times \frac{3}{6} = 2.85 \times \frac{1}{2}$$

$$I_2 = 1.43 \text{ A}$$

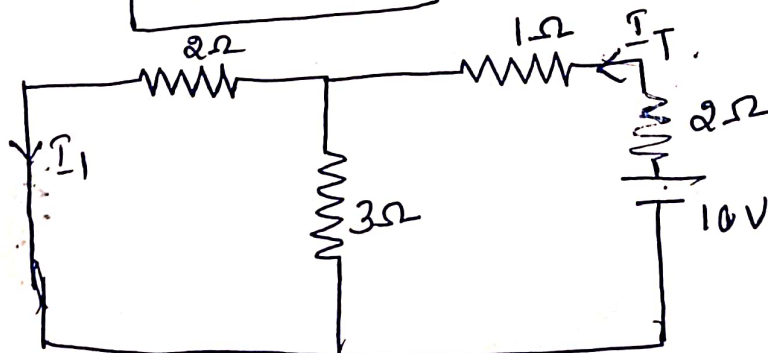

$$R_{eq} = [(2 \parallel 3) + 1] + 2 = 4.2 \Omega$$

(47)

$$I_T = \frac{10}{4.2} = 2.38$$

By ct. division Rule,

$$I_1 = I_T \times \frac{3}{5} \\ = 2.38 \times 0.6$$

$$I_1 = 1.43 \text{ A} \quad \text{--- (2)}$$

$\therefore I_2 = I_1$ Hence Reciprocity theorem is proved.

Reciprocity Theorem: In a linear bi-lateral network with a single voltage source, the current through any branch of the network, due to the voltage source will be the same if the voltage source is moved to that branch and the current is measured at the original location of the source.

