

Lumped parameters networks

The network that has simple elements and a set of connecting leads. it is called a lumped parameter network.

Distributed parameters n/w

n/w that has infinite number of small elements.

Node:- A point at which two or more elements have a common connection

Path:- If no node was encountered once, then the set of nodes and elements that we have passed through is defined as a path.

loop:-

~~node~~:- If the node at which we started is the same as the node on which we ended then the path is called a ~~node~~ loop.

Branches : Branches are connection between nodes.


Network :-

interconnection of two (or) more simple circuit elements.


Circuit:- If the NW contains atleast one closed path it is called a circuit.

Series and parallel connected sources.

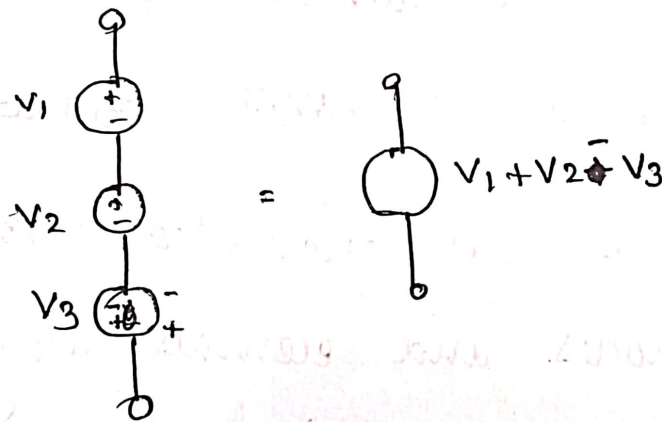- ① series connected voltage source can be replaced by a single source.



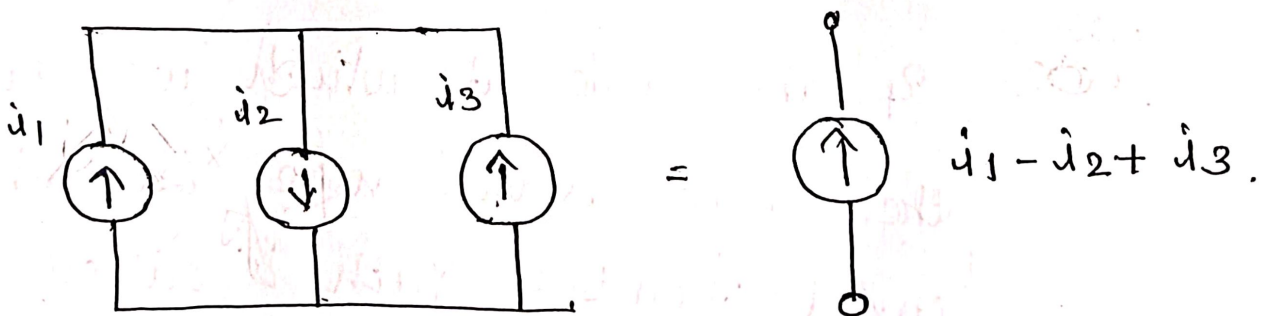
* If voltage sources are in parallel only same voltage will be there.



Practically current sources are not allowed to be connected in series.


Series and parallel connected sources.

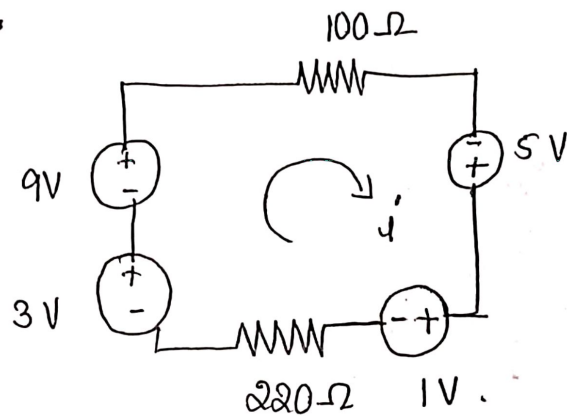- Q1. Determine the current 'i' in the circuit by just combining the sources into a single equivalent voltage source.



soln: series connected voltage sources can be combined into a single source.

$$3V + 9V + 5V - 1V = 16V$$

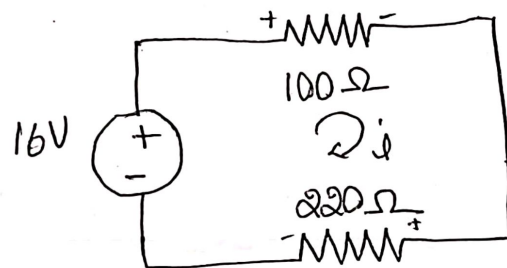

KVL


$$16V + 320i = 0$$

$$320i = -16$$

$$i = \frac{-16}{320}$$

$$= -0.05$$

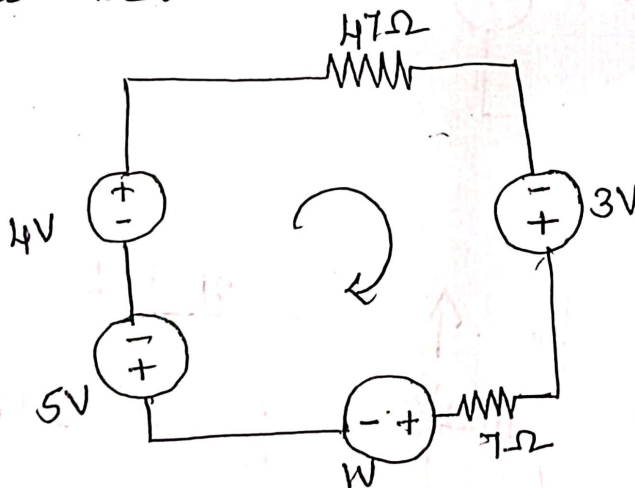- Q2. Determine the current 'i' in the ckt below.



soln

$$-5V + 4V + 3V - 1V = 1V$$

$$54i + 1V = 0$$


$$i = \frac{-1}{54}$$

$$= -0.0185A$$

- Q3. Determine the voltage in the circuit by just combining the source into a single equivalent current source.


(27)

21)

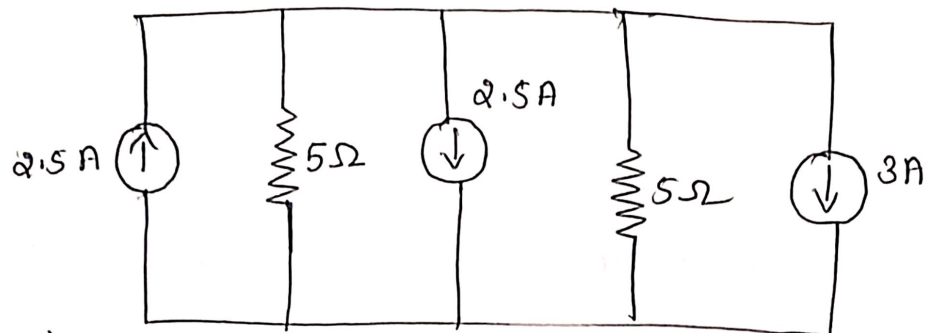

Combine
the source

$$-2.5 + 2.5 + 3 = 3A.$$

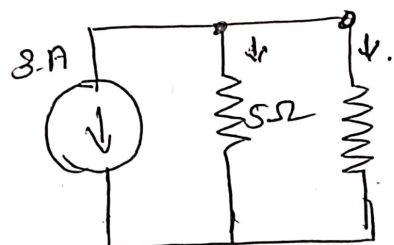

$$R = \frac{25}{10} = \frac{R_1 R_2}{R_1 + R_2}$$


Apply KCL

$$-i = \frac{V}{R}$$


$$\frac{V}{5} + \frac{V}{5} = 3$$

$$\frac{2V}{5} = 3 \Rightarrow V = \frac{15}{2} = 7.5V.$$

24)

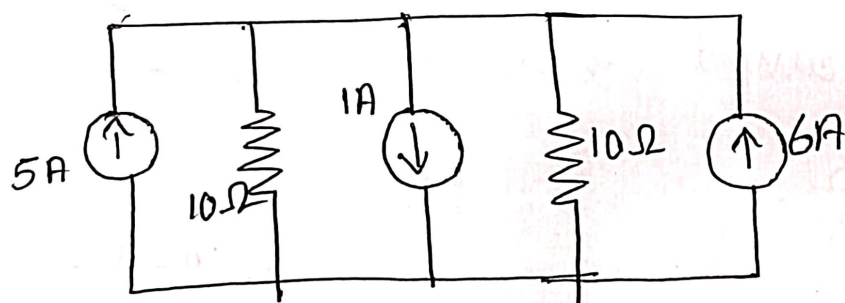

$$5 + 6 - 1 = 10A$$

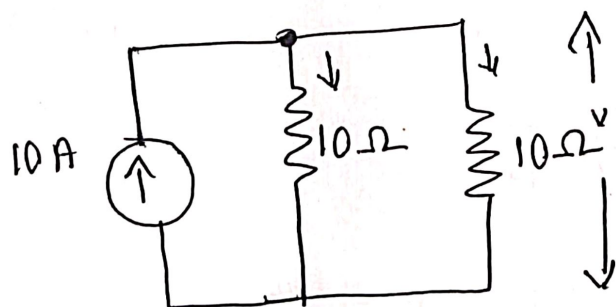

Apply KCL

$$\frac{V}{10} + \frac{V}{10} = 10$$

$$2V = 100$$


$$V = 50V$$

~~Q1~~

Resistors in series and parallel.

28

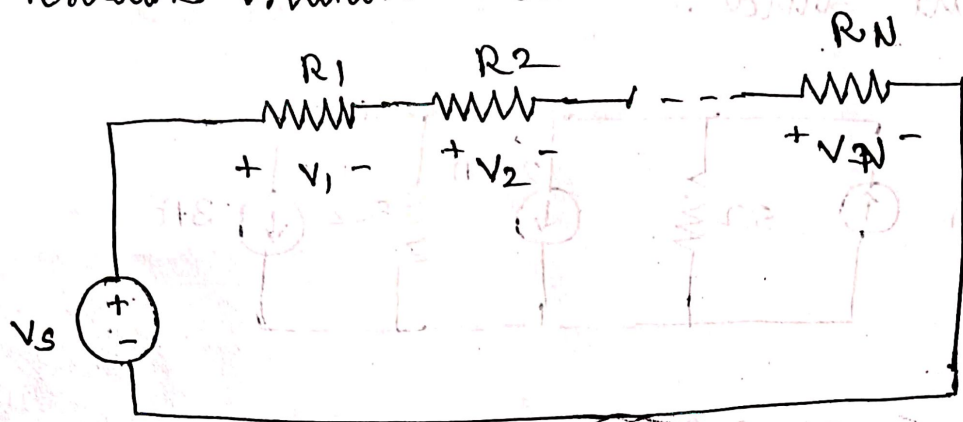Consider the series combination of N -resistors shown below.



We want to replace the N -resistors with a single equivalent resistor R_{eq} .

Apply KVL,

$$V_s = V_1 + V_2 + V_3 + \dots + V_N$$


$$V_s = iR_1 + iR_2 + iR_3 + \dots + iR_N$$

$$V_s = i(R_1 + R_2 + R_3 + \dots + R_N)$$

$$V_s = iR_{eq}$$

where $R_{eq} = R_1 + R_2 + R_3 + \dots + R_N$

For parallel resistors as

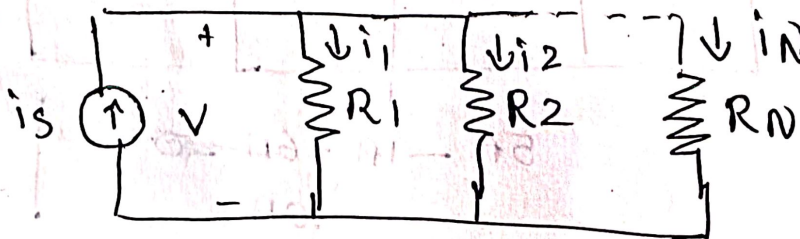

Incoming i_b = outgoing current.

$$i_b = i_1 + i_2 + \dots + i_N.$$

$$i_b = \frac{V}{R_1} + \frac{V}{R_2} + \dots + \frac{V}{R_N}$$

$$= V \left[\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} \right]$$

$$\therefore \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}.$$

18/7 present not enrolled
34, 35, 37, 38, 42, 55


19/7

47 not enrolled

(30)

25 Resistors in series and parallel.

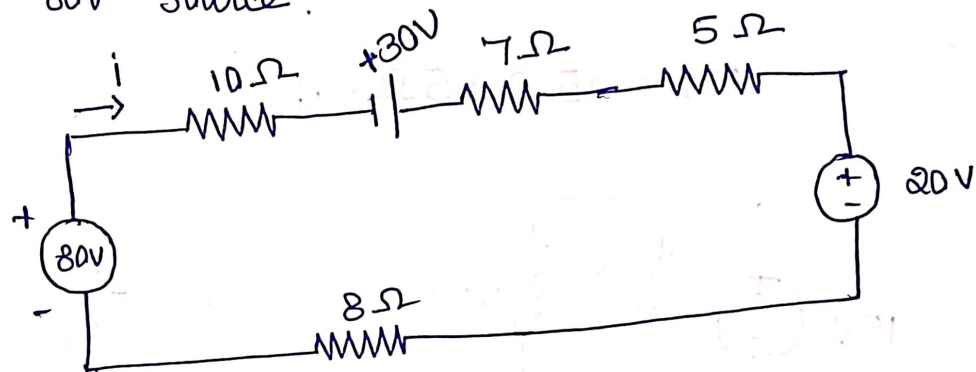25) use resistance and source combination to determine the current 'i' in fig below & the power delivered by the 80V source.




Soln

combine voltage source.

$$+80 + 30V - 20V = 90V$$

combine resistors

$$10 + 7 + 5 + 8 = 30\Omega$$

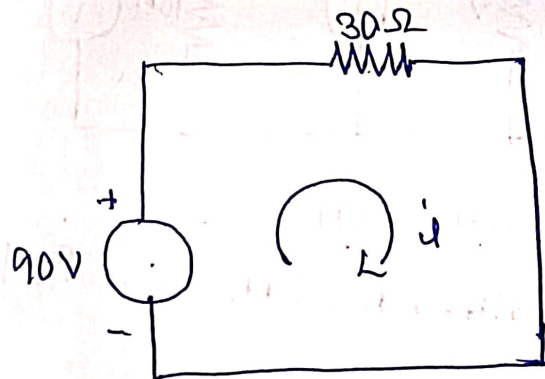

$$i = \frac{V}{R}$$
$$= \frac{90}{30}$$


$$i = 3A$$

$$\text{Power} = VI$$

$$= 80 \times 3$$

$$= 240 \text{ watts}$$


31)
26)

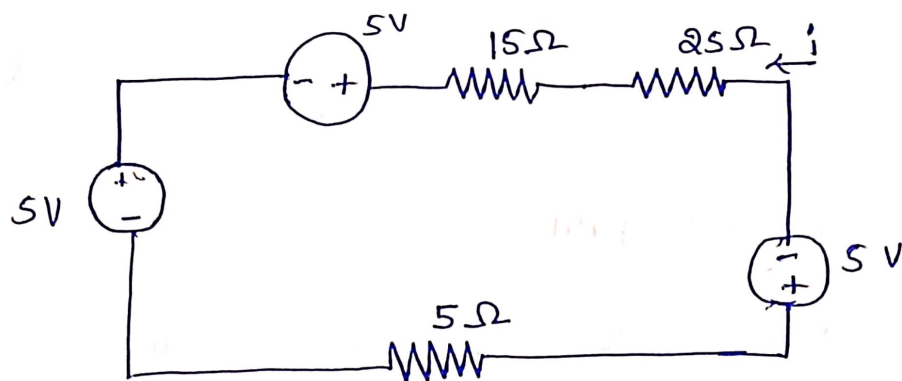

vtg


$$5V + 5V + 5V = 15V.$$
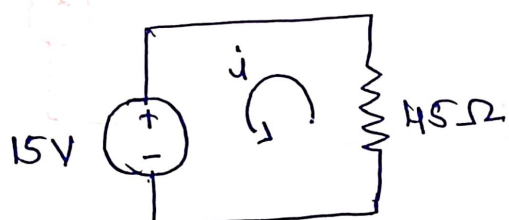
$$15\Omega + 25\Omega + 5\Omega = 45\Omega.$$



$$i = \frac{-V}{R} = \frac{-15}{45} = -0.333A$$

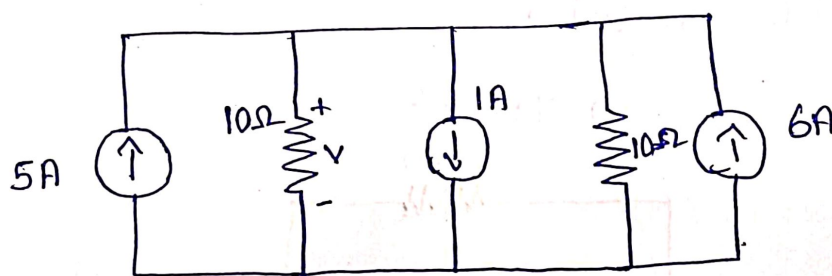27) Determine v in the circuit by combining the 3 current sources and two 10Ω resistors.




$$5A + 6A = 11A$$

$$11A - 1A = 10A$$

$$R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$
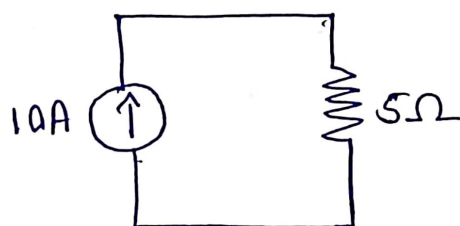
$$= \frac{10\Omega \cdot 10\Omega}{10\Omega + 10\Omega} = 5\Omega$$




$$V = IR$$

$$= 10 \times 5$$

$$\boxed{V = 50V}$$


32

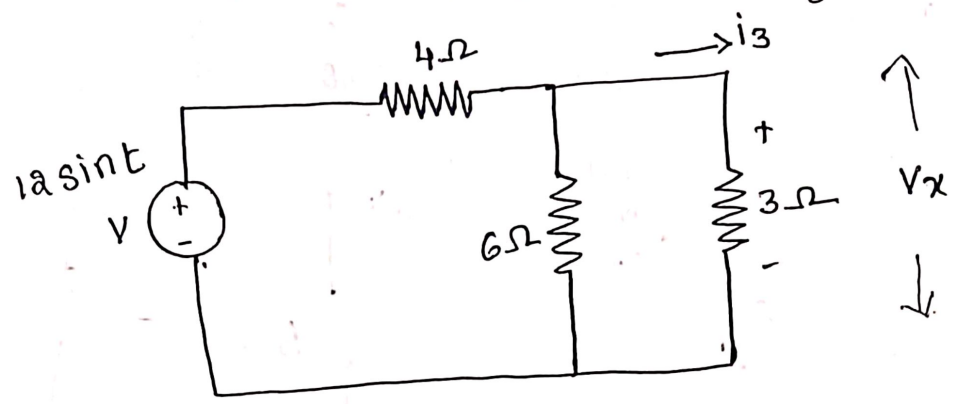28) Determine V_x in the circuit using voltage division rule.



soln
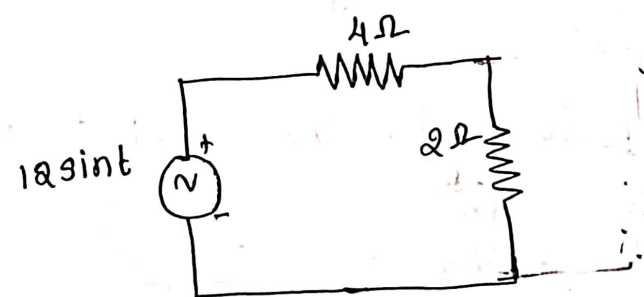
$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2} = \frac{6 \times 3}{6 + 3} = \frac{18}{9} = 2$$



By voltage divider rule,


$$V_x = V \cdot \frac{2}{4 + 2}$$

$$= 12 \sin t \times \frac{2}{6}$$

$$= 4 \sin t$$


$$\boxed{V_x = 4 \sin t}$$

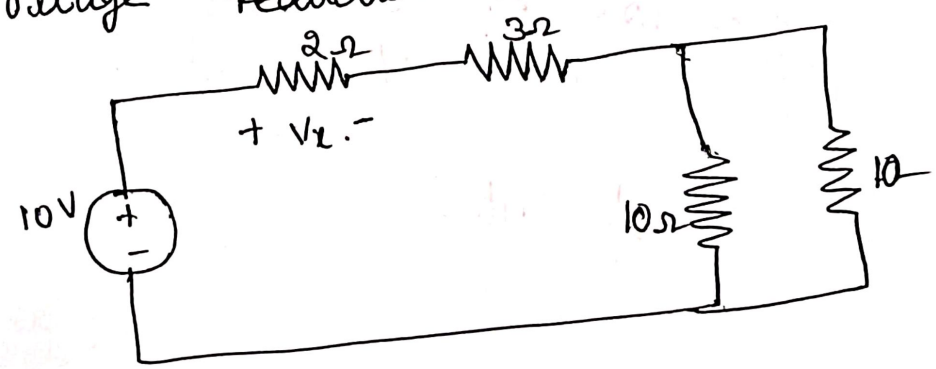29) use voltage division reduction to determine V_x .



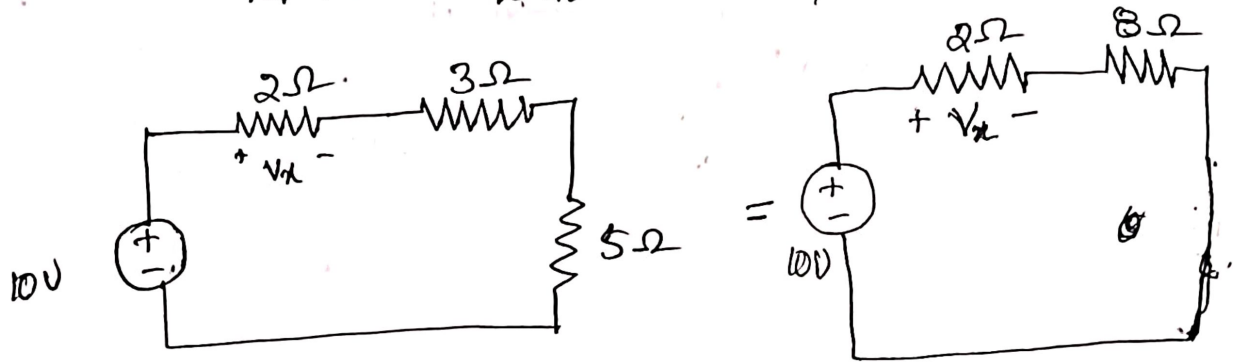(33)


$$R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{10 \times 10}{10 + 10} = \frac{100}{20} = 5 \Omega.$$



By voltage divider Rule

$$V_x = V \cdot \frac{2}{2+8} = 10 \times \frac{2}{10} = 2V.$$

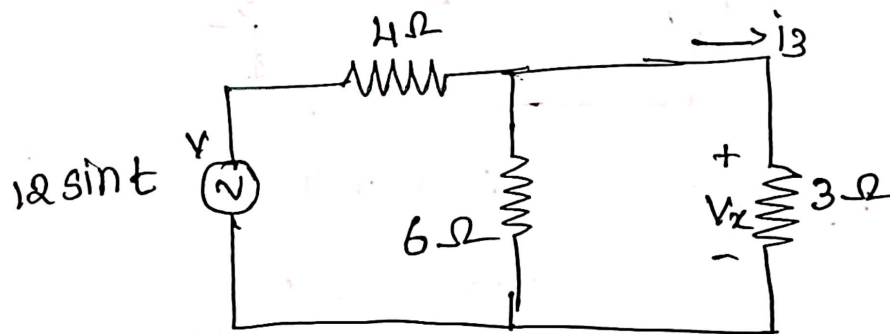
30) write an expression for the current through 3Ω resistor



$$R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{6 \times 3}{6+3} = 2$$

$$i_3 = i \times \frac{6}{6+3} = \frac{4}{6} 12 \sin t \cdot \frac{6}{9}$$

$$= \frac{4}{3} \sin t.$$

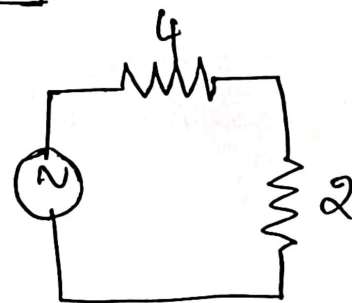

$$i = \frac{V}{R} = \frac{12 \sin t}{6}$$