

At loop 2: $6000(I_1'' - I_3'') + 12000I_1'' = 0$

$$18000I_1'' - 6000I_3'' = 0$$

$$18000I_1'' - 6000(6\text{mA}) = 0$$

$$\therefore I_1'' = \frac{36}{18000} = 2\text{mA}$$

Using Superposition theorem, Current through $12\text{k}\Omega$ is

$$I_1 = I_1' + I_1'' = 0.5\text{mA} + 2\text{mA}$$


$$I_1 = 2.5\text{mA}$$

Thévenin's Theorem

(a NW that behaves the same in both directions of current flow)

So the I - V relation is unchanged even if direction of I is changed.

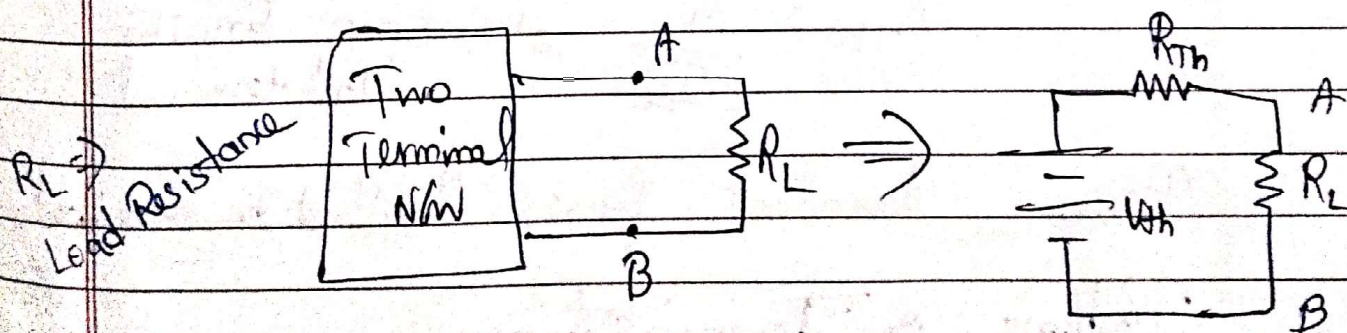Any two terminal bilateral linear NW can be replaced by an equivalent circuit that consisting of a single voltage source (V_{Th}) connected in series with resistance (R_{Th}).



Thévenin's Equivalent Circuit.

Procedure:

Step 1: Remove the load resistance R_L & find the open circuit (V_{Th}) across the load terminal.

Step 2: Deactivate all voltage source & current source in the circuit & find the total equivalent resistance looking through the load terminal.

Step 3: Obtain Thevenin's equivalent circuit by placing R_{Th} in series with V_{Th} .

Step 4: Reconnect R_L across the load terminal & find the load current using the formula.

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

where, $R_{Th} = \text{Thevenin's Resistance}$

$V_{Th} = \text{Thevenin's Voltage}$


In circuit containing dependent source,

$$R_{Th} = \frac{V_{oc}}{I_{sc}} \text{ at open circuited load terminal.}$$

Because dependent sources should not be deactivated.

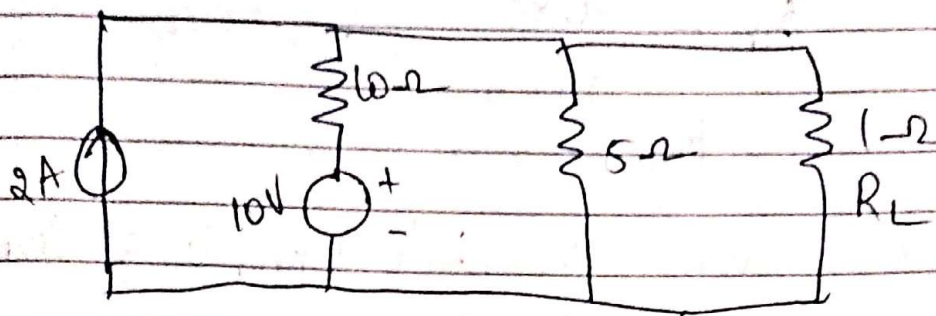Problems on Thevenin's Theorem

- Find the power loss in 1-2 resistors in given circuit using Thevenin's Theorem




Solution:

Let us consider 1Ω resistance as load.

Step 1:

Remove R_L & find V_{Th} .

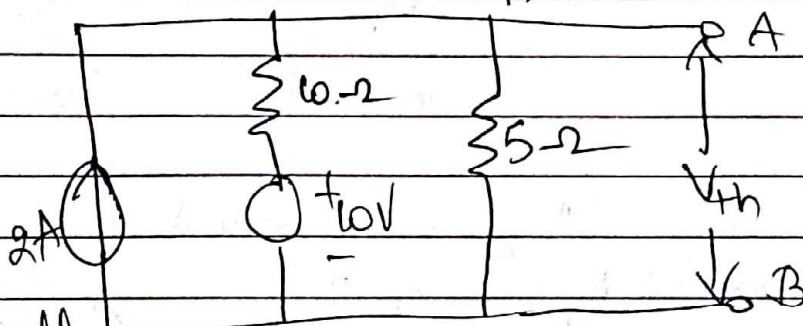

Using nodal analysis.


$$\text{At node A: } \frac{V_A - 10}{10} + \frac{V_A}{5} = 2$$

$$3V_A = 30$$

$$V_A = 10V$$

$$V_{Th} = V_A = 10V$$

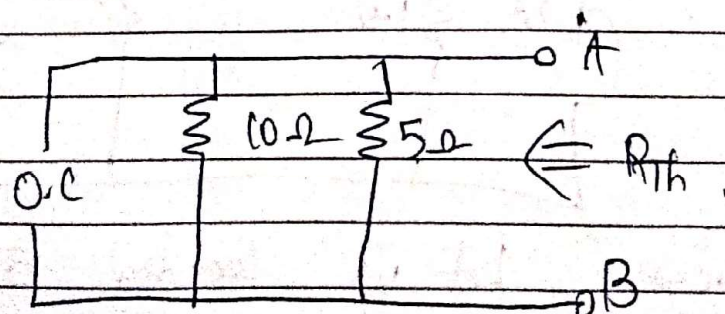
Step 2: Deactivate all sources & find R_{Th} .



$$R_{Th} = \frac{10 \times 5}{10 + 5} = 3.33 \Omega$$

$$R_{Th} = 3.33 \Omega$$

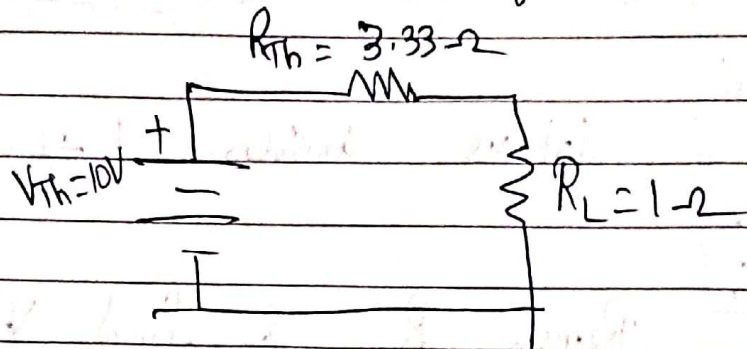Step 3: Draw $\leftarrow$ Thevenin's equivalent & Connect R_L .




$$\therefore I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{10}{3.33 + 1} = \frac{10}{4.33}$$

$$I_L = 2.3095 \text{ A}$$

Power loss in $R_L = I_L^2 R_L = (2.3095)^2 (1 \Omega)$

$$P_{1\Omega} = 5.3336 \text{ W}$$

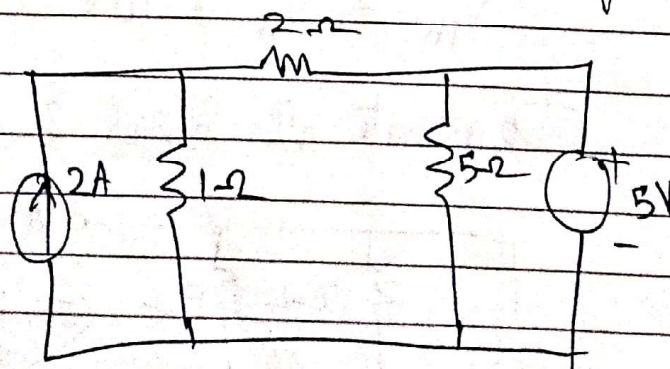
② Find the current through 5Ω resistor using Thevenin's theorem in the given circuit.



Solution

Let us consider 5Ω resistor as

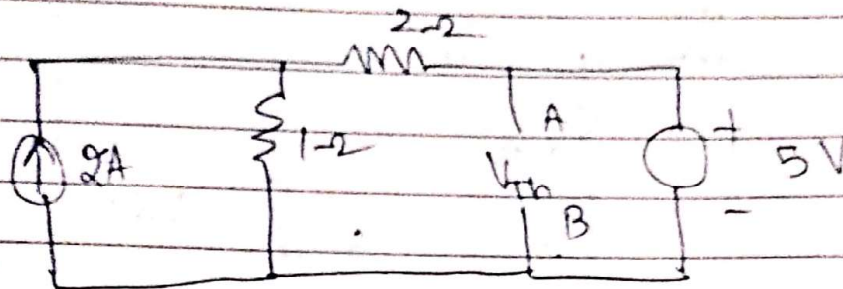
load resistor R_L
Step 1: Remove load R_L & find V_{th}



From the circuit,


$$V_{th} = V_{AB} = 5V$$

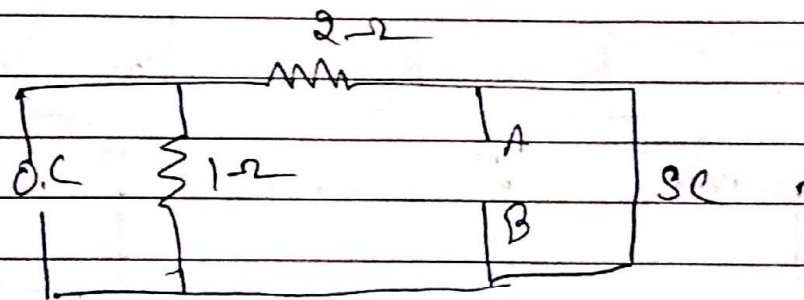Step 2: Deactivate all sources & find R_{th}



Since AB is short circuited $R_{th} = R_{AB} = 0\Omega$ (Resistance across a short circuit is zero)


Step 3: Thevenin's Equivalent Circuit

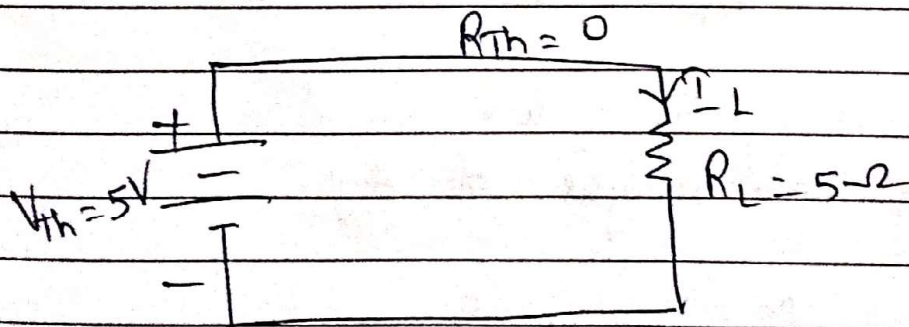

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{5}{0 + 5}$$

$$I_L = 1A$$

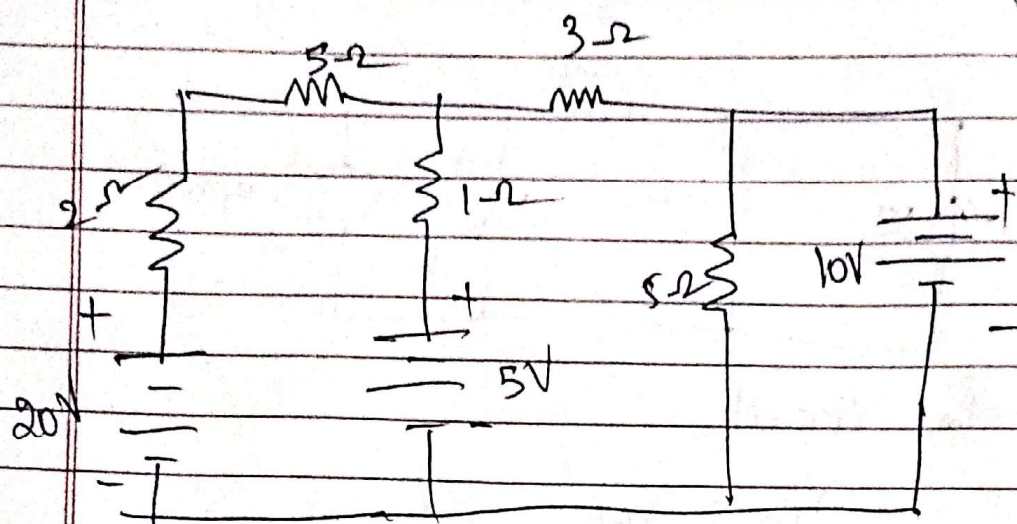
③ Find the power across 3Ω using Thevenin's theorem.



Solution

Let $R_L = 3\Omega$

Step 1: Remove R_L & find V_{Th}

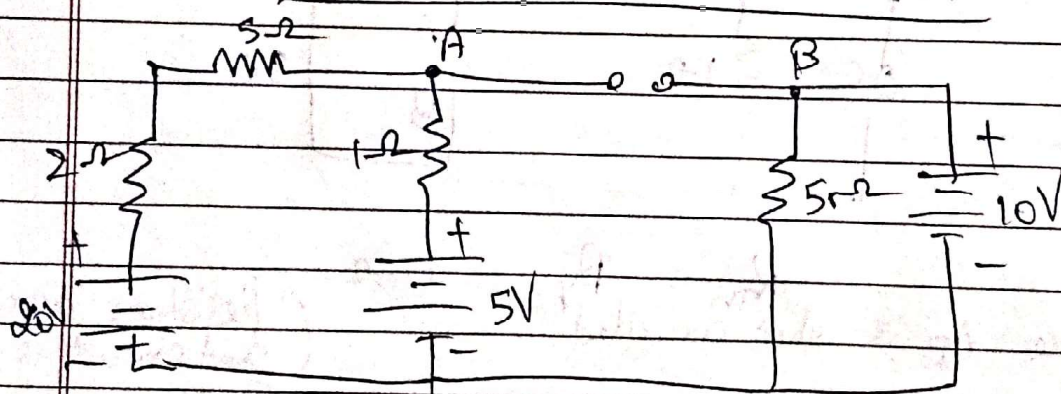

$$V_{Th} = V_A - V_B$$

$$V_B = 10V$$

Using nodal analysis at A,


$$\frac{V_A - 20}{2} + \frac{V_A - 5}{1} = 0$$

$$V_A = 6.875V$$

$$V_{th} = V_A - V_B = 6.875 - 10 = -3.125 V$$

$$V_{th} = -3.125 V$$

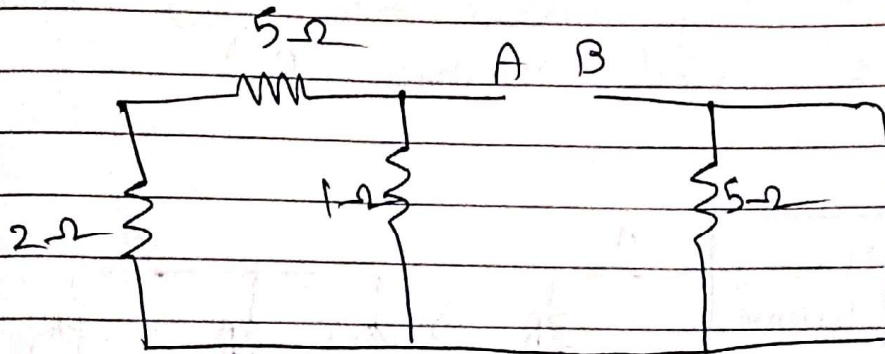Step 2 : Deactivate all sources & find R_{th} .




$$R_{th} = (5+2) \parallel 1 \Omega = \frac{7 \times 1}{7+1} = \frac{7}{8} =$$

$$0.875 \Omega$$

Ans

$$R_{th} = 0.875 \Omega$$

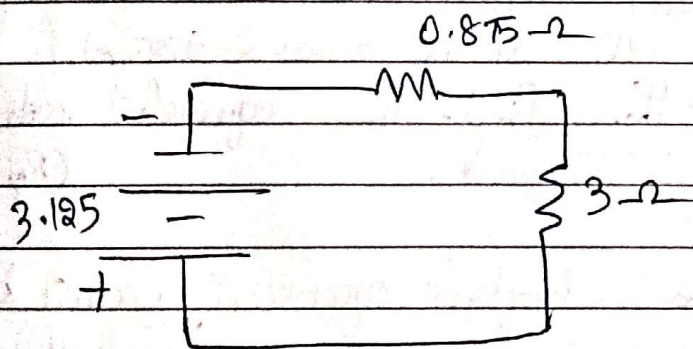

$$\text{Power loss} = I_L^2 R_L$$

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{-3.125}{0.875 + 3} = -0.8065 A$$

$$\text{Power loss} = I_L^2 R_L = (-0.8065)^2 (3)$$

$$P = 1.9513 W$$