

Digital-to-Analog Converter DAC0800

Digital-to-analog converters (DACs) translate digital information into equivalent analog voltage or current.

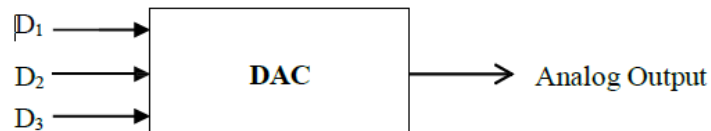


Fig :3-bit DAC

There are two types of DAC:

1. R-2-R ladder network and
2. weighted resistor network.

1. R-2-R ladder network DAC:


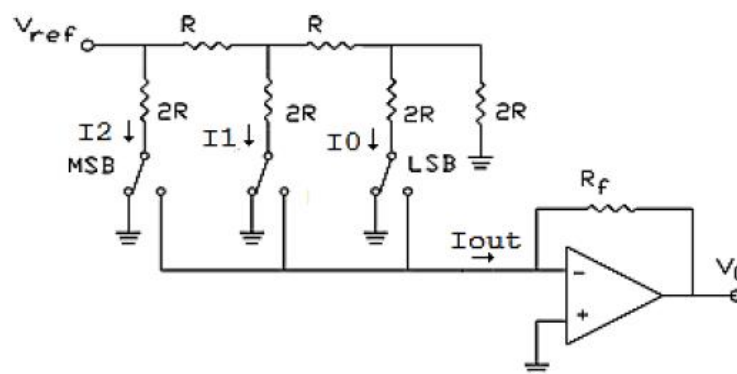


Fig: R-2-R ladder network DAC

It uses only two values of resistor R and $2R$. One of the switch positions is connected to the reference voltage and other switch position is connected to the ground. The switches in the circuit can be transistors which connect the resistance either to the ground or V_{ref} . The resistors are connected in such a way that for any possible binary input, the total current I_T is proportional to the binary input. The op amp converts the current I_T to a voltage signal V_0 .

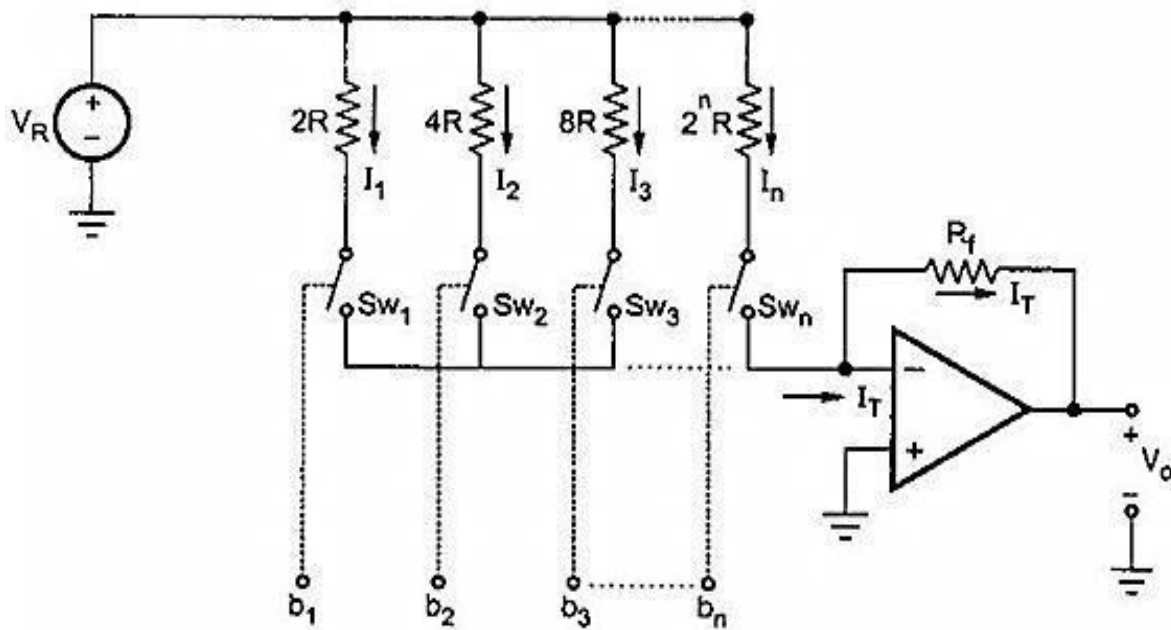2. Weighted resistor DAC:

The weighted resistor DAC uses an op-amp to sum n - binary weighted currents derived from a reference voltage V_R via current scaling resistors $2R, 4R, 8R, \dots, 2^n R$.



The switch positions are controlled by the digital input. When the digit input is 1, it connects the corresponding resistance to the reference voltage V_R , - otherwise it leaves the resistor open. Hence for the ON switch $I = V_R/R$ and for the OFF switch $I = 0$.

The op amp acts as a summing amplifier. The summing current flows through R_f . Hence, the total current through R_f is given as $I_f = I_1 + I_2 + I_3 + \dots + I_n$. The output voltage across R_f is given as: $V_o = -I_f R_f$

Interfacing DAC:

Features:

- DAC0800 is a monolithic 8-bit DAC manufactured by National semiconductor.
- It has settling time around 100ms
- It can operate on a range of power supply voltage i.e. from 4.5V to +18V. Usually the supply V_+ is 5V or +12V. The V_- pin can be kept at a minimum of -12V.
- Resolution of the DAC is 39.06mV

