

Incident matrix.

An incident matrix represents the graph of a given network.

Reduced incident matrix:-


If any row in the incident matrix is deleted, then it is reduced incident matrix.

$$A = \begin{cases} 1 & \text{Branch current leaving the node} \\ -1 & \text{Branch current entering the node} \\ 0 & \text{Branch current neither enter nor leave.} \end{cases}$$

write the incident matrix for the graph

soln

		Branches.						
		Nodes						
incident matrix =	1	a	b	c	d	e	f	
	1	-1	1	0	-1	0	0	
	2	0	-1	1	0	1	0	
	3	1	0	-1	0	0	1	
	4	0	0	0	-1	-1	-1	

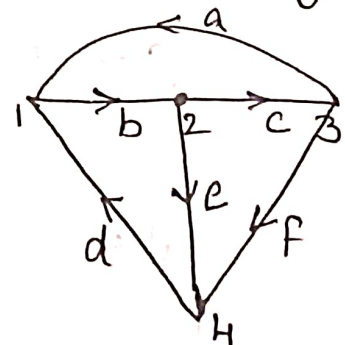

To check the correctness of the matrix the

sum of elements in each column is zero. (21) ~~(22)~~

Reduced incident matrix

node \ Branch	a	b	c	d	e	f
1	-1	1	0	-1	0	0
2	0	-1	1	0	1	0
3	1	0	-1	0	0	1

A =


The set matrix (or) loop matrix

It is used to find the loop & branch current in a circuit.

$$B_{ij} = \begin{cases} +1 & \text{direction of branch } ct \text{ \& } \\ & \text{loop } ct \text{ same} \\ -1 & \text{direction of branch } ct \text{ \& } \\ & \text{loop } ct \text{ not same} \\ 0 & \text{Branch } ct \text{ is not present} \\ & \text{in the loop.} \end{cases}$$

write the tie set matrix and the branch current relation for the graph given.
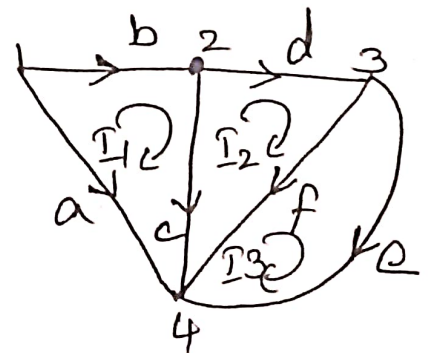
$$B = \begin{bmatrix} a & b & c & d & e & f \\ -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 & 1 \\ 0 & 0 & 0 & 0 & 1 & -1 \end{bmatrix} \begin{matrix} I_1 \\ I_2 \\ I_3 \end{matrix}$$



I_1, I_2, I_3 = Loop ct.

$I_a, I_b, I_c, I_d, I_e, I_f$ = branch ct

Relation B/w Branch & loop ckt.

$$B_T = \begin{bmatrix} \underline{I}_1 & \underline{I}_2 & \underline{I}_3 \\ -1 & 0 & 0 \\ 1 & 0 & 0 \\ 1 & -1 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 0 & 1 & -1 \end{bmatrix} \begin{matrix} \underline{I}_a \\ \underline{I}_b \\ \underline{I}_c \\ \underline{I}_d \\ \underline{I}_e \\ \underline{I}_f \end{matrix}$$

$$\underline{I}_1 = -\underline{I}_a$$

$$\underline{I}_d = \underline{I}_2$$

$$\underline{I}_b = \underline{I}_1$$


$$\underline{I}_e = 1$$

$$\underline{I}_c = \underline{I}_1 - \underline{I}_2$$

$$\underline{I}_f = \underline{I}_2 - \underline{I}_3$$

Derive the relationship between self inductance, (21)
 mutual inductance and the co-efficient of (23)
 coupling. [Apr/May 2022]

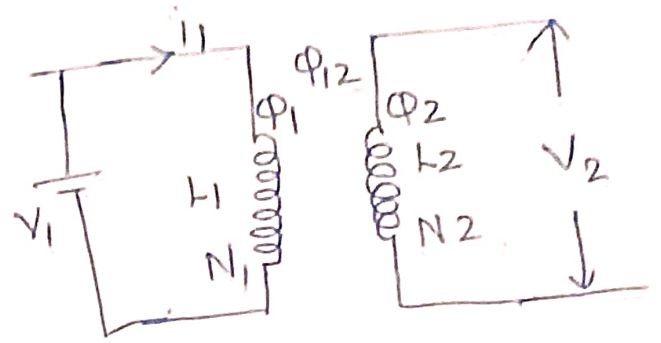The mutual inductance
 in the first coil due to
 second coil is,



$$M_{12} = \frac{K \Phi_1 N_2}{I_1} \quad \text{--- (1)}$$

The current I_1 flowing in the first coil
 produces a flux Φ_1 having turn N_1 , then the
 self inductance $L_1 = \frac{N_1 \Phi_1}{I_1}$ --- (2)

The current I_2 flowing in the second
 coil produces a flux Φ_2 having turn N_2 ,
 then the self inductance,

$$L_2 = \frac{N_2 \Phi_2}{I_2} \quad \text{--- (3)}$$

The mutual inductance in second coil
 due to first coil is,

$$M_{21} = \frac{K \Phi_2 N_1}{I_2} \quad \text{--- (4)}$$

18

multiplying 1 and 4.

24

$$M_{21} M_{12} = \frac{K \Phi_1 N_2}{I_1} \frac{K \Phi_2 N_1}{I_2}$$

$$\therefore M_{21} = M_{12} = M$$

$$M^2 = K^2 \frac{\Phi_1 \Phi_2 N_1 N_2}{I_1 I_2}$$

$\therefore$ By Faraday's Law.

$$= K^2 \left(\frac{\Phi_1 N_1}{I_1} \right) \left(\frac{\Phi_2 N_2}{I_2} \right)$$

$$M^2 = K^2 L_1 L_2$$

$$K^2 = \frac{M^2}{L_1 L_2}$$

$$K = \frac{M}{\sqrt{L_1 L_2}}$$

COE

Exam TimeTable
Placement
Exam

An

Nov/dec 20/25 end sem exam
20-25

Result per Time-table

QW - 20/25.

$\rightarrow$ Reg 20-21

$\rightarrow$ Nov/Dec 20-25.

Exam - Notification - end sem
& link (TimeTable).