

Page _____


$$\text{RMS Value} = 0.707 \times \text{Max Value}$$

$$\text{RMS value} = \sqrt{\frac{\text{Area of the Squared Curve}}{\text{Base}}}$$

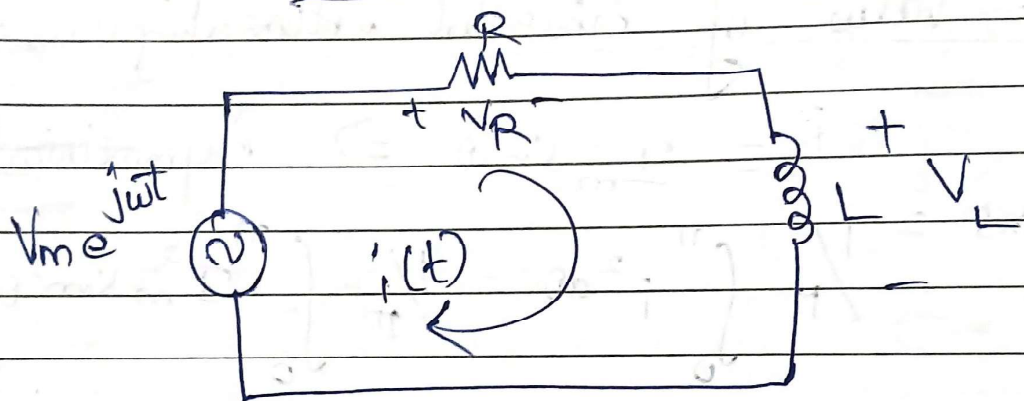3.2 Complex Forcing Functions

Euler's identity gives Sinusoidal & exponentials as related through complex numbers.

$$e^{j\theta} = \cos \theta + j \sin \theta$$



Basic first order circuit.

$$V_m e^{j\omega t} = V_m \cos(\omega t) + j V_m \sin \omega t$$

Apply KVL to the above circuit:

$$V_L + V_R - V_m e^{j\omega t} = 0$$

$$L \frac{di(t)}{dt} + R i(t) = V_m e^{j\omega t} \quad \text{--- (1)}$$

$$\text{Let } i(t) = I_m e^{j(\omega t + \phi)}$$

$$\frac{di(t)}{dt} = j\omega I_m e^{j(\omega t + \phi)} \quad \text{--- (2)}$$

Substituting equation (2) in equation (1).

$$j\omega L I_m e^{j(\omega t + \phi)} + R I_m e^{j(\omega t + \phi)} = V_m e^{j\omega t}$$

$$j\omega L I_m e^{j\omega t} e^{j\phi} + R I_m e^{j\omega t} e^{j\phi} = V_m e^{j\omega t}$$

$$e^{j\omega t} (j\omega L I_m e^{j\phi} + R I_m e^{j\phi}) = V_m e^{j\omega t} \quad \because [e^{a+b} = e^a \cdot e^b]$$

$$I_m (R + j\omega L) e^{j\phi} = V_m$$

$$I_m e^{j\phi} = V_m / (R + j\omega L)$$

$$|I_m e^{j\phi}| = V_m / \sqrt{R^2 + \omega^2 L^2} \quad \text{--- (3)}$$

$$\angle(I_m e^{j\phi}) = -\tan^{-1} \frac{\omega L}{R} \quad \text{--- (4)}$$

We know that

$$i(t) = I_m e^{j\phi} e^{j\omega t} = I_m e^{j(\omega t + \phi)}$$

$$= I_m [\cos(\omega t + \phi) + j \sin(\omega t + \phi)]$$

Substituting equation (4) & (3) in equation (5) (5)

$$i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \left[\cos\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right) + j \sin\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right) \right]$$

Real part of $i(t)$:

$$i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right)$$


Analysis of AC Circuit: Phase Relationship of R, L & C

(a) Purely Resistive

(b) Purely Inductive

(c) Purely Capacitive

Purely Resistive

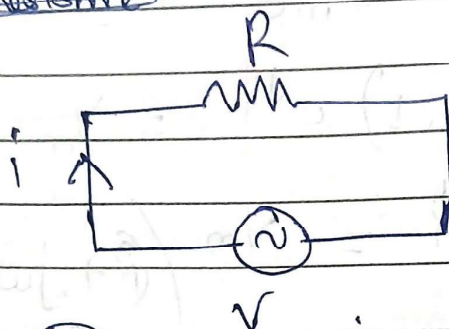

Purely resistive circuit,

$V = V_m \sin \omega t \rightarrow$ Applied voltage

$R =$ Resistance of circuit

$i =$ Instantaneous current flowing in the circuit

(i) By Ohm's law,

$$i = V/R$$

$$i = \frac{V_m \sin \omega t}{R} = I_m \sin \omega t$$


$$i = I_m \sin \omega t$$

$$I_m = V_m / R$$

$$\frac{i}{V} = \frac{I_m \sin \omega t}{V_m \sin \omega t} \quad \text{--- (1)}$$

$$V = V_m \sin \omega t \quad \text{--- (2)}$$

i & V are in phase.

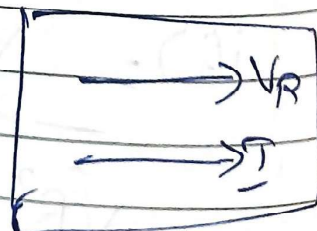

Phase Diagram.

Date _____
Page _____

② To represent V & I in polar form.

Let $V \rightarrow$ RMS Value $\Rightarrow V = V_m / \sqrt{2}$.

$I_m \rightarrow$ RMS Value $\Rightarrow I = I_m / \sqrt{2}$.

Writing equations (1) & (2) in polar form

$$V = |V| \angle 0^\circ$$

$$I = |I| \angle 0^\circ$$

③ Impedance (Z)


In AC Circuit, Ratio of V to I
 $\Rightarrow$ Impedance.

$$Z = V/I = |V| \angle 0^\circ$$

$$|I| \angle 0^\circ$$

$$Z = \frac{|V|}{|I|} \angle 0^\circ$$

$$Z = |Z| \angle 0^\circ$$

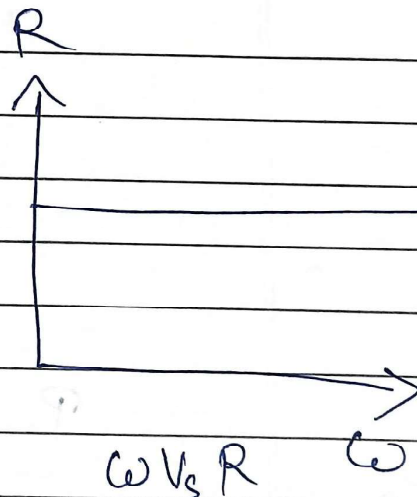

④ Instantaneous Power (W)

$$W = V I$$

$$W = V_m \sin \omega t \times I_m \sin \omega t = V_m \times I_m \sin^2 \omega t$$

$$W = V_m \times I_m \left[\frac{1 - \cos 2\theta}{2} \right] \quad \text{--- (3)} \quad \left[\because \sin^2 \theta = \frac{1 - \cos 2\theta}{2} \right]$$

At $\theta = \pi/2 \Rightarrow w \rightarrow$ maximum value $\Rightarrow V_m I_m \left[\frac{1 - \cos 2\theta}{2} \right]$

~~Also~~ $W = V_m I_m$

⑤ Average Power (P)

$$P = \frac{1}{\pi} \int_0^{\pi} w \cdot d\theta$$

Substituting equation (3) in equation (4)

$$= \frac{1}{\pi} \int_0^{\pi} V_m I_m \left(\frac{1 - \cos 2\theta}{2} \right) d\theta$$

$$= \frac{V_m I_m}{2\pi} \left[\int_0^{\pi} 1 d\theta + 0 \right]$$

$$= \frac{V_m I_m}{2\pi} (\pi)$$

$$P = \frac{V_m I_m}{2} = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}}$$

$$\boxed{P = VI}$$

⑥ Power Factor

The angle between the Voltage & Current is called phase angle & is denoted by ϕ


$\cos \phi = \text{Power Factor}$

Here $\phi = 0$

$\cos 0 = 1$

Power factor = $\cos \phi = 1$

Purely Inductive

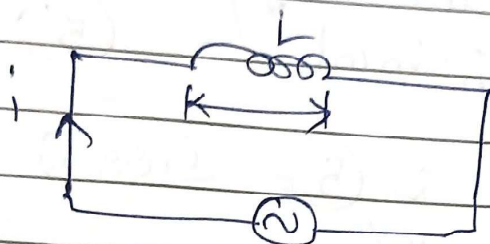

Purely Inductive Circuit

Let $V = V_m \sin \omega t$

i = Instantaneous current

L = Self inductance of coil

$V = L \frac{di}{dt}$ — (1)

$di = \frac{V}{L} dt$

Integrating on both sides

$i = \frac{1}{L} \int V dt = \frac{1}{L} \int V_m \sin \omega t dt$

$= \frac{V_m}{\omega L} [-\cos \omega t]$ $\left[\because \cos \theta = \sin \left(\frac{\pi}{2} - \theta \right) \right]$

$= \frac{V_m}{\omega L} [-\sin \left(\frac{\pi}{2} - \omega t \right)] = \frac{V_m}{\omega L} [\sin (\omega t - \frac{\pi}{2})]$

$i = \frac{V_m}{X_L} \sin (\omega t - \frac{\pi}{2})$ — (2)

$\therefore$ Inductive reactance
 $X_L = \omega L$