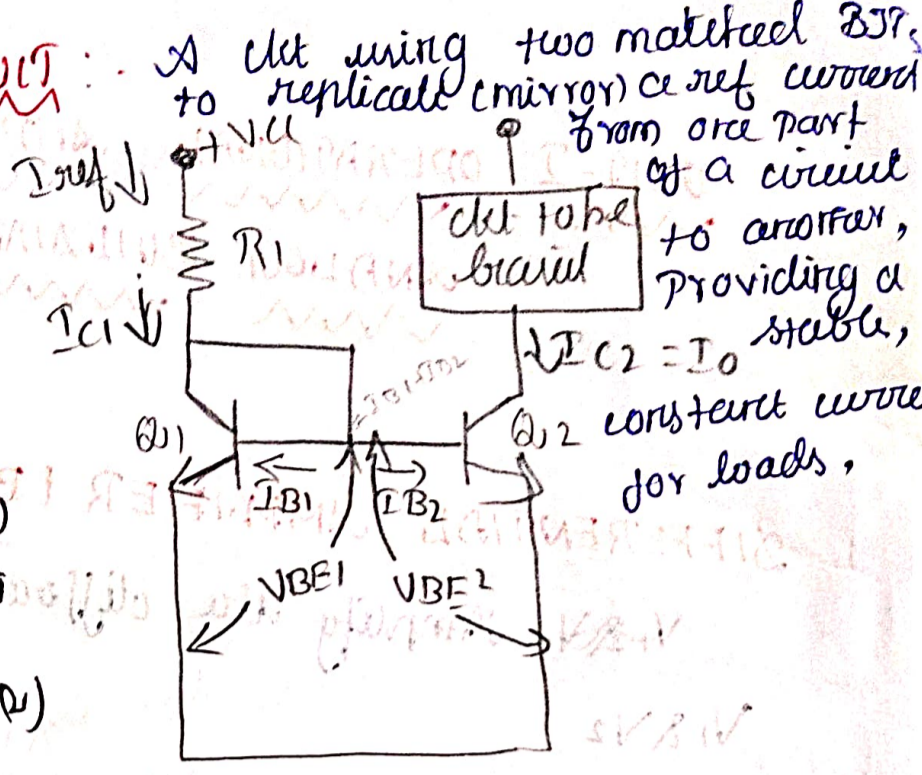


CURRENT MIRROR CIRCUIT



Let Analysis

$$I_{C1} = \beta F I_{ES} e^{V_{BE1}/VT} \quad (1)$$

$$I_{C2} = \beta F I_{ES} e^{V_{BE2}/VT} \quad (2)$$

From eqn (1) & (2)

$$\frac{I_{C2}}{I_{C1}} = \frac{\beta F I_{ES} e^{V_{BE2}/VT}}{\beta F I_{ES} e^{V_{BE1}/VT}}$$

$$\frac{I_{C2}}{I_{C1}} = e^{(V_{BE2} - V_{BE1})/VT}$$

Since $V_{BE1} = V_{BE2}$ (identical)

$$I_{C1} = I_{C2} = I_C = I_O$$

Also both the transistors are identical

$$\beta_1 = \beta_2 = \beta$$

KCL at the collector of the Q1 gives

$$I_{ref} = I_{C1} + I_{B1} + I_{B2}$$

$$= I_{C1} + \frac{I_{C1}}{\beta_1} + \frac{I_{C2}}{\beta_2} \quad (\because I_{C1} = I_{C2})$$

$$I_{ref} = I_{C1} \left(1 + \frac{1}{\beta_1} + \frac{1}{\beta_2} \right)$$

$$\beta = \beta_1 = \beta_2$$

$$I_{ref} = I_{C1} = \left(1 + \frac{1}{\beta} + \frac{1}{\beta} \right)^{-1} I_{ref}$$

$$I_{ref} = I_{C1} \left(1 + \frac{2}{\beta} \right) \quad \text{--- (4)}$$

$$I_{ref} = I_{C1} \left(\frac{\beta + 2}{\beta} \right)$$

$$I_{C1} = I_C = I_0$$

$$I_{ref} = I_C \left(\frac{\beta + 2}{\beta} \right)$$

$$I_C = I_{ref} \left(\frac{\beta}{\beta + 2} \right) \quad \text{--- (5)}$$

where,

$$I_{ref} = \frac{V_{CC} - V_{BE}}{R_{11}} = \frac{V_{CC} - 0.7}{R_{11}} \quad \text{--- (6)}$$

(V_{BE} = 0.7 → small)


from eqn (5)

$$I_C = I_{ref} \left(\frac{\beta}{\beta + 2} \right) \quad \rightarrow \beta$$

$\beta / \beta + 2$ almost unity

$$I_C = I_{ref}$$

$$I_{ref} = I_0$$

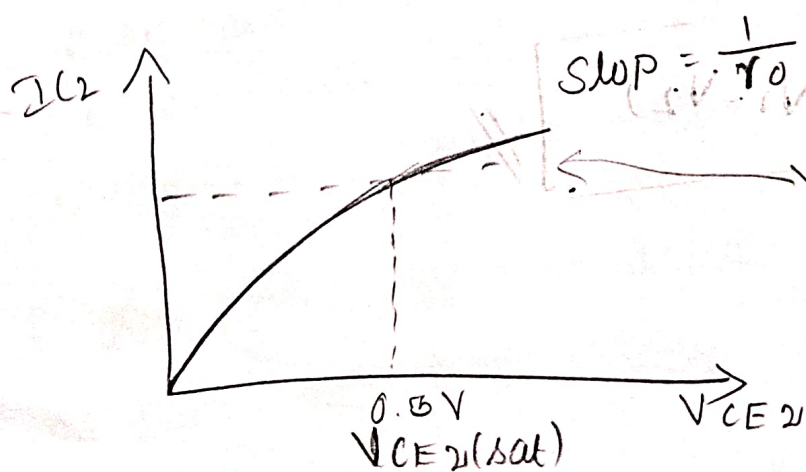

Draw back

$I \ll R$, overcome, $\beta < 1$. Overcome wider current

The nodal equation at node 'b' is

$$\frac{V_1 - V_b}{R_1} + \frac{0 - V_b}{R_2} = 0$$

$$\frac{V_1}{R_1} - \frac{V_b}{R_1} - \frac{V_b}{R_2} = 0$$

$$\frac{V_1}{R_1} = V_b \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$= V_b \left(\frac{R_1 + R_2}{R_1 \cdot R_2} \right)$$

$$V_b = \frac{V_1}{R_1} \left(\frac{R_1 \cdot R_2}{R_1 + R_2} \right) \longrightarrow (2)$$

$$\boxed{V_b = V_a}$$

$$\therefore V_d = V_a - V_b$$

$$= V_a - V_a$$

From equation (1)

$$\frac{V_0}{R_2} = \frac{V_1}{R_1} \left(\frac{R_1 \cdot R_2}{R_1 + R_2} \right) \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{V_2}{R_1}$$
$$= \frac{V_1}{R_1} \left(\frac{R_1 \cdot R_2}{R_1 + R_2} \right) \left(\frac{R_2 + R_1}{R_1 \cdot R_2} \right) - \frac{V_2}{R_1}$$

$$\frac{V_0}{R_2} = \frac{V_1}{R_1} - \frac{V_2}{R_1}$$

$$\therefore \boxed{V_0 = \frac{R_2}{R_1} (V_1 - V_2)}$$