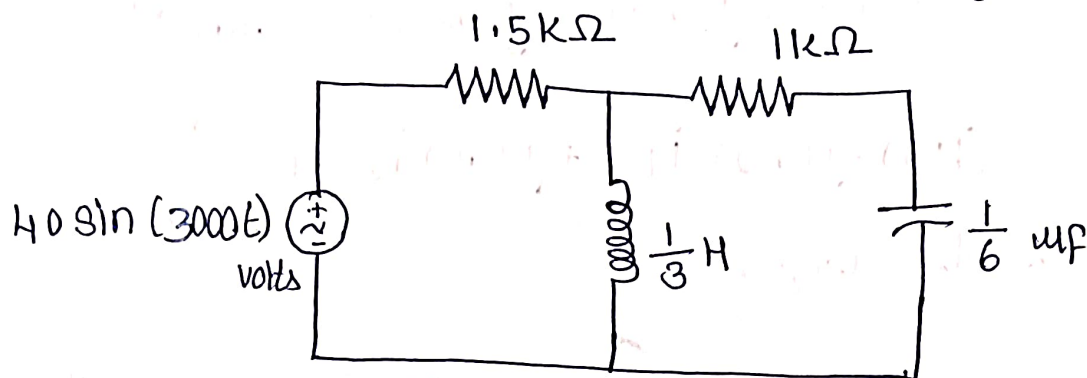


Determine the mesh current for the following circuit using mesh current analysis



- 1) All the passive elements should be represented in terms of impedance.
- 2) Represent time domain current and voltage source in terms of ~~imped~~ polar form.


$$V_m \sin(\omega t) = V_m \angle 0^\circ$$

$$40 \sin(3000t) = 40 \angle 0^\circ \quad [\omega = 3000]$$

$$X_L = j\omega L = j \times 3000 \times \frac{1}{3} = 1000j$$

$$X_C = \frac{1}{j\omega C} = \frac{1}{j \times \frac{1000}{500} \times \frac{1}{62}} = -j \times \frac{10^6}{500} = -j2000$$

The ckt is drawn as,

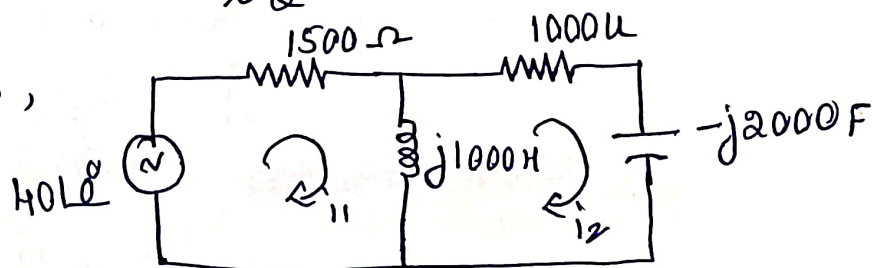

(34) Apply KVL to loop 1,

$$+40 \angle 0^\circ - 1500 i_1 - j1000 (i_1 - i_2) = 0$$

$$1500 i_1 - j1000 i_1 + j1000 i_2 = 40 \angle 0^\circ$$

$$(1500 - j1000) i_1 + j1000 i_2 = 40 \angle 0^\circ \quad \text{--- (1)}$$

Apply KVL to loop 2,

$$-1000j (I_2 - I_1) - 1000 I_2 + j2000 I_2 = 0.$$

$$-1000j I_2 + 1000j I_1 - 1000 I_2 + j2000 I_2 = 0.$$

$$1000j I_1 + (1000j - 1000) I_2 = 0$$

$$\text{--- (2)}$$

$$I_2 = I_1$$

$$\begin{bmatrix} 1500 - j1000 & 1000j \\ 1000j & -1000 + 1000j \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 40 \angle 0^\circ \\ 0 \end{bmatrix}$$

$$\Delta = (1500 - j1000)(-1000 + j1000) - j^2(1000)^2$$

$$= -1500000 + j1500000 + j1000000 - j5010000 + 1000000$$

$$\Delta_2 = j401000$$


$$\Delta_1 = 401000 - j401000$$

$$I_2 = \frac{\Delta_2}{\Delta} = -0.0016 + j0.0112$$

$$I_1 = 0.0128 - j0.0096$$

$$0.0113 \angle 98.13^\circ \text{ A}$$

$$= 0.0113 \angle 98.13^\circ$$

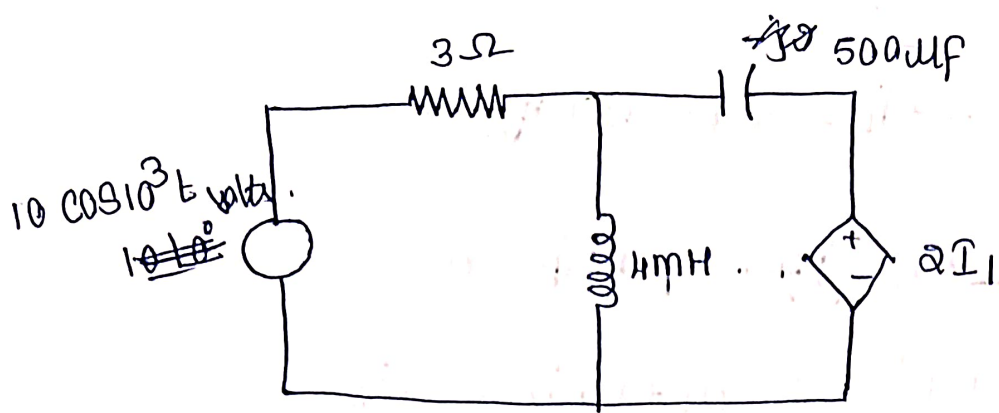

mesh analysis
(35)

soln

$$V_m \cos(\omega t) = 10 \cos(10^3 t) \quad \text{in polar form}$$

$$V_m = 10 \quad \omega t = 10^3 t \Rightarrow \omega = 10^3 \quad \begin{matrix} V_m \angle 0^\circ \\ 10 \angle 0^\circ \end{matrix}$$

$$X_L = j\omega L$$

$$= j10^3 \times 4 \times 10^{-3}$$

$$\boxed{X_L = j4 \Omega}$$


$$X_C = \frac{1}{j\omega C}$$

$$= \frac{1}{j10^3 \times 500 \times 10^{-6}}$$

$$= -j \frac{1}{.500}$$

$$\boxed{X_C = -j2 \Omega}$$

Redrawing the circuit in time domain

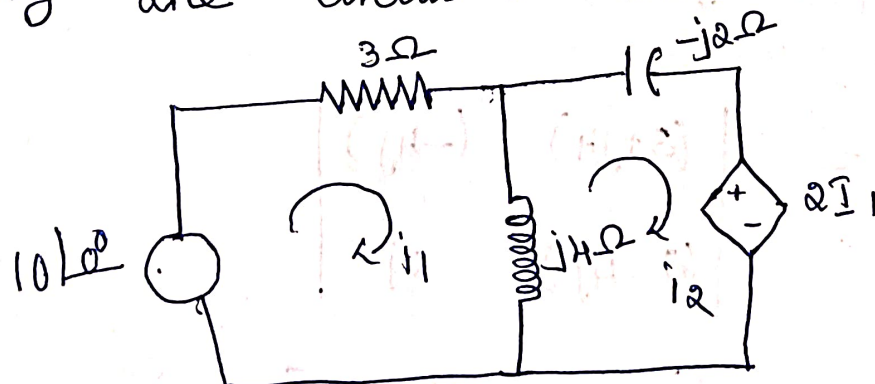

(36)

$$10 \angle 0^\circ - 3\dot{I}_1 - (\dot{I}_1 - \dot{I}_2) 4j = 0$$

$$10 \angle 0^\circ = 3\dot{I}_1 - j4\dot{I}_1 + 4j\dot{I}_2 = 0$$

$$10 \angle 0^\circ = 3\dot{I}_1 + j4\dot{I}_1 - j4\dot{I}_2$$

$$= (3+j4)\dot{I}_1 - j4\dot{I}_2 \quad \text{--- (1)}$$

$$-j4(\dot{I}_2 - \dot{I}_1) = (-j2) - 2\dot{I}_1 = 0$$

$$-j4\dot{I}_2 + j4\dot{I}_1 + j2\dot{I}_2 - 2\dot{I}_1 = 0$$

$$(-2+j4)\dot{I}_1 - 2j\dot{I}_2 = 0 \quad \text{--- (2)}$$

xy by -

$$(2-j4)\dot{I}_1 + 2j\dot{I}_2 = 0 \quad \text{--- (3)}$$

$$\begin{vmatrix} (3+j4) & (-4j) \\ (2-j4) & 2j \end{vmatrix} \begin{bmatrix} \dot{I}_1 \\ \dot{I}_2 \end{bmatrix} = \begin{bmatrix} 10 \angle 0^\circ \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} (3+j4) & (-4j) \\ (2-j4) & 2j \end{vmatrix}$$

$$= [6j - 8] - [-8j - 16]$$

$$\boxed{\Delta = 14j + 8}$$

(37)

$$\Delta_2 = \begin{bmatrix} 3+j4 & 10 \\ 2-j4 & 0 \end{bmatrix}$$

$$= -(2-j4)10$$

$$\boxed{\Delta_1 = -20 + 40j}$$

$$\Delta_1 = \begin{vmatrix} 10 & -4j \\ 0 & 2j \end{vmatrix}$$

$$= 20j$$

$$\hat{I}_1 = \frac{\Delta_1}{\Delta} = \frac{20j}{8+14j} = 1.076 + 0.615j$$

$$I_1 = 1.24 \angle 29.7^\circ$$

$$\boxed{I_1 = 1.24 \cos(10^3 t + 29.7^\circ)}$$

$$\hat{I}_2 = \frac{\Delta_2}{\Delta} = \frac{-20+40j}{8+14j} = 1.53 + 2.30j$$

$$I_2 = 2.77 \angle 56.3^\circ$$

$$I_2 = 2.77 \cos(10^3 t + 56.3^\circ)$$

38

$$\Delta = -500000 + 2500,000 + 1000000$$

$$= -500000 + 3500,000$$

$$0.111111 - =$$

$$[100 + 0.111111 - 1 \Delta]$$

$$\left[\begin{array}{cc|c} 100 & 0.111111 & 1 \Delta \\ 100 & 0 & 0 \end{array} \right]$$

$$100$$

$$[100 + 0.111111 - 1 \Delta] = \frac{100}{100 + 0.111111} = \frac{1 \Delta}{\Delta} = 11$$

$$100 + 0.111111 - 1 \Delta$$

$$100 + 0.111111 - 1 \Delta$$

$$100 + 0.111111 - 1 \Delta$$

$$100 + 0.111111 - 1 \Delta$$

$$100 + 0.111111 - 1 \Delta$$