

## 1.2 OPERATIONAL AMPLIFIERS

An operational amplifier is a direct coupled high gain amplifier consisting of one or more differential amplifiers, followed by a level translator and an output stage. It is a versatile device that can be used to amplify ac as well as dc input signals & designed for computing mathematical functions such as addition, subtraction ,multiplication, integration & differentiation.

### IDEAL OPERATIONAL AMPLIFIERS

Infinite input resistance  $R_i$ , so that almost any signal source can drive it and there is no loading of the proceeding stage. Figure 1.2.1 shows the circuit symbol of an op-amp.

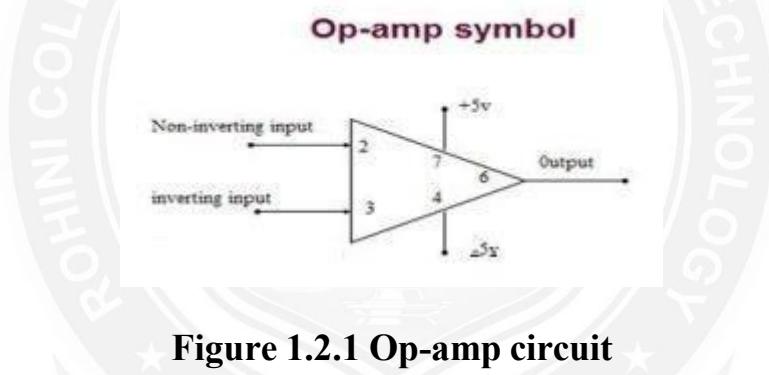


Figure 1.2.1 Op-amp circuit

[source: [https://www.brainkart.com/subject/Linear-Integrated-Circuits\\_220/](https://www.brainkart.com/subject/Linear-Integrated-Circuits_220/)]

### IDEAL OP-AMP CHARACTERISTICS

- Infinite voltage gain  $A$ .
- Infinite input resistance  $R_i$ , so that almost any signal source can drive it and there is no loading of the proceeding stage.
- Zero output resistance  $R_o$ , so that the output can drive an infinite number of other devices.
- Zero output voltage, when input voltage is zero.
- Infinite bandwidth, so that any frequency signals from 0 to  $\infty$  HZ can be amplified without attenuation.
- Infinite common mode rejection ratio, so that the output common mode noise voltage is zero.

- Infinite slew rate, so that output voltage changes occur simultaneously with input voltage changes.

## GENERAL OPERATIONAL AMPLIFIER STAGES AND INTERNAL CIRCUIT DIAGRAMS OF IC 741

An operational amplifier generally consists of three stages, namely

1. A differential amplifier
2. Additional amplifier stages to provide the required voltage gain and dc level shifting.
3. An emitter-follower or source follower output stage to provide current gain and low output resistance.

A low-frequency or dc gain of approximately 104 is desired for a general purpose op-amp and hence, the use of active load is preferred in the internal circuitry of op-amp. The output voltage is required to be at ground, when the differential input voltages are zero, and this necessitates the use of dual polarity supply voltage. Since the output resistance of op-amp is required to be low, a complementary push-pull emitter – follower or source follower output stage is employed. Figure 1.2.2 Shows the Stages of general Operational Amplifier and internal circuit diagrams of IC 741. Moreover, as the input bias currents are to be very small of the order of pico amperes, an FET input stage is normally preferred.


### INPUT STAGE

The input differential amplifier stage uses p-channel JFETs  $M_1$  and  $M_2$ . It employs a three-transistor active load formed by  $Q_3$ ,  $Q_4$ , and  $Q_5$ . The bias current for the stage is provided by a two-transistor current source using PNP transistors  $Q_6$  and  $Q_7$ . Resistor  $R_1$  increases the output resistance seen looking into the collector of  $Q_4$  as indicated by  $R_{04}$ . This is necessary to provide bias current stability against the transistor parameter variations. Resistor  $R_2$  establishes a definite bias current through  $Q_5$ . A single ended output is taken out at the collector of  $Q_4$ . MOSFET's are used in place of JFETs with

additional devices in the circuit to prevent any damage for the gate oxide due to electrostatic discharges.

## GAIN STAGE

The second stage or the gain stage uses Darlington transistor pair formed by  $Q_8$  and  $Q_9$  as shown in figure 1.2.2. The transistor  $Q_8$  is connected as an emitter follower, providing large input resistance. Therefore, it minimizes the loading effect on the input differential amplifier stage. The transistor  $Q_9$  provides an additional gain and  $Q_{10}$  acts as an active load for this stage. The current mirror formed by  $Q_7$  and  $Q_{10}$  establishes the bias current for  $Q_9$ . The VBE drop across  $Q_9$  and drop across  $R_5$  constitute the voltage drop across  $R_4$ , and this voltage sets the current through  $Q_8$ . It can be set to a small value, such that the base current of  $Q_8$  also is very less.

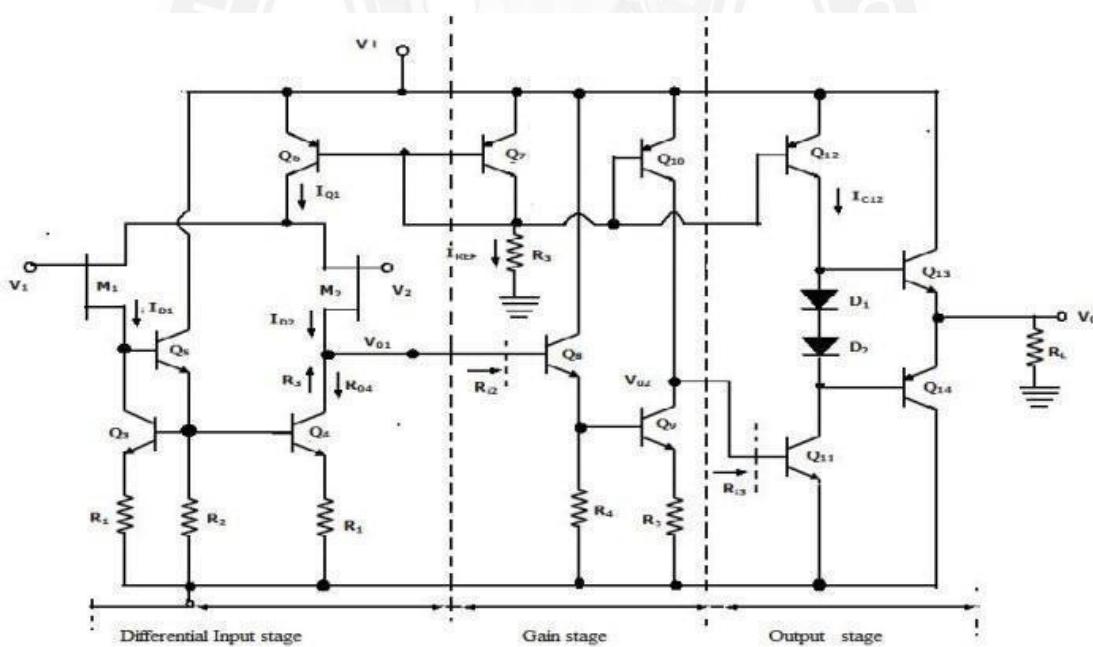

**Figure 1. 2.2 Stages of general Operational Amplifier and internal circuit diagrams of IC 741**

[source: [https://www.brainkart.com/subject/Linear-Integrated-Circuits\\_220/](https://www.brainkart.com/subject/Linear-Integrated-Circuits_220/)]

## OUTPUT STAGE

The final stage of the op-amp is a class AB complementary push-pull output stage.  $Q_{11}$  is an emitter follower, providing a large input resistance for minimizing the loading effects on the gain stage. Bias current for  $Q_{11}$  is provided by the current mirror formed

by  $Q_7$  and  $Q_{12}$ , through  $Q_{13}$  and  $Q_{14}$  for minimizing the cross over distortion. Transistors can also be used in place of the two diodes.

The overall voltage gain  $A_V$  of the op-amp is the product of voltage gain of each stage as given by

$$A_V = |A_d| |A_2| |A_3|$$

Where  $A_d$  is the gain of the differential amplifier stage,  $A_2$  is the gain of the second gain stage and  $A_3$  is the gain of the output stage.

## IC 741 BIPOLAR OPERATIONAL AMPLIFIER INTERNAL CIRCUIT DIAGRAM

The IC 741 produced since 1966 by several manufacturers is a widely used general purpose operational amplifier. Figure 1.2.2 shows the equivalent circuit of the 741 op-amp, divided into various individual stages. The op-amp circuit consists of three stages.

1. The input differential amplifier
2. The gain stage
3. the output stage.

A bias circuit is used to establish the bias current for the whole of the circuit in the  $I_C$ . The op-amp is supplied with positive and negative supply voltages of value  $\pm 15V$  and the supply voltages as low as  $\pm 5V$  can also be used.

### BIAS CIRCUIT

The reference bias current  $I_{REF}$  for the 741 circuit is established by the bias circuit consisting of two diodes-connected transistors  $Q_{11}$  and  $Q_{12}$  and resistor  $R_5$ . The Widlar current source formed by  $Q_{11}$ ,  $Q_{10}$  and  $R_4$  provide bias current for the differential amplifier stage at the collector of  $Q_{10}$ . Transistors  $Q_8$  and  $Q_9$  form another current mirror providing bias current for the differential amplifier. The reference bias current  $I_{REF}$  also provides mirrored and proportional current at the collector of the double -collector lateral PNP transistor  $Q_{13}$ . The transistors  $Q_{13}$  and  $Q_{12}$  thus form a two-output current mirror with  $Q_{13A}$  providing bias current for output stage and  $Q_{13B}$  providing bias current for  $Q_{17}$ . The transistors  $Q_{18}$  and  $Q_{19}$  provide dc bias for the output stage. Formed by  $Q_{14}$  and

$Q_{20}$  and they establish two VBE drops of potential difference between the bases of  $Q_{14}$  and  $Q_{18}$ .

## INPUT STAGE

The input differential amplifier stage consists of transistors  $Q_1$  through  $Q_7$  with biasing provided by  $Q_8$  through  $Q_{12}$ . The transistor  $Q_1$  and  $Q_2$  form emitter – followers contributing to high differential input resistance, and whose output currents are inputs to the common base amplifier using  $Q_3$  and  $Q_4$  which offers a large voltage gain. The transistors  $Q_5$ ,  $Q_6$  and  $Q_7$  along with resistors  $R_1$ ,  $R_2$  and  $R_3$  from the active load for input stage. The single-ended output is available at the collector of  $Q_6$ . The two null terminals in the input stage facilitate the null adjustment. The lateral PNP transistors  $Q_3$  and  $Q_4$  provide additional protection against voltage breakdown conditions. The emitter-base junction  $Q_3$  and  $Q_4$  have higher emitter-base breakdown voltages of about 50V. Therefore, placing PNP transistors in series with NPN transistors provide protection against accidental shorting of supply to the input terminals.

## GAIN STAGE

The Second or the gain stage consists of transistors  $Q_{16}$  and  $Q_{17}$ , with  $Q_{16}$  acting as an emitter – follower for achieving high input resistance. The transistor  $Q_{17}$  operates in common emitter configuration with its collector voltage applied as input to the output stage. Level shifting is done for this signal at this stage.

Internal compensation through Miller compensation technique is achieved using the feedback capacitor  $C_1$  connected between the output and input terminals of the gain stage.

## OUTPUT STAGE

The output stage is a class AB circuit consisting of complementary emitter follower transistor pair  $Q_{14}$  and  $Q_{20}$ . Hence, they provide an effective loss output resistance and current gain. The output of the gain stage is connected at the base of  $Q_{22}$ , which is connected as an emitter follower providing a very high input resistance, and it offers no appreciable loading effect on the gain stage. It is biased by transistor  $Q_{13}$  which also

drives Q18 and Q19, that are used for establishing a quiescent bias current in the output transistors Q<sub>14</sub> and Q<sub>20</sub>.

