



# ROHINI

## COLLEGE OF ENGINEERING & TECHNOLOGY

Approved by AICTE and Affiliated to Anna University (An ISO Certified Institution) | Accredited with A+ Grade by NAAC  
Recognized under Section 2(f) of University Grants Commission, UGC ACT 1956  
(AUTONOMOUS)

### PRACTICAL USE IN AUDIO MIXER

#### Definition:

An **audio mixer** is a device or circuit that **combines two or more audio signals** into a single output signal without significant distortion. In LICs, this is implemented using **operational amplifiers (op-amps)**.

#### **Practical Uses**

##### **1. Combining Multiple Audio Sources**

- In recording studios, radio, or public address systems, signals from **microphones, instruments, or playback devices** are combined into one output.
- LICs allow this combination with **minimal hardware** and compact design.

##### **2. Volume Control and Signal Adjustment**

- Each input can have a **potentiometer or gain control**, so the operator can adjust the level of individual audio sources before mixing.
- This ensures **balanced output** without distortion.

##### **3. Signal Isolation and Impedance Matching**

- Op-amp-based mixers prevent one source from **loading or affecting another**.
- Useful in circuits where multiple microphones or line inputs are connected.

##### **4. Pre-Amplification**


- Weak signals from microphones can be amplified in LICs before mixing.
- LICs can provide both **mixing and amplification** in one compact circuit.

## 5. Stereo and Mono Mixing

- LIC mixers can combine signals for **mono output** or mix **left and right channels** for stereo systems.
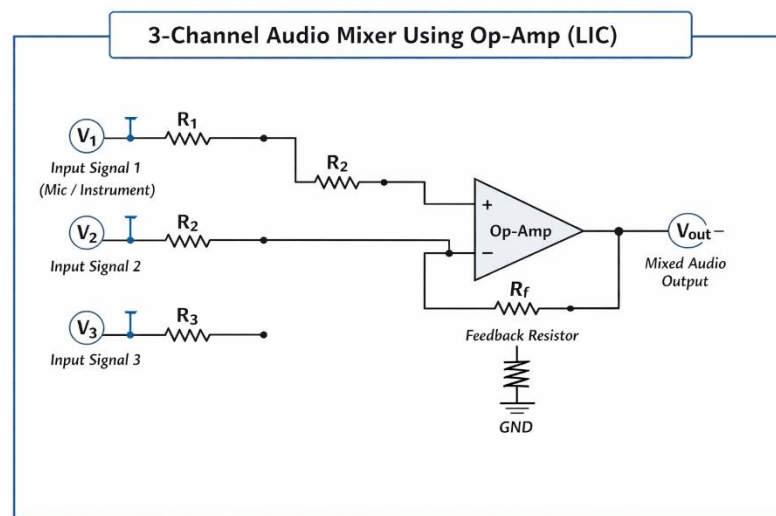
### Basic Audio Mixer Circuit

- Usually implemented as an **inverting summing amplifier** using an **op-amp**.



Audio Mixer is designed to combine multiple audio signals into a single output. Each input signal ( $V_1$ ,  $V_2$ ,  $V_3$ ) passes through an input resistor ( $R_1$ ,  $R_2$ ,  $R_3$ ) which controls the level of the signal and prevents interference between sources. These signals are fed into the inverting input of an op-amp, while the feedback resistor ( $R_f$ ) determines the overall gain of the mixer. The op-amp adds all input signals together and provides a mixed audio output ( $V_{out}$ ) with low distortion. This configuration allows volume control for each channel (if resistors are replaced by potentiometers), ensures signal isolation, and produces a clean, compact, and efficient audio mixing circuit suitable for recording, broadcasting, and live sound applications.

- Formula for output voltage:

$$V_{out} = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \right)$$

Where:

- $V_1, V_2, \dots, V_n$  = input audio signals
- $R_1, R_2, \dots, R_n$  = input resistors
- $R_f$  = feedback resistor

**Key Features in LIC Mixers:**

- Compact and low-cost
- High input impedance
- Low distortion and noise
- Easy to scale for multiple channels

**Notes:**

Audio mixers in LICs (op-amp based) are used to combine multiple audio signals, control volume, match impedance, and amplify signals for recording or broadcasting systems. They are simple, compact, and provide clean, low-noise output.

