
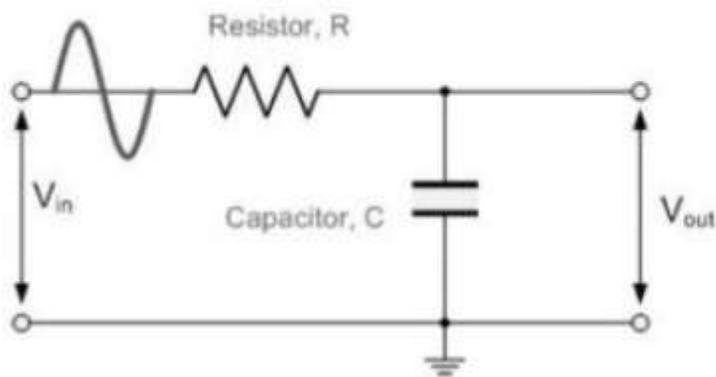


RC Low Pass Filter Circuit (Integrator)


- The **Integrator** is basically a low pass filter circuit
- converts a square wave "step" response input signal into a triangular shaped waveform output as the capacitor charges and discharges.
- A **Triangular** waveform consists of alternate but equal, positive and negative ramps.
- It allows low frequency components
- A simple passive Low Pass Filter or LPF, can be easily made by connecting together in series a single Resistor with a single Capacitor

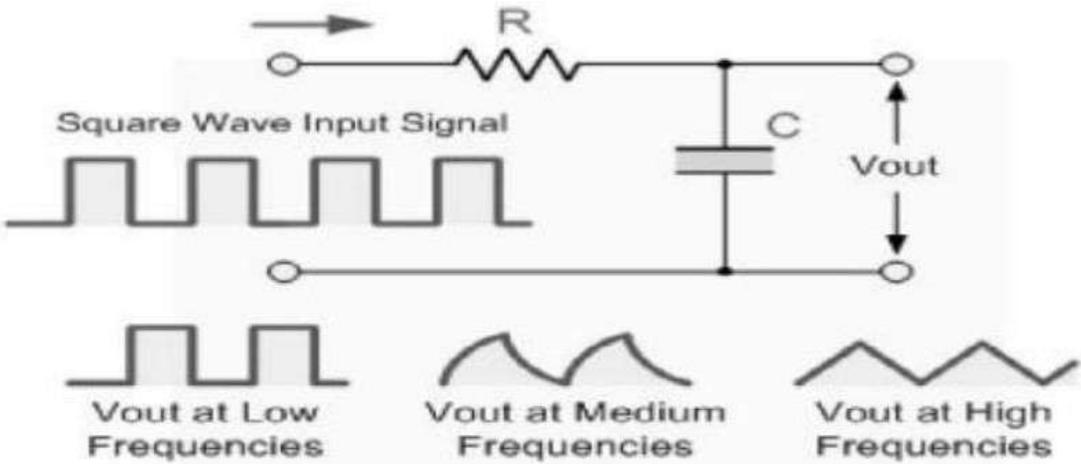

- input signal (V_{in}) is applied to the series combination (both the Resistor and Capacitor together)
- the output signal (V_{out}) is taken across the capacitor only.
- This type of filter is known generally as a "first-order filter" or "one-pole filter"



RC Integrator Time Constant

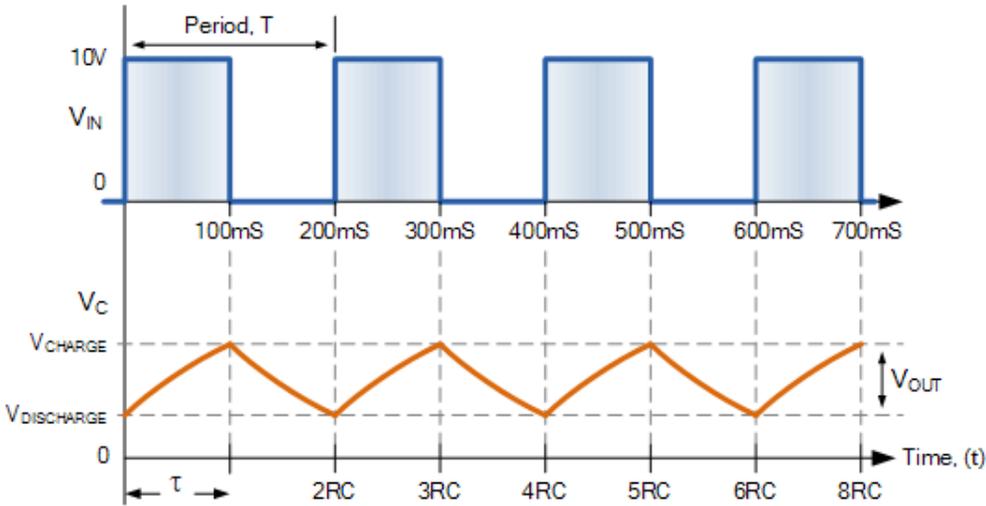


ROHINI COLLEGE OF ENGINEERING & TECHNOLOGY

- Converting one type of electronic signal to another for use in wave-generating or wave- shaping circuits.
- The reactance of a capacitor varies inversely proportional with frequency,

$$X_c = 1/(2\pi fC)$$


- **X_c**- reactance of a capacitor
- **f**- frequency
- RC High Pass Filter Circuit

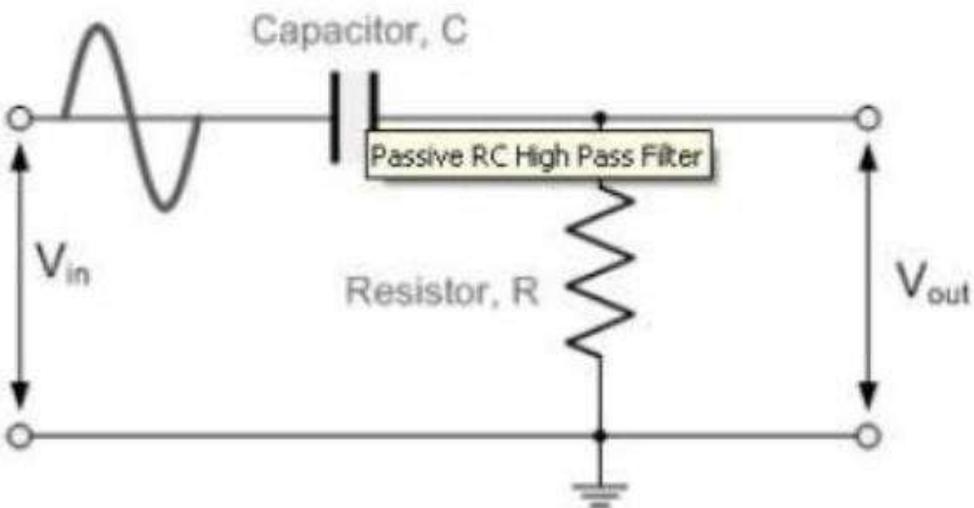connecting together in series a single Resistor with a single Capacitor



RC Differentiator

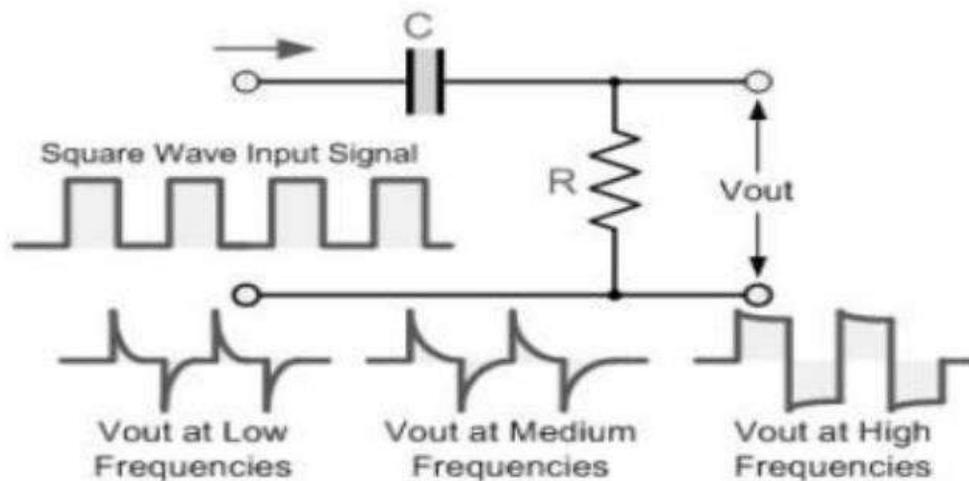- **Square Wave** signal operating in the time domain giving an impulse or step response input, the output waveform will consist of short duration pulse or spikes.



- The time constant $t=RC$
- Square wave input waveform produces two spikes at the output, one positive and one negative and whose amplitude is equal to that of the input.