



# ROHINI

## COLLEGE OF ENGINEERING & TECHNOLOGY

Approved by AICTE and Affiliated to Anna University (An ISO Certified Institution) | Accredited with A+ Grade by NAAC  
Recognized under Section 2(f) of University Grants Commission, UGC ACT 1956

(AUTONOMOUS)

### FET DIFFERENTIAL AMPLIFIER

The JFET differential amplifier with resistive load is considered for the analysis. MOSFETs are widely used in the input stages due to their better stability.

- i. FETs are used instead of BJT when we require
  - a. High Impedance
  - b. Better Stability
- ii. Fig.3.23 shows the dual input balanced output differential amplifier using JFET.

Apply KVL to the input loop,

$$V_{I1} - V_{I2} = V_{GS1} - V_{GS2}$$
$$V_{I1} = V_{GS1} - V_{GS2} + V_{I2}$$

We know that

$$V_{GS} = V_P \left( 1 - \sqrt{\frac{I_D}{I_{DSS}}} \right)$$

Where  $I_D \rightarrow$  Saturation drain current

$I_{DSS} \rightarrow I_{DS}$  when  $V_{GS} = 0$

$V_P \rightarrow$  Pinch-off voltage


The differential voltage in the input

$$V_{ID} = V_{I1} - V_{I2}$$

Assuming  $Q_1$  and  $Q_2$  as ideal transistors, then

$$V_{P1} = V_{P2}$$

$$I_{SS} = I_{D1} + I_{D2}$$

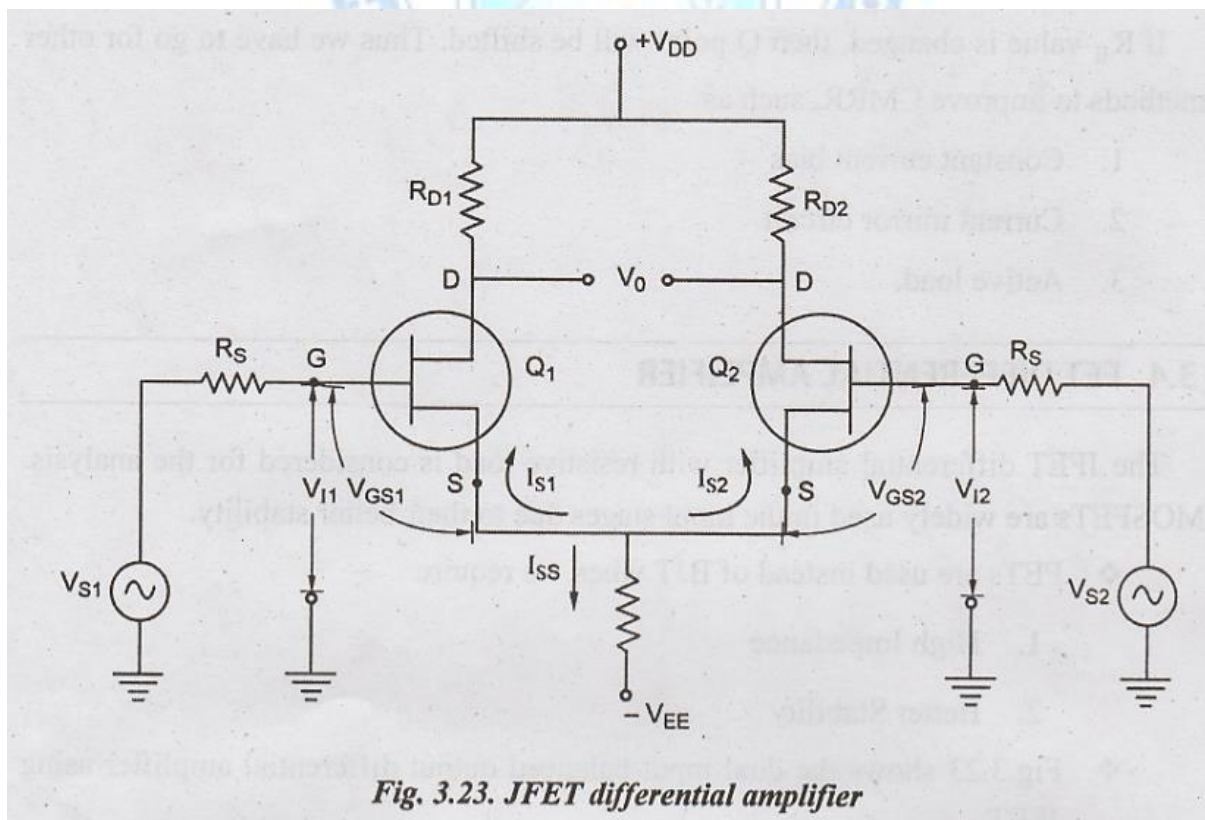

JFET differential amplifier can handle larger input signals than BJT differential amplifier. The drain output voltage is obtained from the Fig.3.23 is

$$\begin{aligned}V_{o1} &= V_{DD} - I_{D1} R_{D1} \\V_{o2} &= V_{DD} - I_{D2} R_{D2}\end{aligned}$$


If  $R_{D1} = R_{D2} = R_D$ , then

$$\begin{aligned}V_{o1} &= V_{DD} - I_{D1} R_D \\V_{o2} &= V_{DD} - I_{D2} R_D\end{aligned}$$

Then the output differential voltage

$$\begin{aligned}V_{OD} &= V_{o1} - V_{o2} \\&= (V_{DD} - I_{D1} R_D) - (V_{DD} - I_{D2} R_D) \\&= -I_{D1} R_D + I_{D2} R_D \\&= R_D (I_{D2} - I_{D1})\end{aligned}$$

For smaller differential input voltage, the transfer function is approximately linear. The transfer characteristics of FET differential amplifier is shown in Fig. 3.24.

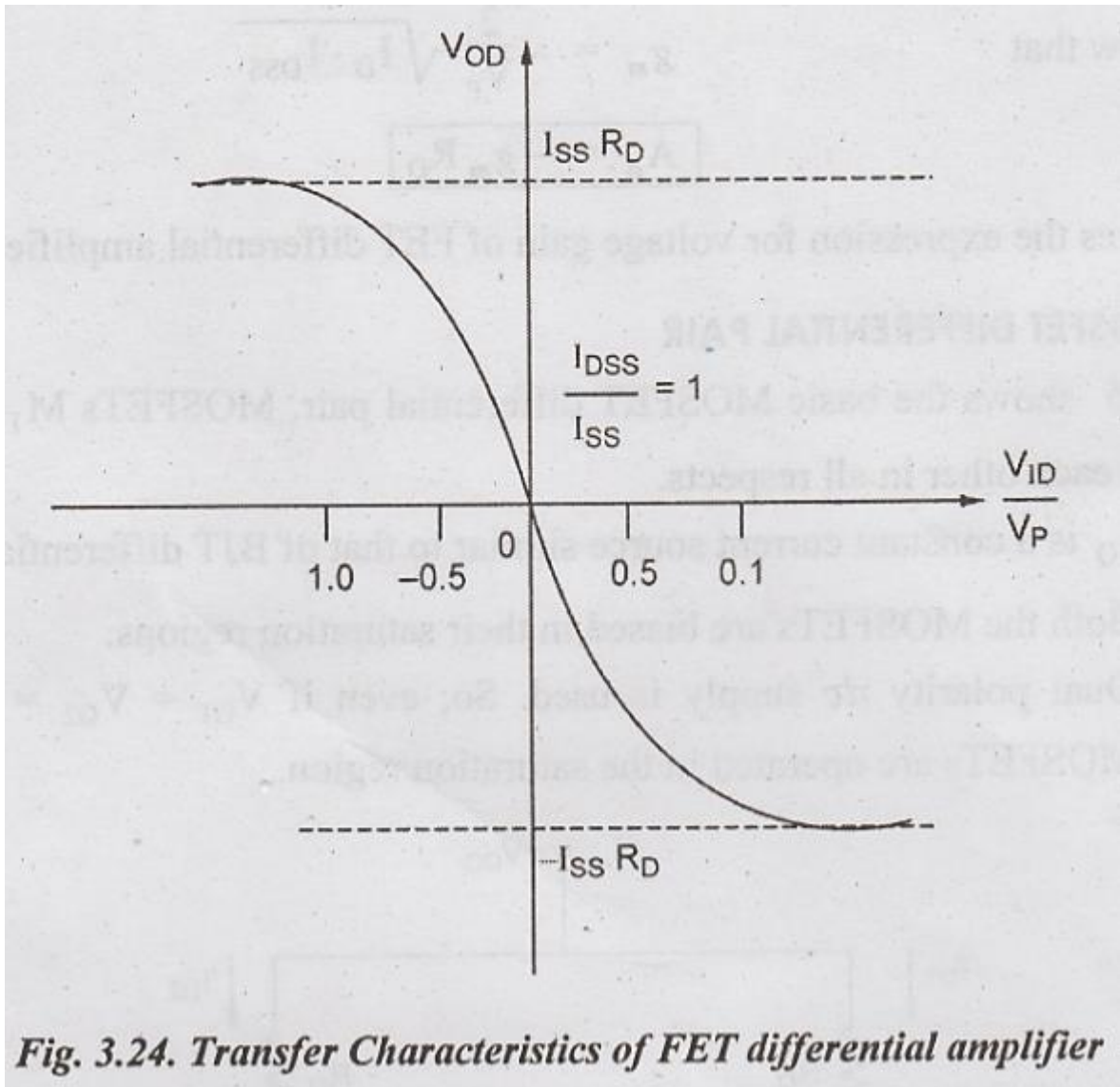

**Fig. 3.24. Transfer Characteristics of FET differential amplifier**

The differential voltage gain is the ratio of differential output voltage to differential input voltage

$$\begin{aligned}
 A_d &= \left. \frac{d V_{OD}}{d V_{ID}} \right|_{V_{ID}=0} \\
 &= \frac{I_{SS} R_D}{V_P} \sqrt{\frac{2 I_{DSS}}{I_{SS}}} \\
 &= \frac{R_D}{V_P} \frac{\sqrt{2 I_{DSS} I_{SS}^2}}{\sqrt{I_{SS}}}
 \end{aligned}$$

$$A_d = \frac{R_D}{V_P} \sqrt{2 I_{DSS} I_{SS}}$$

At  $V_{ID} = 0$ ,  $I_{SS} = 2 I_D$

$$\begin{aligned}
 A_d &= \frac{R_D}{V_P} \sqrt{2 I_{DSS} \cdot 2 I_D} \\
 &= \frac{2 R_D}{V_P} \sqrt{I_D \cdot I_{DSS}}
 \end{aligned}$$

We know that  $g_m = -\frac{2}{V_P} \sqrt{I_D \cdot I_{DSS}}$

$$A_d = -g_m R_D$$

This gives the expression for voltage gain of FET differential amplifier.