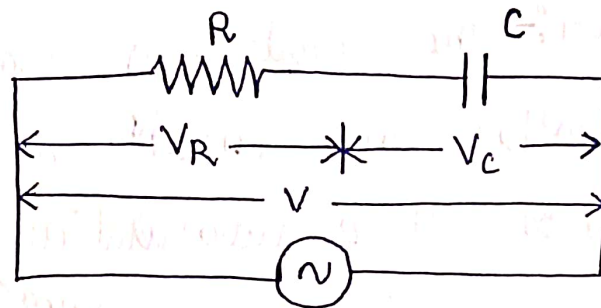


Resistance - Capacitance (R-C) series circuit

A circuit that contains pure resistance R connected in series with a pure capacitor of capacitance C farads is known as

RC series circuit. A sinusoidal voltage is applied and current I flows through the circuit




$$V = V_m \sin \omega t$$

where, V_R = Voltage across the resistance R

V_C = Voltage across capacitor C .

V = Total voltage across RC series ckt

Phasor diagram:-

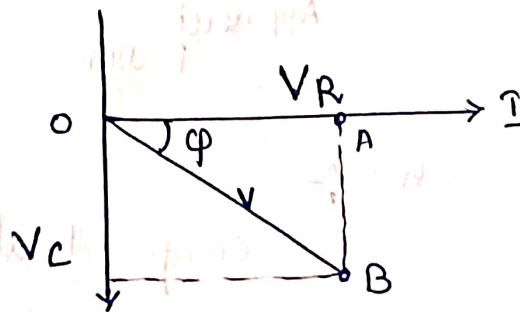

- + Take the current I (rms value) as a reference vector
- * Voltage drop in resistance $V = IR$ is inphase with current.

(25)

Voltage drop in capacitor is 90° behind the current
 In the OAB

$$V^2 = (V_R)^2 + (V_C)^2$$

$$V = \sqrt{(V_R)^2 + (V_C)^2}$$

$$= \sqrt{(IR)^2 + (IX_C)^2}$$

$$= I \sqrt{R^2 + (X_C)^2}$$

$$V = I Z$$

$$I = \frac{V}{Z}$$

Phase angle :-

The current leads the voltage by an angle ϕ . This angle is called phase angle.

$$\tan \phi = \frac{V_C}{V_R} = \frac{I X_C}{I R}$$

$$\phi = \tan^{-1} \left(\frac{X_C}{R} \right)$$

Let $V = V_m \sin(\omega t)$ be the instantaneous voltage

$I = I_m \sin(\omega t + \phi)$ be the instantaneous current

Instantaneous power is

$$P = V_m \sin \omega t \cdot I_m \sin(\omega t + \phi)$$

$$= V_m I_m \sin \omega t \sin(\omega t + \phi)$$

$$= \frac{V_m I_m}{2} [\cos(-\phi) - \cos(2\omega t + \phi)]$$

$$= \frac{V_m I_m}{2} [\cos\phi - \cos(2\omega t + \phi)]$$

Average power is

$$= \text{avg} \left[\frac{V_m I_m}{2} \cos\phi - \frac{V_m I_m}{2} \cos(2\omega t + \phi) \right] \rightarrow 0$$

$$P_{\text{avg}} = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos\phi$$

$$P = VI \cos\phi$$

active power $\rightarrow$ power factor.


$$= VI \times \frac{V_R}{V}$$

$$= VI \times \frac{IR}{IZ}$$

$$= I \cancel{I} \cdot \frac{R}{\cancel{I}}$$

$$P_{\text{avg}} = I^2 R$$


waveform & power curve.

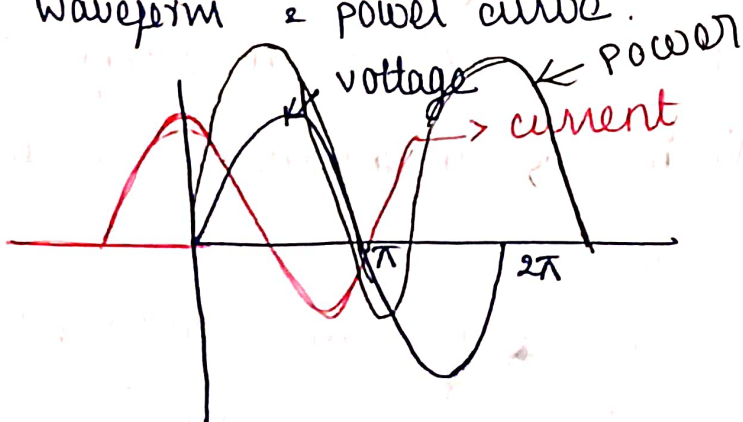

(27)


The power is negative between $(180^\circ - \phi)$ & $(360^\circ - \phi)$ & 360° , rest of the cycle the power is positive

Impedance triangle

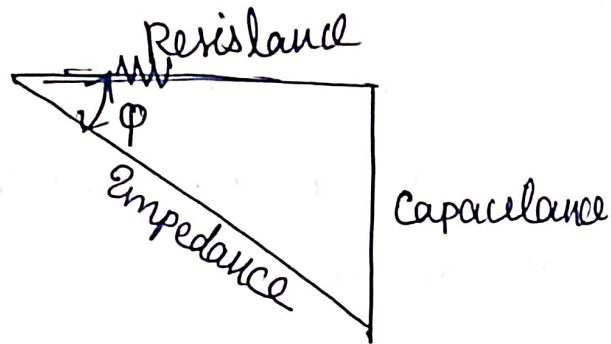

RLC series circuit

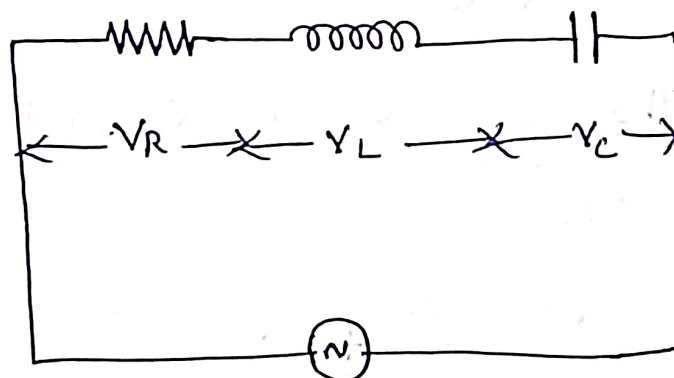When a pure resistor, inductor and capacitor are connected in series it is called a RLC series circuit. The current flowing through each element will be the same.



$$V = V_m \sin \omega t$$


In the circuit, $X_L = 2\pi fL$ and $X_C = \frac{1}{2\pi fC}$

$V_R = IR$ Voltage across resistor & is in phase with $\underline{I}$
 $V_L = IX_L$ Voltage across inductor L & it leads the current by 90° .

V_C is voltage across the capacitor & it lags the current by 90° .

Phasor diagram:

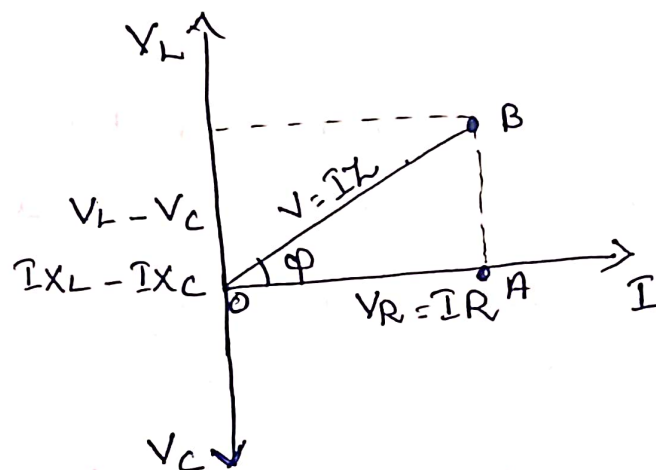The phasor diagram of the RLC series circuit is shown below. When $V_L > V_C$ the circuit acts as an inductive circuit and if $V_L < V_C$ the circuit will behave as a capacitive circuit.



~~The~~ The two vectors V_L and V_C are opposite to each other.

$$V^2 = V_R^2 + (V_L - V_C)^2$$

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$= \sqrt{I^2 R^2 + (I \cdot X_L - I \cdot X_C)^2}$$

$$V = I \sqrt{R^2 + (X_L - X_C)^2}$$

$$I = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$I = \frac{V}{Z}$$

Phase angle

From phasor diagram

$$\begin{aligned} \tan \phi &= \frac{V_L - V_C}{V_R} \\ &= \frac{IX_L - IX_C}{IR} \\ &= \frac{X_L - X_C}{R} \end{aligned}$$

$$\phi = \tan^{-1} \frac{X_L - X_C}{R}$$

Power in RLC series circuit

The product of current & voltage is power

$$P = VI \cos \phi$$

$$P = I^2 R$$

When $X_L > X_C$ $\phi = +ve$ circuit acts as series RL ckt

$X_L < X_C$ $\phi = -ve$ circuit acts as a RC ckt.

$X_L = X_C$ $\phi = 0$ circuit acts as a pure resistive circuit.

(30)

A coil having resistance of 6Ω and inductance of $0.03H$ is connected across $100V, 50Hz$ supply. Calculate i) the current 2) phase angle b/w I and V , c) power factor d) power.

soln

current $I = \frac{V}{Z}$

$$= \frac{V}{\sqrt{X_L^2 + R^2}}$$

$$= \frac{100}{\sqrt{88.73 + 36}}$$

$$= \frac{100}{\sqrt{124.7}}$$

$$= \frac{100}{11.16}$$


$$\boxed{I = 8.96 A}$$

Phase angle $\phi = \tan^{-1} \frac{X_L}{R}$

$$= \tan^{-1} \left(\frac{9.42}{6} \right)$$

$$= \tan^{-1} (1.57)$$
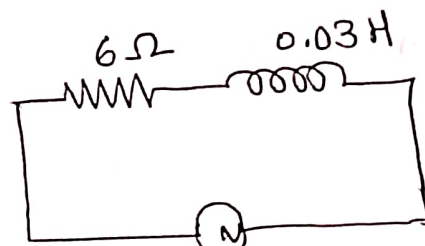
$$\boxed{\phi = 57.3^\circ \text{ lag}}$$



$$X_L = \omega L = 2\pi f \times L$$

$$X_L = 2 \times \pi \times 50 \times 0.03$$

$$= 9.42$$

$$\text{Power} = |V| |I| \cos \phi$$

$$= 100 \times 8.96 \times 0.537$$

$$= 481 \text{ watts.}$$

Power factor $\cos \phi = \cos 57.3$

$$= 0.537$$

In an ac circuit the applied voltage is given by $V = 200 \sin 314t$ and the expression for the leading current is given by $i = 10 \cos 314t$. Find the circuit current and find power factor of the circuit. Draw the phasor diagram.

Soln

$$V = 200 \sin 314t$$

$$i = 10 \cos 314t$$

power factor

$$\cos \phi = \cos 90^\circ = 0$$

$$\left. \begin{aligned} i &= 10 \cos 314t \\ &= 10 \sin(314t + \pi/2) \\ &= I_m \sin(\omega t + \pi/2) \end{aligned} \right\} \begin{aligned} V &= 200 \sin 314t \\ &\quad \downarrow \quad \downarrow \\ &\quad V_m \sin \omega t \end{aligned}$$

$$I_m = 10$$

$$\omega = 314$$


$$V_m = 200$$

$$X_c = \frac{V_m}{I_m} = \frac{200}{10}$$

$$X_c = 20 \Omega$$

$$\frac{1}{C\omega} = 20$$
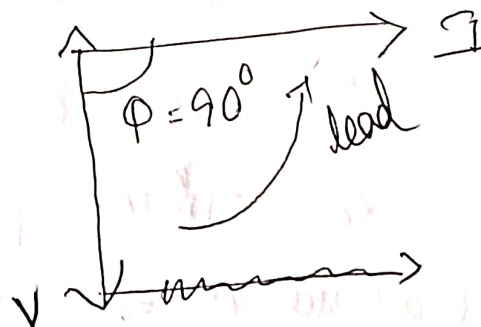
$$C = \frac{1}{\omega \times 20} = \frac{1}{314 \times 20} = 159 \mu F$$



$$V = \frac{V_m}{\sqrt{2}}$$

$$V = 141.4 \text{ V}$$

$$I = \frac{I_m}{\sqrt{2}}$$

$$I = 7.07 \text{ A}$$

③ A Capacitor having a capacitance of $10\mu\text{F}$ is connected in series with non-inductive resistance of 120Ω across $100\text{V}, 50\text{Hz}$. Calculate current, power, phase difference b/w V & I .

Soln

$$I = \frac{V}{Z} = \frac{100}{\sqrt{X_C^2 + R^2}}$$


$$= \frac{100}{\sqrt{318^2 + (120)^2}}$$

$$= \frac{100}{\sqrt{101124 + 14400}}$$

$$X_C = \frac{1}{C\omega}$$

$$= \frac{1}{10 \times 10^{-6} \times 2\pi \times 50} = \frac{10^6}{3140} = 318\Omega$$
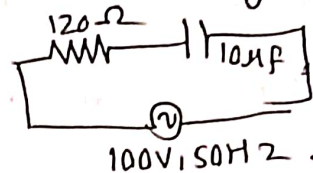
$$= \frac{100}{\sqrt{115524}} = \frac{100}{339.8} = 0.294\text{ A}$$



$$I = 0.294\text{ A}$$

$$\text{Power} = VI \cos \phi$$

$$= 100 \times 0.29 \times \cos 69.3$$

$$=$$

$$P = 10.4\text{ watts}$$

$$\phi = \tan^{-1} \left(\frac{X_C}{R} \right)$$

$$= \tan^{-1} \left(\frac{318}{120} \right)$$

$$= \tan^{-1} (2.65)$$

$$\phi = 69.3^\circ$$

A coil of $R=10\Omega$, $L=0.1\text{H}$, $C=150\mu\text{F}$ are connected across a $200\text{V}, 50\text{Hz}$ supply. Calculate a) X_L b) X_C c) net reactance, d) current e) power factor


$$X_L = \omega L = 2\pi f \times L$$

$$= 2 \times 3.14 \times 50 \times 0.1 = 31.4\Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f \times C} = \frac{1}{2 \times 3.14 \times 50 \times 150 \times 10^{-6}}$$

$$X_C = 21.2\Omega$$

$$X_C = 21\Omega$$

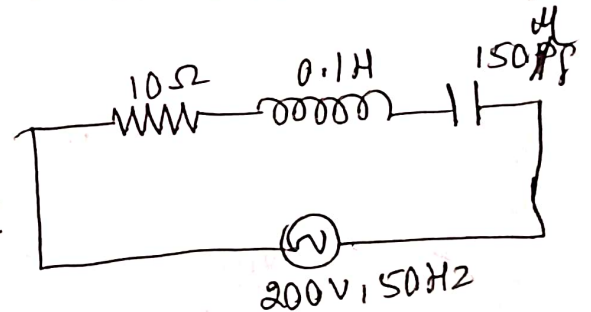

$$\text{Net Reactance is } X = X_L - X_C = 31.4 - 21 = 10.4\Omega$$

$$\text{Current} = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + X^2}} = \frac{200}{\sqrt{10^2 + (10.4)^2}} = \frac{200}{\sqrt{208.16}} = \frac{200}{14.4}$$

$$I = 13.88$$

$$\text{Power Factor, } \cos \phi = 0.7$$

$$\phi = \tan^{-1} \frac{X}{R} = \tan^{-1} \left(\frac{10.4}{10} \right) = 46.12^\circ$$