



ROHINI

COLLEGE OF ENGINEERING & TECHNOLOGY

Approved by AICTE and Affiliated to Anna University (An ISO Certified Institution) | Accredited with A+ Grade by NAAC
Recognized under Section 2(f) of University Grants Commission, UGC ACT 1956

(AUTONOMOUS)

5.6 IC 723 – GENERAL PURPOSE REGULATOR

Disadvantages of fixed voltage regulator:

- Do not have the short circuit
- Output voltage is not adjustable

These limitations can be overcome in IC723.

Features of IC723:

- Unregulated dc supply voltage at the input between 9.5V & 40V
- Adjustable regulated output voltage between 2 to 3V.
- Maximum load current of 150 mA ($I_{Lmax} = 150mA$).
- With the additional transistor used, I_{Lmax} upto 10A is obtainable.
- Positive or Negative supply operation
- Internal Power dissipation of 800mW.
- Built in short circuit protection.
- Very low temperature drift.
- High ripple rejection.

BLOCK DIAGRAM OF IC723

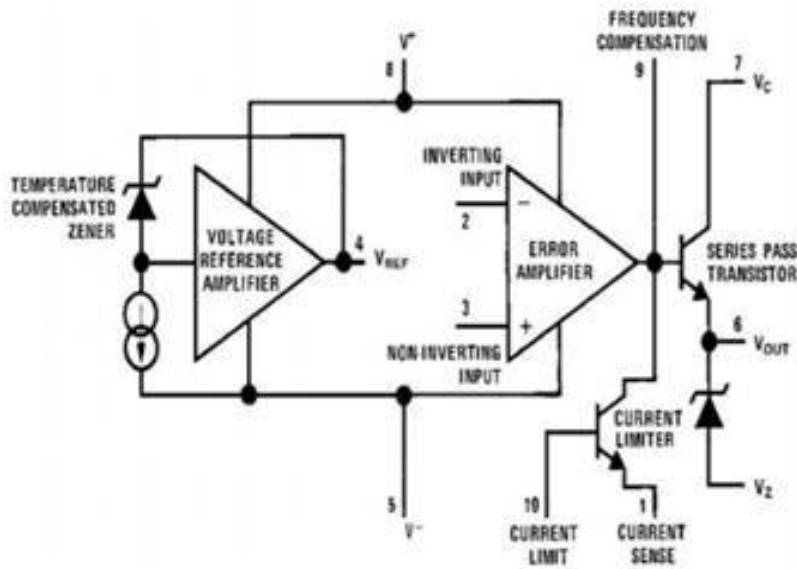


Figure 5.6.1 Functional block diagram of IC723

[source: https://www.brainkart.com/subject/Linear-Integrated-Circuits_220/]

Functional block diagram of IC723 is shown in figure 5.6.1. The simplified functional block diagram can be divided into 4 blocks.

1. Reference Generating block:

The temperature compensated Zener diode, constant current source & voltage reference amplifier together form the reference generating block. The Zener diode is used to generate a fixed reference voltage internally. A constant current source will make the Zener diode to operate at a fixed point & it is applied to the Non – inverting terminal of the error amplifier. The unregulated input voltage $\pm V_{CC}$ is applied to the voltage reference amplifier as well as the error amplifier.

2. Error Amplifier:

The error amplifier is a high gain differential amplifier with 2 inputs (inverting & Noninverting). The Non-inverting terminal is connected to the internally generated reference voltage. The Inverting terminal is connected to the full regulated output voltage.

3. Series Pass Transistor:

Q1 is the internal series pass transistor which is driven by the error amplifier. This transistor actually acts as a variable resistor & regulates the output voltage. The collector of transistor Q1 is connected to the Un-regulated power supply. The maximum collector voltage of Q1 is limited to 36Volts. The maximum current which can be supplied by Q1 is 150mA.

4. Circuitry to limit the current:


The internal transistor Q2 is used for current sensing & limiting. Q2 is normally OFF transistor. It turns ON when the I_L exceeds a predetermined limit. Low voltage, Low current is capable of supplying load voltage which is equal to or between 2 to 7Volts. Pin diagram of IC723 in figure 5.6.2.

$$V_{\text{load}} = 2 \text{ to } 7\text{V and } I_{\text{load}} = 50\text{mA}$$

NC	1	IC 723	14	NC
Current limit	2		13	Frequency compensation
Current sense	3		12	+Vcc
Inverting Input	4		11	Vc
Non-Inverting Input	5		10	Vo
Vref	6		9	Vz
-Vcc	7		8	NC

Figure 5.6.2. Pin diagram of IC723

[source: https://www.brainkart.com/subject/Linear-Integrated-Circuits_220/]

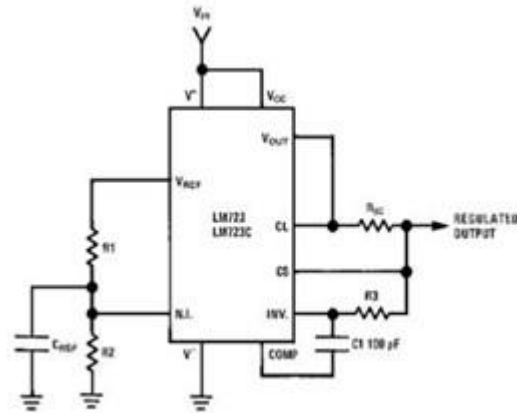IC723 as a LOW voltage LOW current:**Figure 5.6.3. Typical circuit connection diagram**

[source: https://www.brainkart.com/subject/Linear-Integrated-Circuits_220/]

- ✓ Circuit connection is shown in fig 3. R_1 & R_2 form a potential divider between V_{ref} & Gnd.
- ✓ The Voltage across R_2 is connected to the Non – inverting terminal of the regulator

$$V_{non-inv} = \frac{R_2}{(R_1+R_2)} V_{ref}$$

- ✓ Gain of the internal error amplifier is large

$$V_{non-inv} = V_{in}$$

- ✓ Therefore the V_o is connected to the Inverting terminal through R_3 & R_{SC} must also

be equal to $V_{non-inv}$

$$V_o = V_{non-inv} = \frac{R_2}{(R_1+R_2)} V_{ref}$$

R_1 & R_2 can be in the range of 1 K Ω to 10K Ω & value of R_3 is given by

$$R_3 = R_1 || R_2 = \frac{R_1 R_2}{(R_1+R_2)}$$

Rsc (current sensing resistor) is connected between Cs & CL. The voltage drop across Rsc is proportional to the IL.

- ✓ This resistor supplies the output voltage in the range of 2 to 7 volts, but the load current can be higher than 150mA.
 - ✓ The current sourcing capacity is increased by including a transistor Q in the circuit.
- The output voltage , $V_o = R_2 / (R_1 + R_2) V_{ref}$

IC723 as a HIGH voltage LOW Current:

- ✓ This circuit is capable of supplying a regulated output voltage between the ranges of 7 to 37 volts with a maximum load current of 150 mA.
- ✓ The Non – inverting terminal is now connected to V_{ref} through resistance R_3 .
- ✓ The value of R_1 & R_2 is adjusted in order to get a voltage of V_{ref} at the inverting terminal at the desired output.

$$V_{in} = V_{ref} = R_2 / (R_1 + R_2) V_o$$

$$V_o = [1 + R_1 / R_2] V_{in}$$

- ✓ Rsc is connected between CL & Cs terminals as before & it provides the shortCircuit current limiting $R_{sc} = 0.6 / I_{limit}$
- ✓ The value of resistors R_3 is given by ,

$$R_3 = R_1 || R_2 = R_1 R_2 / (R_1 + R_2)$$

IC723 as a HIGH voltage HIGH Current:

- ✓ An external transistor Q is added in the circuit for high voltage low current regulator to improve its current sourcing capacity. Circuit connection of IC 723 as a High voltage High current regulator is shown in figure 5.6.4. below

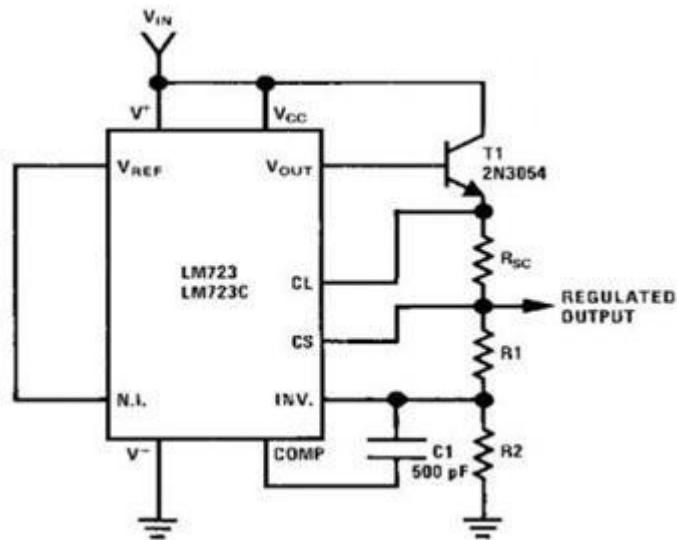


Figure 5.6.4. Circuit connection of IC 723 as a High voltage High current regulator

[source: https://www.brainkart.com/subject/Linear-Integrated-Circuits_220/]

- ✓ For this circuit the output voltage varies between 7 & 37V.
- ✓ Transistor Q increase the current sourcing capacity thus I_L (MAX) is greater than 150mA.
- ✓ The output voltage V_o is given by ,

$$V_o = V_o = [1 + R_1/R_2] V_{in}$$

$$R_{sc} = 0.6/I \text{ limit}$$