

⑥ Dot conversion in mutual Inductance


⑥

Dot conversion is used to find the sign for the mutually induced voltage in coupled circuits.

There are 4 Types of dot conversions

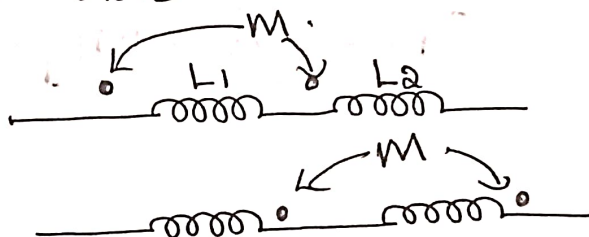1) series aiding

Here the dot is placed either at the entry of the two mutually coupled coils or at the exit.




Equivalent inductance

$$L_{eq} = L_1 + L_2 + 2M$$

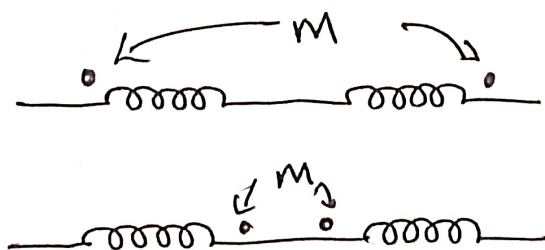2) series opposing

when dots are placed at entry of coil 1 and exit of coil 2 and vice versa.




$$L_{eq} = L_1 + L_2 - 2M$$

⑦

Parallel Aiding

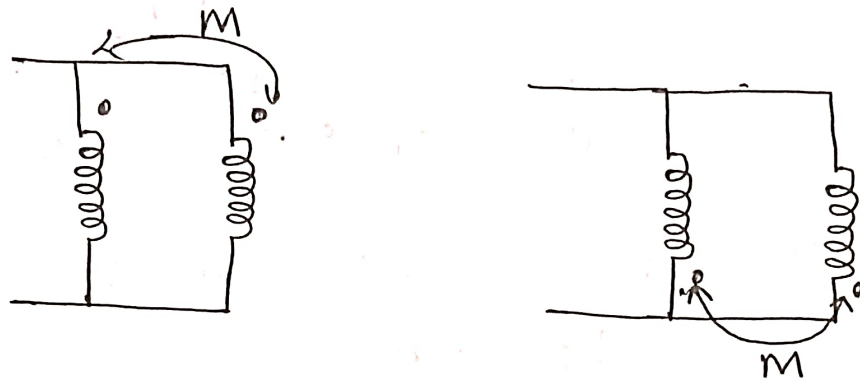
When the coils are connected in parallel and the dots are placed either at entry (or) at the exit of the coil.



$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$

Parallel opposing.

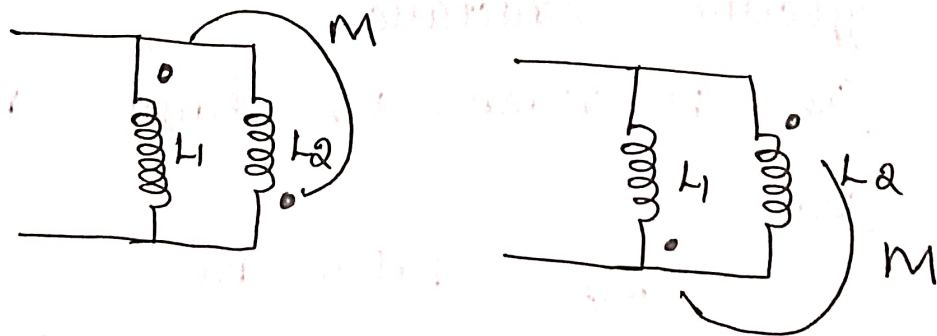
When the coils are connected parallelly and the dots are placed at entry of coil and at exit, viceversa.



$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$

8

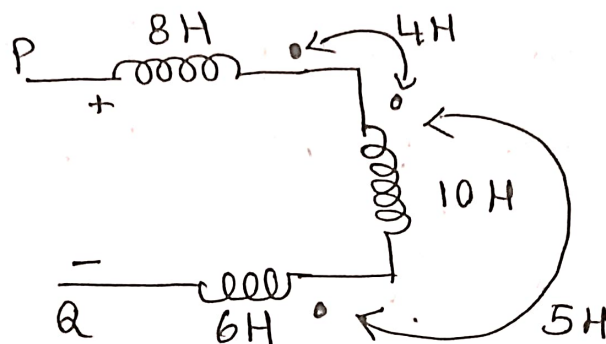- 1) Calculate the equivalent inductance between the terminals P and Q.



Given

$$L_1 = 8H, L_2 = 10H, L_3 = 6H, L_{12} = 4H, L_{23} = 5H.$$

$$L_{eq} = L_1 + L_2 + L_3 - 2L_{12} + 2L_{23}$$

$$= 8 + 10 + 6 - (2 \times 4) + 2(5)$$

$$L_{eq} = 26H$$

- 2) Two inductors with self inductance 75mH and 55mH connected in parallel aiding. The mutual inductance is given by 22.5mH. Find the effective inductance.

Given $L_1 = 75mH, L_2 = 55mH, M = 22.5mH.$


soln

$$L_{eff} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} = \frac{75 \times 55 - (22.5)^2}{75 + 55 - 2(22.5)}$$

$$L_{eff} = 42.6mH$$

(9)

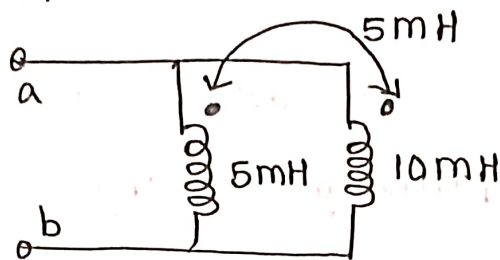3) Find the equivalent inductance of the circuit given



Soln

$$L_1 = 5\text{mH}, L_2 = 10\text{mH}, M = 5\text{mH}$$


$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} = \frac{5 \times 10^{-3} \times 10 \times 10^{-3} - (5 \times 10^{-3})^2}{5 \times 10^{-3} + 10 \times 10^{-3} - 2 \times 5 \times 10^{-3}}$$

$$= \frac{50 \times 10^{-6} - 25 \times 10^{-6}}{25 \times 10^{-3}} = \frac{(50 - 25) \times 10^{-6}}{25 \times 10^{-3}}$$

$$= \frac{10^{-6} [50 \times 10^3 - 25]}{25 \times 10^{-3}} = \frac{25 \times 10^{-3}}{25}$$

$$L_{eq} = 1\text{mH}$$

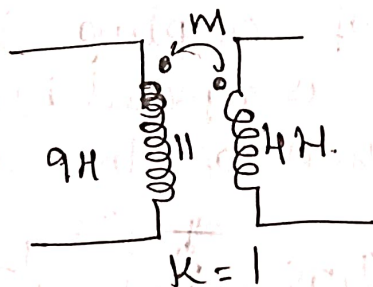4) Find the mutual inductance of the circuit given



$$M = K \sqrt{L_1 L_2}$$

$$= 1 \sqrt{9 \times 4}$$

$$M = 6\text{H}$$