
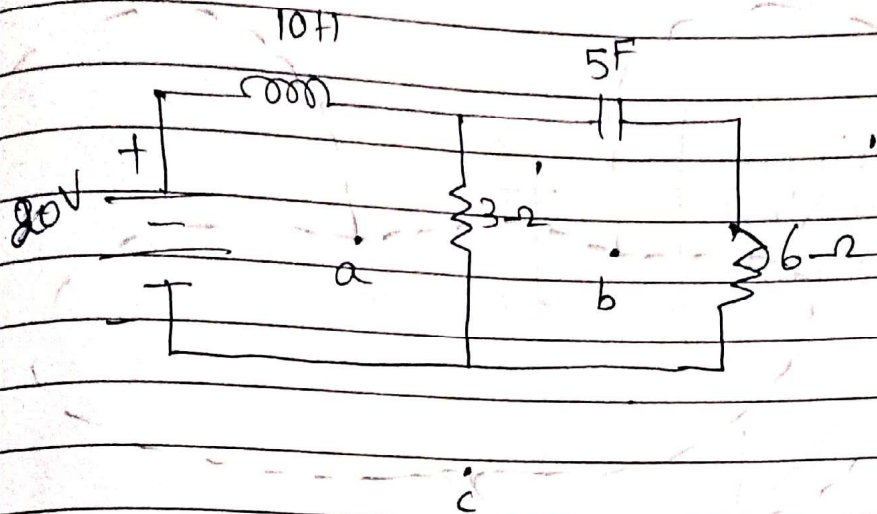


② Draw the dual n/w for given n/w.

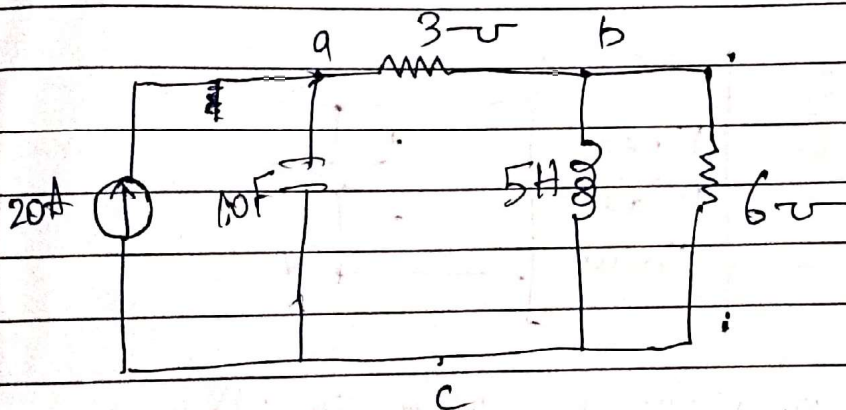

Dual N/w



Reciprocity Theorem




* In a linear bilateral circuit a voltage source V volt in a branch gives the current I in another branch.

* The ratio of voltage (V) to current (I) remains constant when the position of V & I are interchanged.

* The ratio (V/I) is called transfer resistance.

* The circuit which satisfies reciprocity theorem

is called Reciprocal Circuit

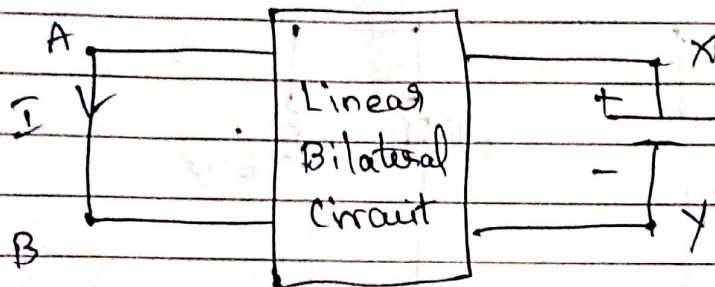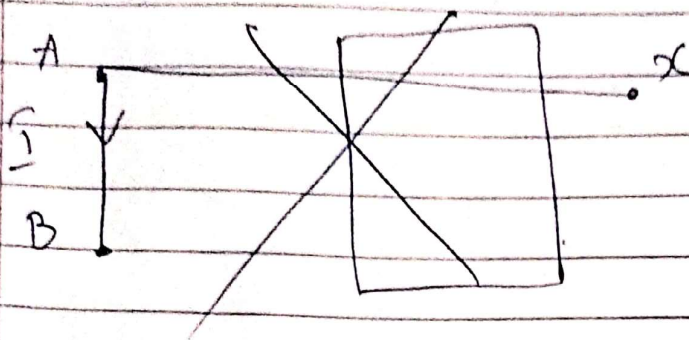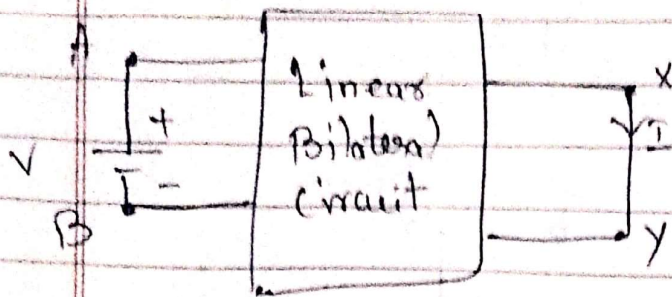


Representation of reciprocity theorem.

Steps to be followed to apply Reciprocity theorem

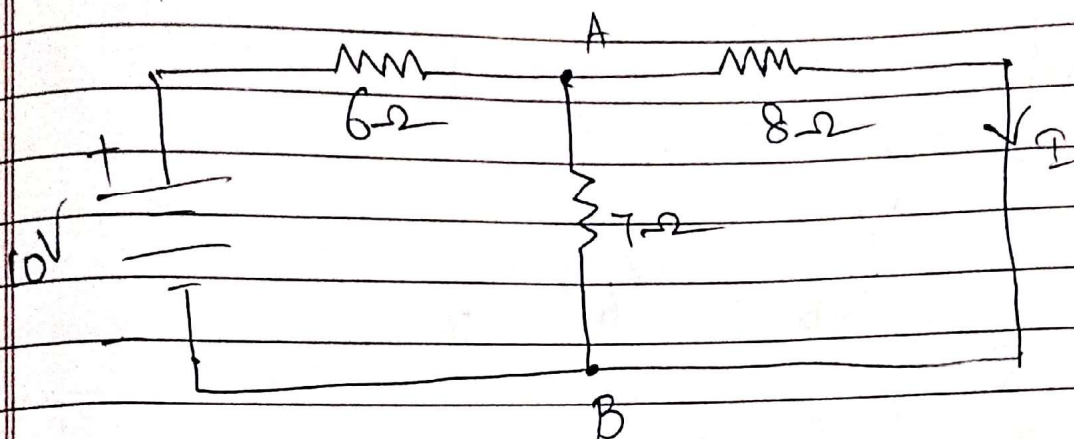- (1) Identify the source & the load, in the given circuit.
- (2) Find the current flowing through the load by using any of the n/w reduction techniques.
- (3) Interchange the position of source & load.
- (4) Find the current flowing through the load.

⑤ Verify the ratio (V/I) in both cases.
It will be the same.

Proof of Reciprocity Theorem with an example circuit



$$R_{AB} \Rightarrow 7 \parallel 8 \quad \frac{1}{R_{AB}} = \frac{1}{7} + \frac{1}{8}$$

$$R_{AB} = 3.73 \Omega \quad \frac{1}{R_{AB}} = \frac{15}{56} \Rightarrow R_{AB} = \frac{56}{15}$$

$$R_{eq} = 6 + R_{AB} = 9.73 \Omega$$

$$\text{Current } \frac{I}{I_T} = \frac{10}{R_{eq}} = \frac{10}{9.73} = 1.028 \text{ A}$$

Applying current division at node A,


$$\text{Current } \frac{I}{I_T} = \frac{I_T \times 7}{8 + 7} = \frac{1.028 \times 7}{15}$$

$$I = 0.48 \text{ A}$$

$$\text{ratio } V/I = 10 / 0.48 = 20.83 \Omega$$

(Transfer resistance)

Interchanging source & load.

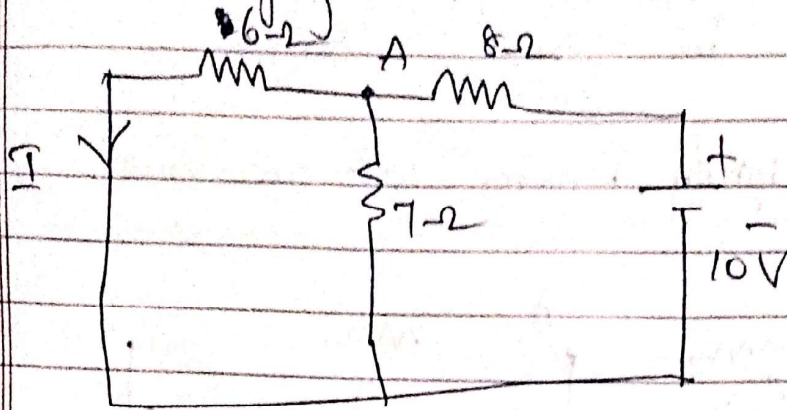

$$\frac{1}{R_{AB}} = \frac{1}{6} + \frac{1}{7}$$

$$R_{AB} = 3.23 \Omega$$

$$R_{eq} = 3.23 + 8 = 11.23 \Omega$$

$$I_1 = \frac{10}{11.23} = 0.89 \text{ A}$$

Applying current division at A -

$$I_6 = I = \frac{0.89 \times 7}{6 + 7}$$

$$= \frac{0.89 \times 7}{13}$$

$$I = 0.48 \text{ A}$$

$$\therefore \text{The ratio } \left(\frac{V}{I} \right) = \frac{10}{0.48} = 20.83 \Omega$$

⇒ Transfer Resistance


Thus, the ratio is found to be same in both cases & hence reciprocity theorem is proved.

Limitations

- ① This theorem cannot be applicable for circuits having more than one source.
- ② This theorem will not be suitable for circuits having time-varying elements.
- ③ This theorem will be satisfied only for circuits which does not have dependent sources.

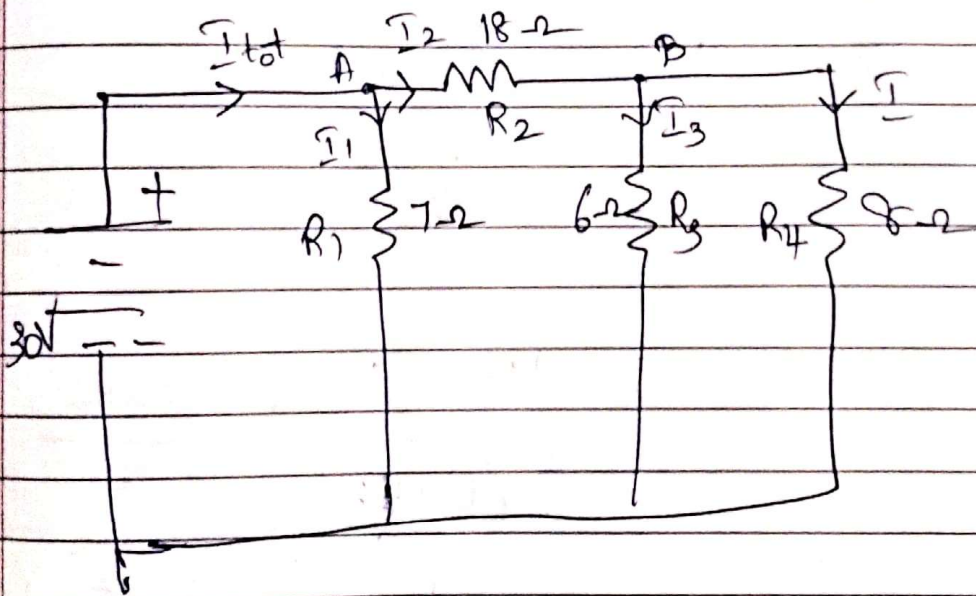Example

In the Nth shown in figure, find the current in the 8Ω resistor, verify the reciprocity theorem.



To Find the Equivalent resistance,

$$R_{eq}' = (8 \parallel 6 + 18) \parallel 7$$

$$= \left[\left(\frac{6 \times 8}{6+8} \right) + 18 \right] \parallel 7 = 5.28\Omega$$

$$I_{tot}' = \frac{V}{R_{eq}'} = \frac{30}{5.28} = 5.68 \text{ A}$$

Applying Current division technique at node A

$$I_2' = \frac{I_{tot}' \times R_1}{R_1 + R_{234}}$$

$$= \frac{5.68 \times 7}{7 + 21.43}$$

$$I_2' = 1.4 \text{ A}$$


Applying current division technique at node B

$$I = \frac{I_2' \times R_3}{R_3 + R_4}$$

$$= \frac{1.4 \times 6}{(6 + 8)} = \frac{1.4 \times 6}{14}$$

$$I = 0.6 \text{ A}$$

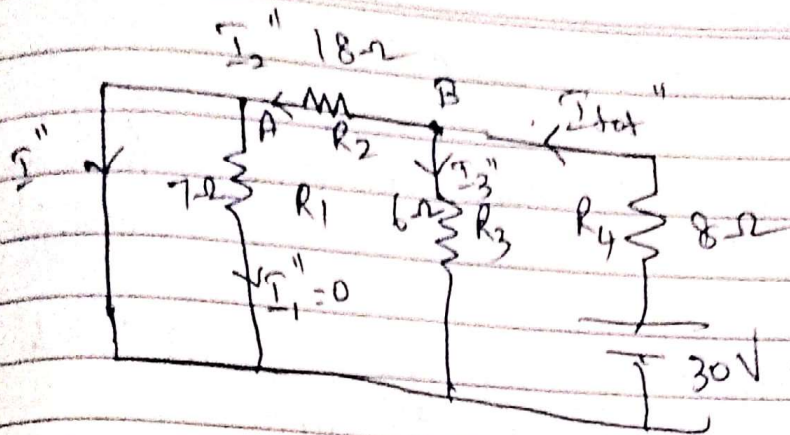On changing the 30V voltage source to the 8Ω resistor branch, circuit will be changed as follows,



As 7Ω resistor (R_1) is short circuited it cannot be considered for calculating I_1 .

$$\therefore I_1 = I_2$$

Now,

R_2 & R_3 are connected in 11^{st}

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{18} + \frac{1}{6}$$

$$R_{23} = 4.5\Omega$$

Total Current,

$$I_{\text{tot}} = \frac{V}{R_{23} + R_4}$$

$$= \frac{30}{4.5 + 8}$$

[Series Connection]

$$= \frac{30}{12.5}$$

$$I_{\text{tot}} = 2.4\text{A}$$

Apply current division technique at node 'B'

$$I_2 = I_{\text{tot}} \times \frac{R_3}{(R_2 + R_3)}$$

$$= 2.4 \times 6$$


$$(18 + 6)$$

$$I_2'' = I_L'' = 0.6A$$

$I_L' = I_L'' \Rightarrow$ Thus, reciprocity theorem is verified.

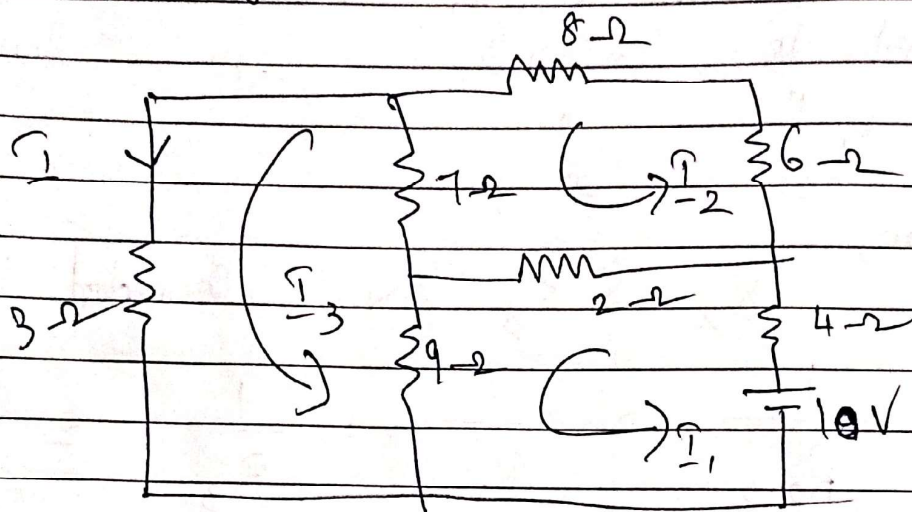Example

In the circuit of figure, find I & verify reciprocity theorem.



In matrix form,

$$[R][I] = [V]$$

$$\begin{bmatrix} 15 & -2 & -9 \\ -2 & 23 & -7 \\ -9 & -7 & 19 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix}$$


$$\Delta = \begin{vmatrix} 15 & -2 & -9 \\ -2 & 23 & -7 \\ -9 & -7 & 19 \end{vmatrix} = 3629$$

$$\Delta_3 = \begin{bmatrix} 15 & -2 & 10 \\ -2 & 23 & 0 \\ -9 & -7 & 0 \end{bmatrix} = 2210$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{2210}{3629}$$

$$I_3 = I' = 0.61A \quad \text{--- (1)}$$

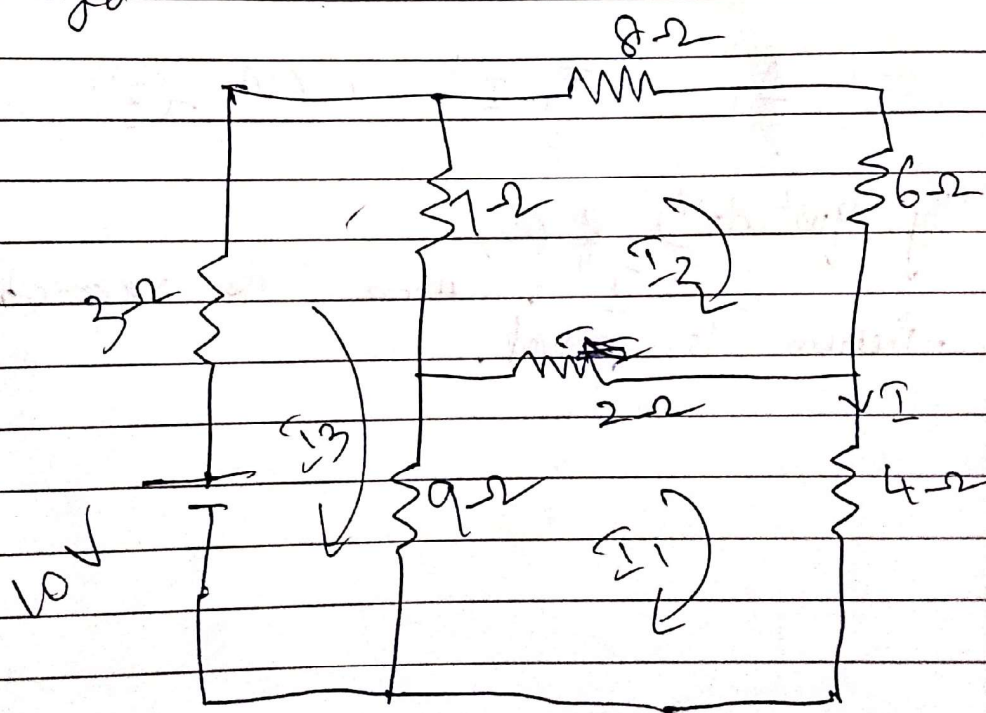On changing the 10V battery source to the 3-2 resistor branch, circuit will be changed.



In matrix form,

$$[R][I] = [V]$$

$$\begin{bmatrix} 15 & -2 & -9 \\ -2 & 23 & -7 \\ -9 & -7 & 19 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 10 \end{bmatrix}$$

$$\Delta_2 = \begin{vmatrix} 15 & -2 & -9 \\ -2 & 23 & -7 \\ -9 & -7 & 19 \end{vmatrix} = 3629$$

$$\Delta_1 = \begin{vmatrix} 0 & -2 & -9 \\ 0 & 23 & -7 \\ 10 & -7 & 19 \end{vmatrix} = 2210$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{2210}{3629}$$

$$\Delta_1 = I_1 = I'' = 0.61A \quad \text{--- (2)}$$


By equation (1) & (2)

$I' = I''$ Hence the reciprocity theorem is proved.

Star-Delta Transformations


In some of the circuits, there won't be series (or) parallel combination of resistors. In that case to reduce the complexity of a circuit another useful technique called (Δ -Y) (Delta-Wye) conversion is used.

Delta Conversion (Δ Connection).

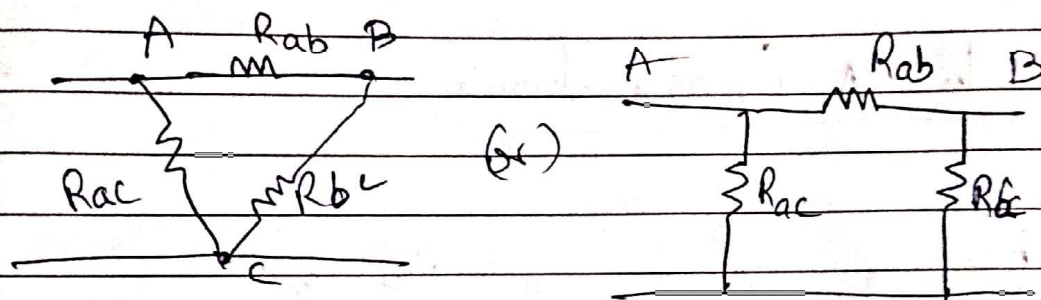


Delta circuit.

Star Connection (γ Connection)

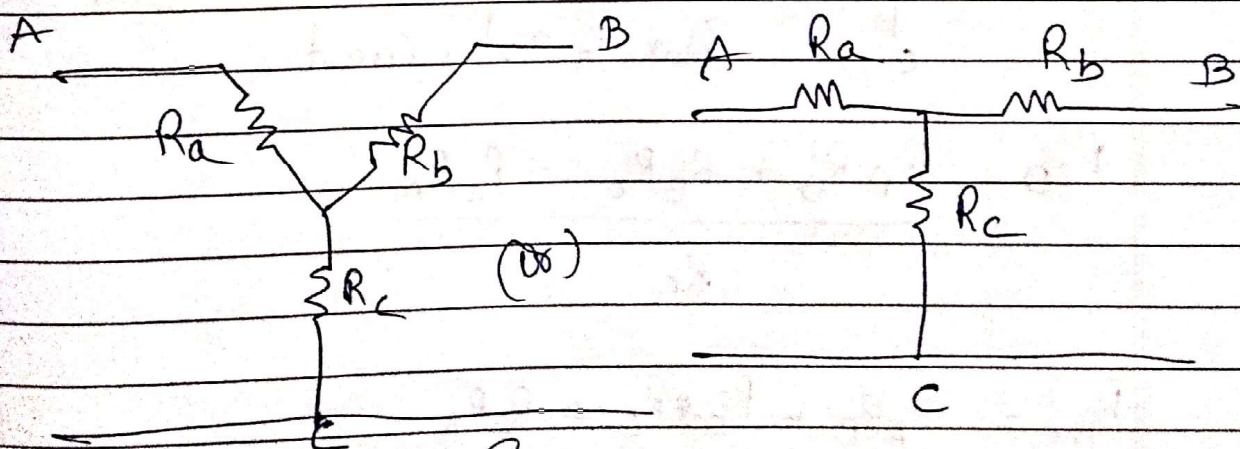

Star circuit.

Δ to γ Conversion Formula

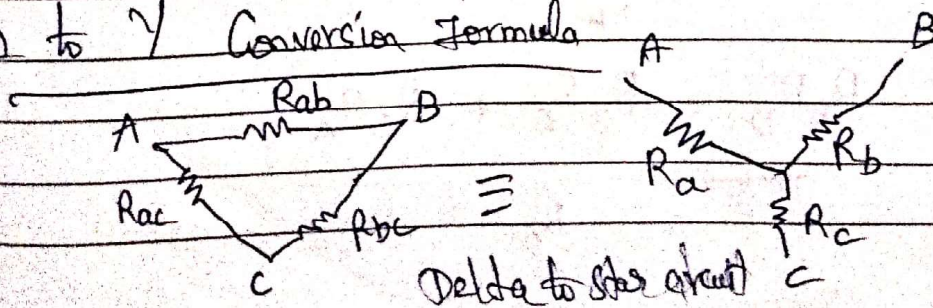


Delta to Star circuit

$$R_a = \frac{R_{ab} R_{ac}}{R_{ab} + R_{ac} + R_{bc}}$$

$$R_b = \frac{R_{ab} R_{bc}}{R_{ab} + R_{bc} + R_{ac}}$$

$$R_c = \frac{R_{ac} R_{bc}}{R_{ab} + R_{bc} + R_{ac}}$$

Y to Δ Conversion Formula

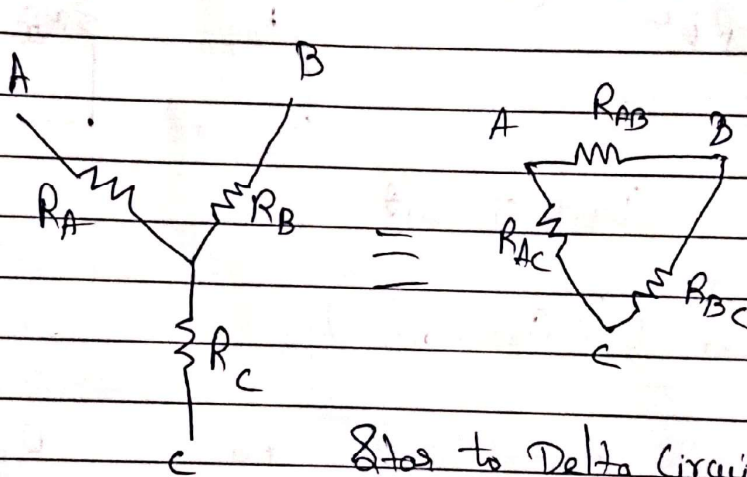

Star to Delta Circuit


$$R_{AB} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_C}$$

$$R_{BC} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_A}$$

$$R_{AC} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_B}$$


Problems based on Δ -Y Conversion

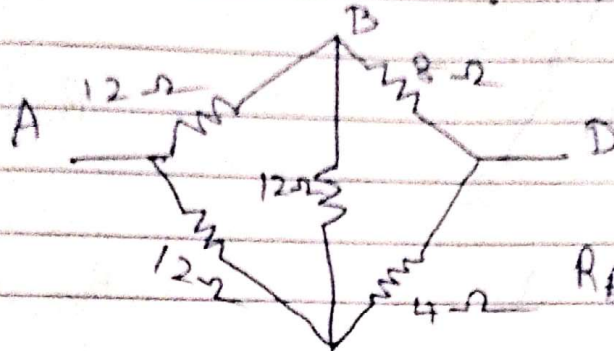Example ① Calculate the R_{eq} (Equivalent Resistance) between A & D.



$$R_{AB} = R_{BC} = R_{AC} = 12\ \Omega$$

Step 1: $\Delta ABC \Rightarrow Y ABC$

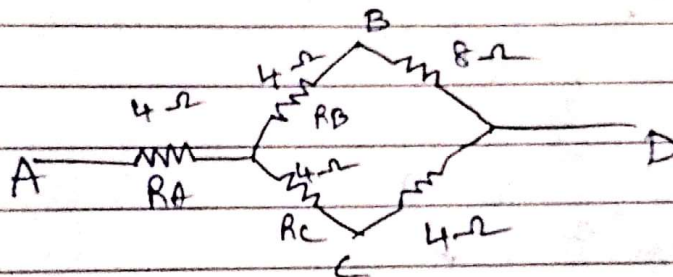

$$R_A = \frac{12 \times 12}{12 + 12 + 12}$$

$$= \frac{144}{36} = 4\ \Omega$$

$$= \frac{144}{36} = 4\ \Omega$$

$$R_B = 4\ \Omega$$


$$R_C = 4\ \Omega$$

Step 2: Since $8\ \Omega$ and $4\ \Omega$ are in series,

$$\therefore R_{eq1} = 8 + 4 = 12\ \Omega$$

|| $4\ \Omega$ & $4\ \Omega$ are in series -

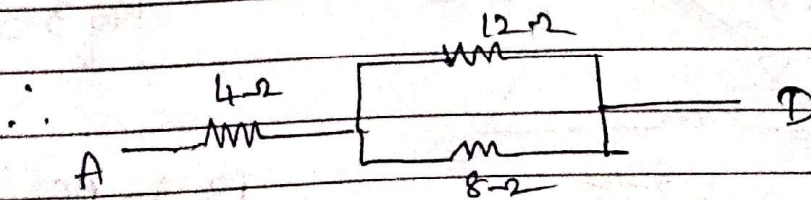
$$\therefore R_{eq2} = 4 + 4 = 8\ \Omega$$



$$12 \parallel 8 \Rightarrow \frac{12 \times 8}{12 + 8} = 4.8\ \Omega$$

$$R_{eq} = 4.8 + 4 = 8.8\ \Omega //$$

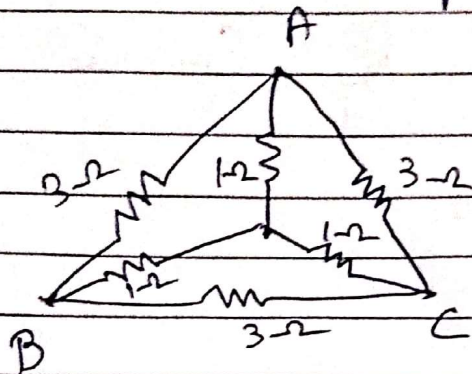Example: Find R_{eq} between terminal B & C




$$R_{AB} = R_A + R_B + \frac{R_A R_C + R_C}{R_C}$$

$$R_{AB} = \frac{12 \times 12}{12 + 12} = 3\Omega$$

$$R_{BC} = R_C = 3\Omega$$

Step 1: Δ to Δ

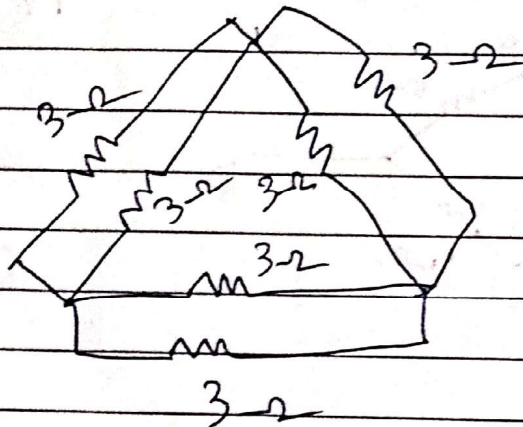


Step 2: Since 3Ω & 3Ω are in parallel,


$$R_{eq1} = \frac{3 \times 3}{3 + 3} = \frac{9}{6} = 1.5\Omega$$

$$R_{eq2} = 1.5\Omega$$

$$R_{eq3} = 1.5\Omega$$

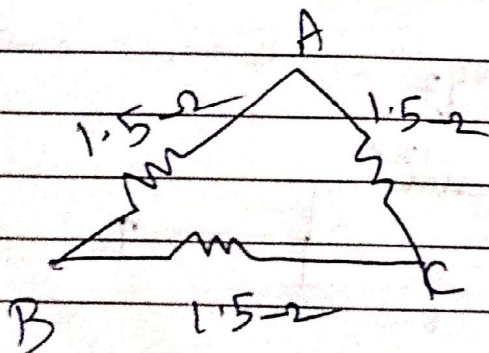

AB & AC are in series

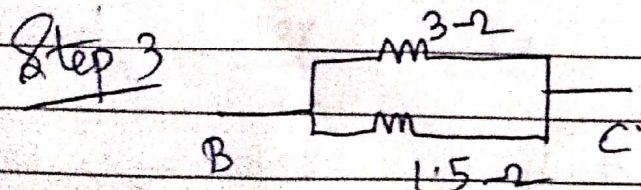

and BC is


$$1.5 + 1.5 = 3\Omega$$

$$R_{eq} = R \frac{3 \times 1.5}{3 + 1.5} = \frac{4.5}{4.5} = 1 \Omega$$


$$R_{eq} = 1 \Omega$$

Maximum Power Transfer Example

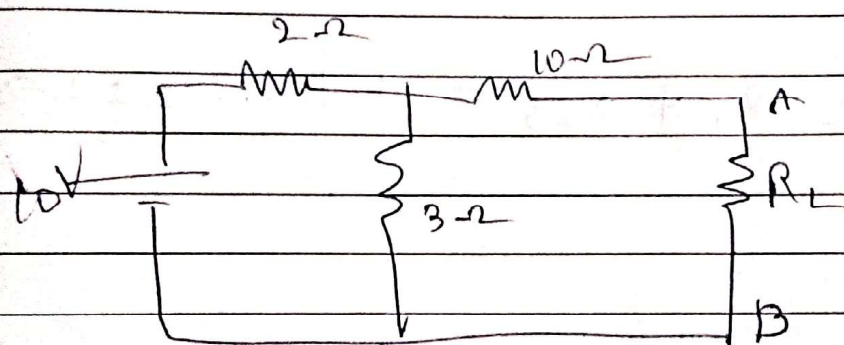Find the value of R_L at which maximum power is transferred to R_L & hence the maximum power transferred to R_L



Find V_{th} .

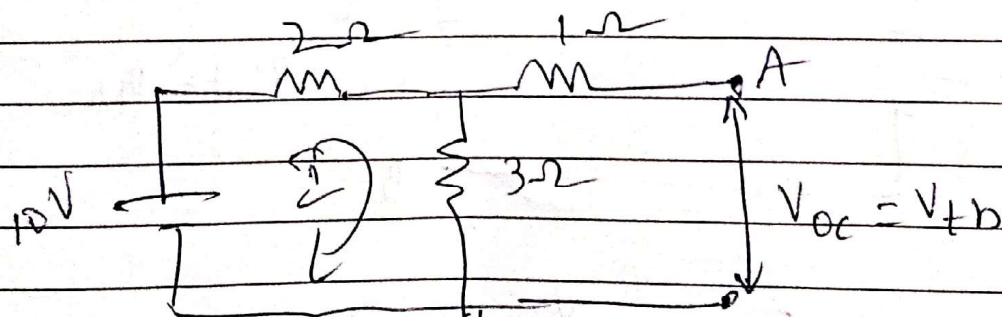

$$I = \frac{10}{2 + 3} = 2A = I_{2\Omega} = I_{3\Omega}$$

$$V_{oc} = V_{th} = V_{1\Omega} + V_{3\Omega}$$

Series


But Connection

$$V_{1\Omega} = 0, I_{1\Omega} = 0$$

$$I_{2\Omega} = 2A$$

$$= V_{3\Omega} = (I_{3\Omega} \times 3) = V_{th} = 2 \times 3 = 6V$$

To find R_{th}

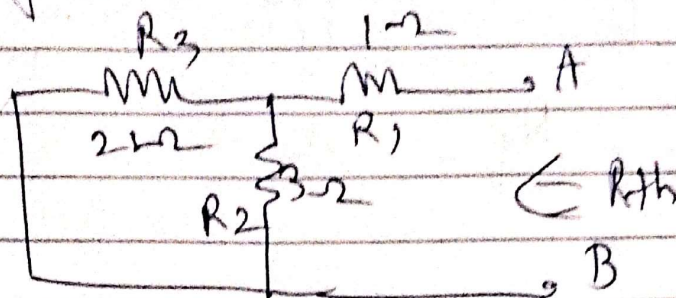


R_2 & R_3 are in $||$

$$\text{So } \frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3} \quad \frac{2}{2} + \frac{1}{3}$$

$$R_{23} = 1.2 \Omega$$

$$R_{th} = R_1 + R_{23} = 1 + 1.2 = 2.2 \Omega$$

For $R_L = R_{th}$

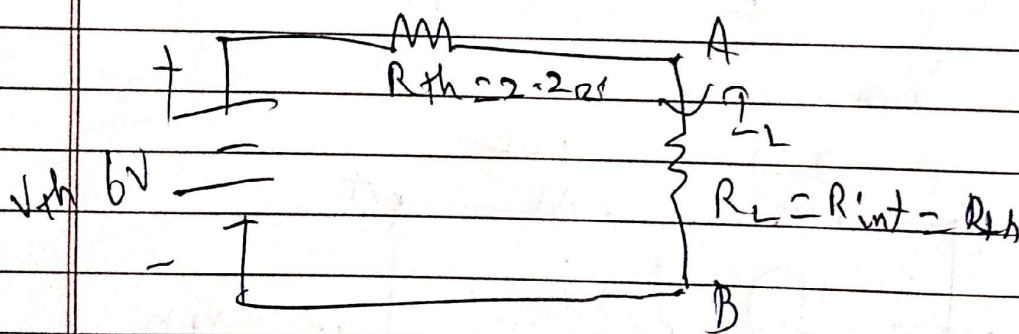

$$\Rightarrow I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{V_{th}}{2R_{th}} = \frac{6}{2 \times 2.2}$$

$$I_L = 1.36 \text{ A}$$

$$\text{Max Power at } R_L \Rightarrow P_{max} = I_L^2 R_L = (1.36)^2 \times 2.2 = 4.069 \text{ W}$$

(6) Max Power across $R_L = (I_L)^2 R_L$

$$P_L = \frac{(V_{th})^2}{4R_{th}}$$

$$= \frac{6^2}{4 \times 2.2}$$

$$= \frac{36}{8.8}$$

$$P_L = 4.09 \text{ Watts}$$