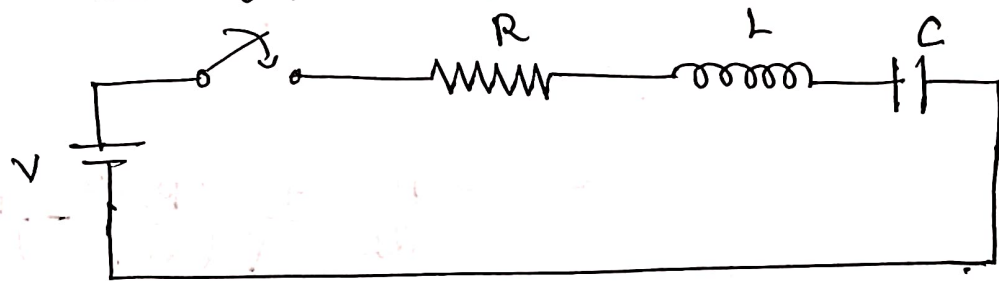


Transient Response of RLC circuit.

Forced Response of RLC circuit

Driven Response of RLC circuit

An RLC circuit is connected to a DC battery through a switch. Assume the initial current in the circuit to be 0 and voltage in capacitor be 0.



Apply KVL

$$V = V_R + V_L + V_C$$

$$= iR + L \frac{di}{dt} + \frac{1}{C} \int i \cdot dt$$

Taking Laplace transform on both sides.

$$\frac{V}{s} = R I(s) + L \left[s I(s) - i(0) \right] + \frac{1}{C} \frac{I(s)}{s}$$

$$= I(s) \left[R + Ls + \frac{1}{Cs} \right]$$

$$I(s) = \frac{V}{s \left[R + Ls + \frac{1}{Cs} \right]}$$

$$= \frac{V}{s^2 L + sR + \frac{1}{C}}$$

(24)

$$I(s) = \frac{V/L}{\left(s^2 + s \frac{R}{L} + \frac{1}{LC}\right)}$$

$$s = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

2a

$$= \frac{-R/L \pm \sqrt{(R/L)^2 - \frac{4}{LC}}}{2}$$

$$= \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

 $\Downarrow$ $\Downarrow$

$$s = \alpha \pm \beta$$

If roots are real & distinct $\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$.

$$s_1 = \alpha + \beta$$



$$s_2 = \alpha - \beta$$

$$I(s) = \frac{A}{s - (\alpha + \beta)} + \frac{B}{s - (\alpha - \beta)}$$

Taking inverse Laplace Transform.

$$i(t) = A e^{(\alpha + \beta)t} + B e^{(\alpha - \beta)t}$$
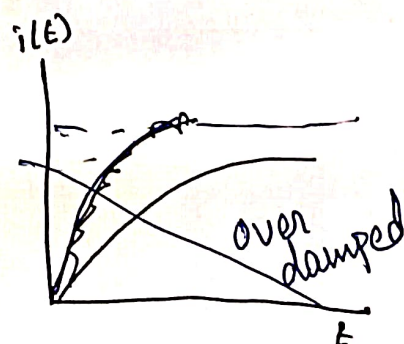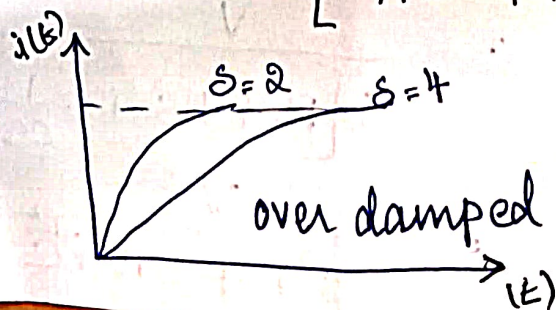
$$= e^{\alpha t} \left[A e^{\beta t} + B e^{-\beta t} \right]$$



case ii Roots are real. $\left(\frac{R}{2L}\right)^2 - \frac{1}{LC} = 0.$

$$\therefore \left(\frac{R}{2L}\right)^2 = \frac{1}{LC}.$$

$\therefore$ The roots are $(s-\alpha)^2$ and $(s-\alpha)$

$$I(s) = \frac{A}{(s-\alpha)^2} + \frac{B}{(s-\alpha)}$$


Taking inverse Laplace Transform.

$$i(t) = Ate^{\alpha t} + Be^{\alpha t}.$$

$$i(t) = e^{\alpha t}(At+B)$$

when roots are complex
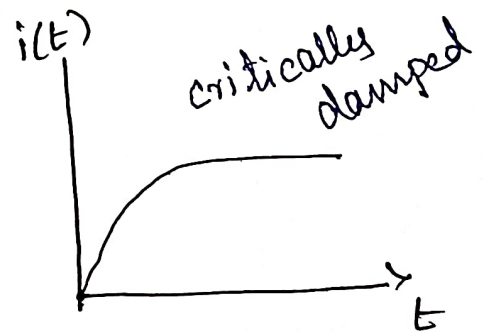
$$\left(\frac{R}{2L}\right)^2 < \frac{1}{LC}$$




$\therefore$ The roots are $(\alpha + j\beta)$ & $(\alpha - j\beta)$

$$I(s) = \frac{A}{s - (\alpha + j\beta)} + \frac{B}{s - (\alpha - j\beta)}.$$

Taking inverse Laplace transform.

$$i(t) = Ae^{(\alpha + j\beta)t} + Be^{(\alpha - j\beta)t}$$
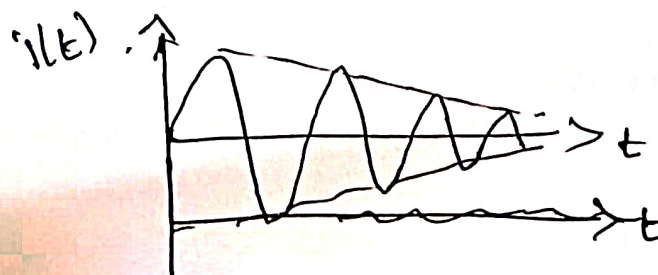
$$i(t) = e^{\alpha t} [Ae^{j\beta t} + Be^{-j\beta t}]$$



This says the current is oscillating and decaying.