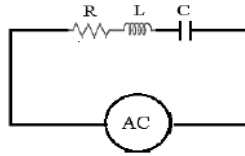



Derive the expression for the current, power, power factor and impedance for series RL and series RC CIRCUITS connected to an AC Voltage source

Solution

RLC Circuit



RL Circuit

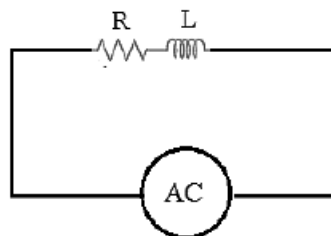

R_L circuit

$$V_R = IR$$

$$V_L = I_{XL} \quad (X_L = 2\pi fL)$$

$$\begin{aligned} V &= V_R + jV_L = IR + jI_{XL} \\ &= I[R + jX_L] \end{aligned}$$

$$\boxed{V = IZ}$$

$$Z \text{ is impedance} = R + jX_L$$

$$|Z| = \sqrt{R^2 + X_L^2}$$

$$\angle Z = \theta = \tan^{-1} \frac{X_L}{R}$$

$$\boxed{Z = |Z| \angle \theta}$$

$$\text{Real power } P = VI \cos \theta$$

$$\text{Reactive power } Q = VI \sin \theta$$

$$\text{Apparent power } S = VI$$

$$\text{power factor } \cos \phi = \frac{R}{Z}$$

Series R-C circuit:

$$V_R = IR$$

$$V_C = IX_C = I \left(\frac{1}{C\omega} \right)$$

$$X_C = \frac{1}{2\pi fC}$$

$$\begin{aligned} V &= V_R + jV_C \\ &= I_R + jIX_C \\ &= I[R + jX_C] \end{aligned}$$

$$\boxed{V=IZ}$$

Z is impedance = $R - jX_C$

$$|Z| = \sqrt{R^2 + X_C^2}$$

$$\angle Z = \theta = \tan^{-1} \left[\frac{X_C}{R} \right]$$


Power factor = $\cos \theta$

Real power $P = VI \cos \theta$

Reactive power $Q = VI \sin \theta$

Apparent power $S = VI$

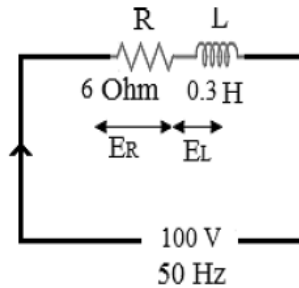RL series circuit having a resistance of 6Ω and an inductance of 0.03 H is connected across a $100\text{ V } 50\text{ Hz}$, ac supply. Calculate the phase angle between the current and voltage and the power factor.
(May/June 2014)



Solution

$$\begin{aligned}\text{Inductive Reactance } X_L &= 2\pi fL \\ &= 2\pi \times 50 \times 0.3 \\ X_L &= 94.2\end{aligned}$$


$$\begin{aligned}\text{Impedance } Z &= \sqrt{R^2 + X_L^2} = \sqrt{6^2 + 94.2^2} \\ &= \sqrt{36 + 8873.64} \\ &= \sqrt{8909.64} \\ Z &= 94.390\end{aligned}$$

$$\begin{aligned}\text{Circuit current } I &= \frac{E}{Z} = \frac{100}{94.39} \\ I &= 1.059\end{aligned}$$

$$\begin{aligned}\text{Phase angle } \phi &= \tan^{-1}\left(\frac{\omega L}{R}\right) = \tan^{-1}\left(\frac{94.2}{6}\right) \\ &= \tan^{-1}(15.7) \\ \phi &= 86.3555\end{aligned}$$

$$\begin{aligned}\text{Power factor} &= \cos \phi = \cos (86.555) \\ &= -0.03828\end{aligned}$$

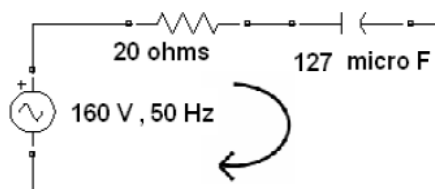A series R-C circuit with $R = 20\ \Omega$ and $C = 127\ \mu\text{F}$ has 160 V, 50 Hz supply connected to it. Find the impedance, current, power, power factor, Voltage drop across R, and C.



Solution

Given:

$$R = 20\Omega$$

$$C = 127\mu\text{F}$$

$$X_c = \frac{1}{2\pi fC}$$

$$X_c = \frac{1}{2\pi \times 50 \times 127 \times 10^{-6}}$$

$$X_c = 25.06\Omega$$

$$Z = \sqrt{R^2 + X_c^2} = \sqrt{(20)^2 + (25.06)^2} = 32.06\Omega$$

$$I = \frac{V}{Z} = \frac{160}{32.06} = 4.99\text{A}$$

$$\text{Power factor} : \frac{R}{Z} = \frac{20}{25.06} = 0.798$$

$$\begin{aligned} \text{Power (P)} &= VI \cos \phi \\ &= 160 \times 4.99 \times 0.798 \end{aligned}$$

$$\boxed{P = 637.12\text{ w}}$$


$$V_R = IR = 4.99 \times 20 = 99.8\text{ V}$$

$$V_C = IX_c = 4.99 \times 25.06 = 125.05\text{ V}$$

$$\therefore V_R = 99.8\text{V}$$

$$\boxed{V_C = 125.05\text{V}}$$

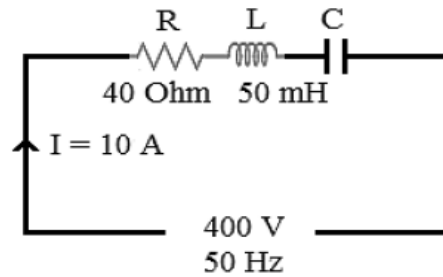A series circuit having pure resistance of 40Ω , pure inductance of 50 mH and a capacitor is connected across a 400 V , 50 Hz ac supply. This RLC circuit draws a current of 10 A . Calculate a) Power factor of the circuit b) Capacitor value.



Solution

$$\text{Current } I = \frac{E}{Z}$$

$$\text{Impedance} = Z = \frac{E}{I} = \frac{400}{10} = 40\ \Omega$$

$$\cos \phi = \frac{R}{Z} = \frac{40}{40} = 1$$

$$\text{Inductive reactance} = X_L = 2\pi f L = 2\pi \times 50 \times 50 \times 10^{-3} = 15.7\Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$40 = \sqrt{40^2 + (X_L - X_C)^2}$$

$$40^2 = 40^2 + (X_L - X_C)^2$$

$$(X_L - X_C)^2 = 0$$

$$X_L = X_C = 15.7\Omega$$


$$X_C = 15.7 = \frac{1}{2\pi f C}$$

$$C = \frac{1}{2\pi \times 50 \times 15.7}$$

$$C = 202.74\mu\text{F}$$

— — — —

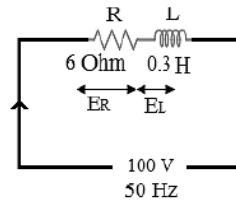RL series circuit having a resistance of 6Ω and an inductance of 0.03 H is connected across a 100 V , 50 Hz , ac supply. Calculate the phase angle between the current and voltage and the power factor
(May/June 2014)



Solution

$$\begin{aligned}\text{Inductive Reactance } X_L &= 2\pi fL \\ &= 2\pi \times 50 \times 0.3 \\ X_L &= 94.2\end{aligned}$$

$$\begin{aligned}\text{Impedance } Z &= \sqrt{R^2 + X_L^2} = \sqrt{6^2 + 94.2^2} \\ &= \sqrt{36 + 8873.64} \\ &= \sqrt{8909.64} \\ Z &= 94.390\end{aligned}$$

$$\begin{aligned}\text{Circuit current } I &= \frac{E}{Z} = \frac{100}{94.39} \\ I &= 1.059\end{aligned}$$

$$\begin{aligned}\text{Phase angle } \phi &= \tan^{-1}\left(\frac{\omega L}{R}\right) = \tan^{-1}\left(\frac{94.2}{6}\right) \\ &= \tan^{-1}(15.7) \\ \phi &= 86.3555\end{aligned}$$


Instantaneous Power:

The Product of instantaneous Voltage and instantaneous Current is called Instantaneous Power.

$$P = VI \cos \phi \text{ Watts.}$$

Steady State Analysis of RLC Circuits:

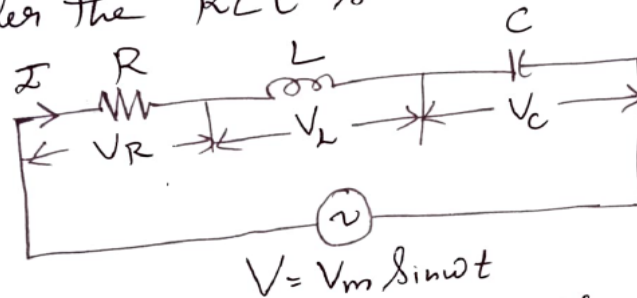Consider the RLC Series Circuits shown in figure.



Supply Voltage $V = V_m \sin \omega t$ Volts
Supply Current I Amps.

Voltage across resistance, $V_R = IR$ Volts

Voltage across Inductance, $V_L = I X_L$ Volts

Voltage across Capacitance, $V_C = I X_C$ Volts.

Impedance, $Z = \sqrt{R^2 + (X_L - X_C)^2} \Omega$.


$$X_L = 2\pi f L \Omega \quad \& \quad X_C = \frac{1}{2\pi f C} \Omega$$

$$I = \frac{V}{Z} \text{ Amps}$$

Power = $VI \cos \phi$ Watts.

A Series RLC Circuits with $R = 25\Omega$, $L = 0.3H$ and $C = 66\mu F$ is Supplied at $220V$, $50Hz$. Find the impedance of the Circuit, Current and Voltage across each Element Power, Reactive power and power factor.

Solution:

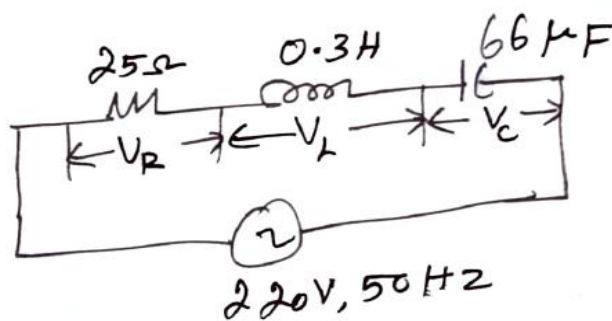

Given Data:

$$\begin{aligned} R &= 25\Omega \\ L &= 0.3H \\ C &= 66\mu F \\ V &= 220V \\ f &= 50Hz \end{aligned}$$

- Find i) impedance (Z)
 ii) Current (I)
 iii) V_R , V_L & V_C
 iv) Power
 v) Reactive power
 vi) Power factor.

i) Impedance (Z)

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Inductive Reactance $\left\{ \begin{aligned} X_L &= 2\pi fL = 2 \times \pi \times 50 \times 0.3 \\ X_L &= 94.24\Omega \end{aligned} \right.$

$$\text{Capacitive Reactance} \left\{ X_C = \frac{1}{2\pi fC} = \frac{1}{2 \times 50 \times 66 \times 10^{-6}} \right.$$

$$X_C = 48.22 \Omega$$

$$\therefore Z = \sqrt{25^2 + (94.24 - 48.22)^2}$$

$$Z = 52.37 \Omega$$

$$\text{ii) Current, } I = \frac{V}{Z} = \frac{220}{52.37} = 4.2 \text{ A.}$$

iii) a) Voltage across the resistor, V_R

$$V_R = I \cdot R = 4.2 \times 25 = 105 \text{ volts}$$

b) Voltage across the Inductor, V_L

$$V_L = I X_L = 4.2 \times 94.24 = 395.8 \text{ V}$$

c) Voltage across the Capacitor, V_C

$$V_C = I X_C = 4.2 \times 48.22 = 202.52 \text{ V}$$

$$\text{iv) Power} = I^2 R = 4.2^2 \times 25 = 441 \text{ Watts.}$$

$$\text{v) Power factor} = \cos \phi = \frac{R}{Z} = \frac{25}{52.37} = 0.477 \text{ (lag)}$$


vi) Reactive power, Q .

$$Q = VI \sin \phi = 220 \times 4.2 \sin 61.5 = 812 \text{ VAR}$$

$$\cos \phi = 0.477$$

$$\phi = \cos^{-1} 0.477 = 61.51^\circ$$

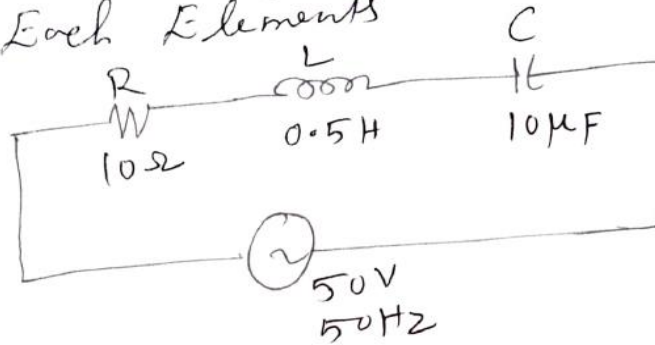In the circuit given determine the total impedance, Current, Phase angle and the Voltage across Each Elements



Solution:

Given data: $V = 50V$ $R = 10\Omega$
 $f = 50Hz$ $L = 0.5H$
 $C = 10\mu F$

Find i) Impedance, Z

ii) Current, I

iii) Phase angle θ (or) ϕ

iv) Voltage across Resistor, V_R

Voltage across Inductor, V_L

Voltage across Capacitor, V_C

i) Impedance, $Z = \sqrt{R^2 + (X_L - X_C)^2}$

Inductive Reactance, $X_L = 2\pi fL$

$= 2 \times \pi \times 50 \times 0.5$

$X_L = 157\Omega$

Capacitive Reactance, $X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times \pi \times 50 \times 10 \times 10^{-6}}$

$$X_C = 318.3 \Omega$$

$$\therefore Z = \sqrt{10^2 + (157 - 318.3)^2} = \sqrt{10^2 + (-161.3)^2}$$

$$= \sqrt{100 + 26017.69} = 161.6 \Omega$$

$$Z = 161.6 \Omega$$

ii) Current, $I = \frac{V}{Z} = \frac{50}{161.6} = 0.31 \text{ Amps}$

$$I = 0.31 \text{ Amps}$$

iii) Phase angle (θ) or (ϕ)

$$\cos \phi = \frac{R}{Z} = \frac{10}{161.6} = 0.0618$$

$$\phi = \cos^{-1}(0.0618) = 86.45^\circ$$

$$\phi = 86.46^\circ$$

iv) Voltage across the resistor, $V_R = I \times R$
 $= 0.31 \times 10 = 3.1 \text{ V}$

$$V_R = 3.1 \text{ Volts}$$

v) Voltage across the Inductor $= V_L = I \times X_L = 0.31 \times 157$

$$V_L = 48.67 \text{ Volts}$$

vi) Voltage across the Capacitor $= V_C = I \times X_C = 0.31 \times 318.3$

$$V_C = 98.67 \text{ Volts}$$

7.