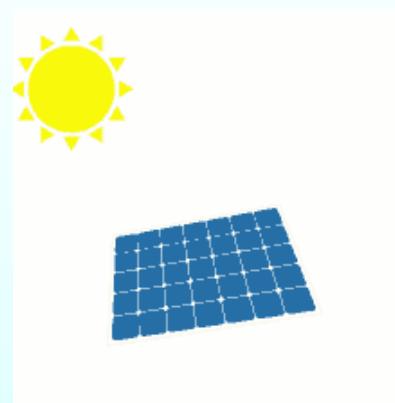


# Mesh Method



*Rohini College of Engineering and Technology*





## MESH METHOD (Loop Method)

Mesh method was first proposed by Maxwell, which simplifies the solution for several networks. Mesh method is also called as loop method or loop current method. In this method loop currents are considered instead of branch currents.

Consider a circuit shown in figure in which two batteries are connected in a five resistor network. A loop is a closed path for current flow. In each loop, a loop current is assumed

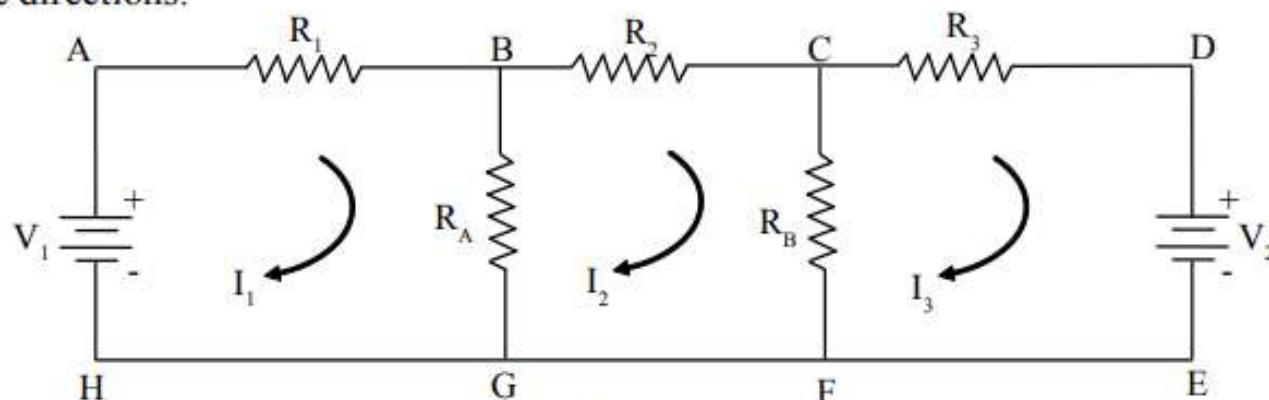as  $I_1$ ,  $I_2$  and  $I_3$ . The current flowing through  $R_1$  is  $I_1$ . Both currents  $I_1$  and  $I_2$  flow through  $R_A$  but in opposite directions.



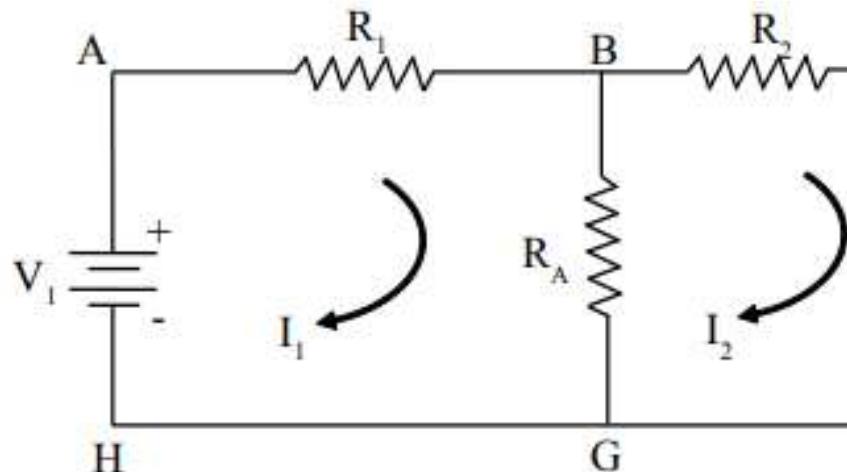


By applying kirchhoff's voltage law in the loop 1 [ABGHA], we get

$$V_1 - I_1 R_1 - (I_1 - I_2) R_A = 0$$

$$\Rightarrow I_1 R_1 + (I_1 - I_2) R_A = V_1$$
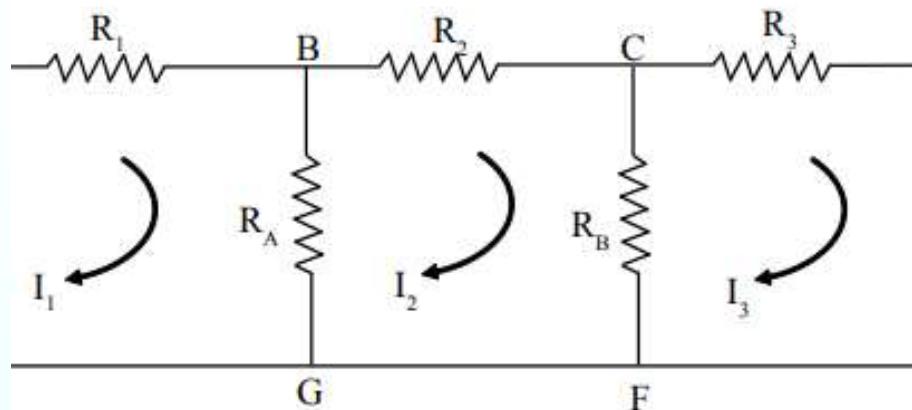
$$\Rightarrow I_1 (R_1 + R_A) - I_2 R_A = V_1$$




By applying KVL in the loop 2 [BCFGB], we get

$$-I_2 R_2 - (I_2 - I_3) R_B - (I_2 - I_1) R_A = 0$$

$$\Rightarrow I_2 R_2 + (I_2 - I_3) R_B + (I_2 - I_1) R_A = 0$$
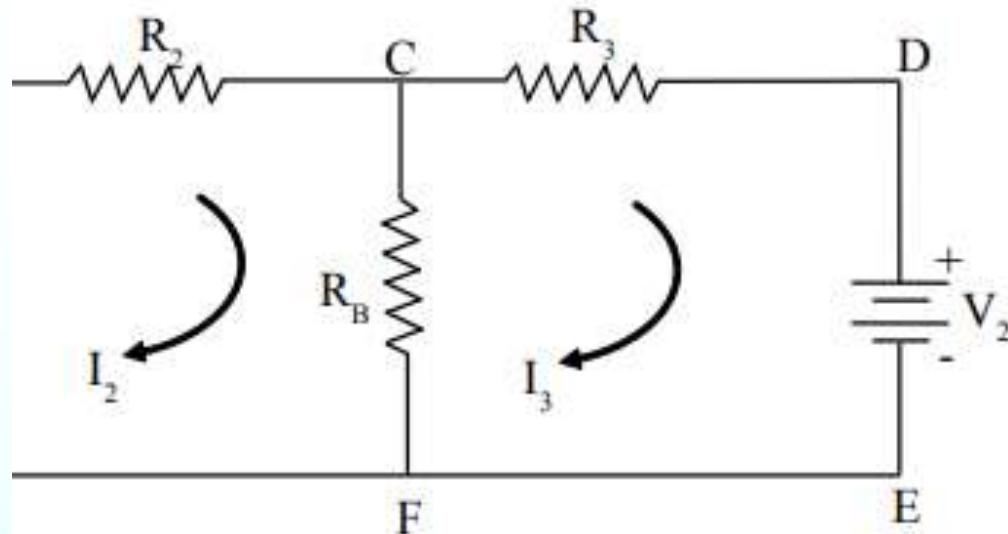
$$\Rightarrow -I_1 R_A + (R_A + R_B + R_2) I_2 - I_3 R_B = 0$$



By applying KVL in the loop 3 [CDEFC], we get

$$-(I_3 - I_2)R_B - I_3R_3 - V_2 = 0$$

$$\Rightarrow (I_3 - I_2)R_B + I_3R_3 = -V_2$$

$$\Rightarrow -I_2R_B + I_3(R_B + R_3) = -V_2$$

$$\Rightarrow I_1(R_1 + R_A) - I_2 R_A = V_1$$

$$\Rightarrow -I_1 R_A + (R_A + R_B + R_2) I_2 - I_3 R_B = 0$$

$$\Rightarrow -I_2 R_B + I_3 (R_B + R_3) = -V_2$$

These equations can be written in the matrix form as,

$$\begin{bmatrix} (R_1 + R_A) & -R_A & 0 \\ -R_A & (R_A + R_2 + R_B) & -R_B \\ 0 & -R_B & (R_B + R_3) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ 0 \\ -V_2 \end{bmatrix}$$

$$I_1 = \frac{\Delta_1}{\Delta}$$

$$I_2 = \frac{\Delta_2}{\Delta}$$

$$I_3 = \frac{\Delta_3}{\Delta}$$

# Thank You

