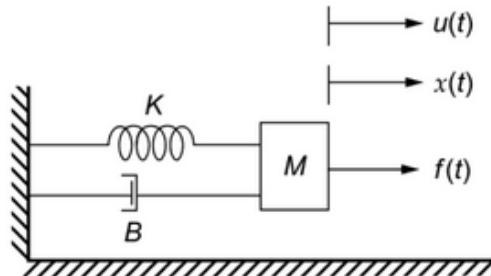


## 1.4 ELECTRICAL ANALOGY OF MECHANICAL SYSTEMS

### FORCE-VOLTAGE ANALOGY

Consider a simple translational mechanical system as shown in figure 1.4.1.



**Figure 1.4.1 Translational mechanical system**


[Source: "Control Systems Engineering" by S.Salivahanan, R.Rengaraj, G.R.Venkatakrishnan, Page: 1.51]

Using D' Alembert's principle, we have,

Sum of the applied forces = Sum of the opposing forces

$$f(t) = M \frac{du(t)}{dt} + Bu(t) + K \int u(t) dt$$

Consider a series RLC circuit as shown in figure 1.4.2.

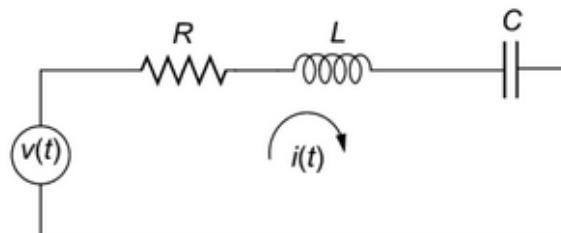

**Figure 1.4.2 Series RLC circuit**

[Source: "Control Systems Engineering" by S.Salivahanan, R.Rengaraj, G.R.Venkatakrishnan, Page: 1.52]


Using KVL, the integro-differential equations can be written as

$$v(t) = L \frac{di(t)}{dt} + Ri(t) + \frac{1}{C} \int i(t) dt$$

Translational system	Electrical system
Force ( $f$ )	Voltage ( $v$ )
Velocity ( $u$ )	Current ( $i$ )
Displacement ( $x$ )	Charge ( $q$ )
Mass ( $M$ )	Inductance ( $L$ )
Damping coefficient ( $B$ )	Resistance ( $R$ )
Spring constant ( $K$ )	1/Capacitance ( $C$ )

## FORCE-CURRENT ANALOGY

Consider a simple parallel RLC circuit as shown in figure 1.4.3.

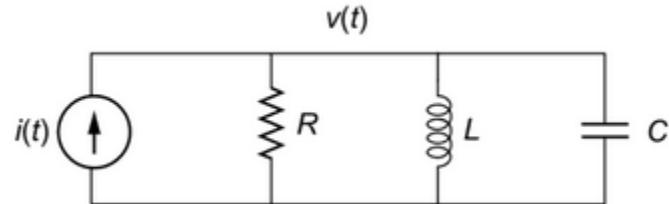

**Figure 1.4.3 Parallel RLC circuit**

[Source: "Control Systems Engineering" by S.Salivahanan, R.Rengaraj, G.R.Venkatakrishnan, Page: 1.52]

Using KCL, the integro-differential equations can be written as follows:

$$i(t) = C \frac{dv(t)}{dt} + G v(t) + \frac{1}{L} \int v(t) dt$$


where, conductance,  $G=1/R$ .

On comparing with the mechanical translational system equation, we get,

Translational System	Electrical System
Force ( $f$ )	Current ( $i$ )
Velocity ( $u$ )	Voltage ( $v$ )
Displacement ( $x$ )	Flux ( $\Phi$ )
Mass ( $M$ )	Capacitance ( $C$ )
Damping coefficient ( $B$ )	Conductance ( $G$ )
Spring constant ( $K$ )	1/Inductance ( $L$ )

## TORQUE-VOLTAGE ANALOGY

Consider a simple rotational mechanical system as shown in figure 1.4.4.

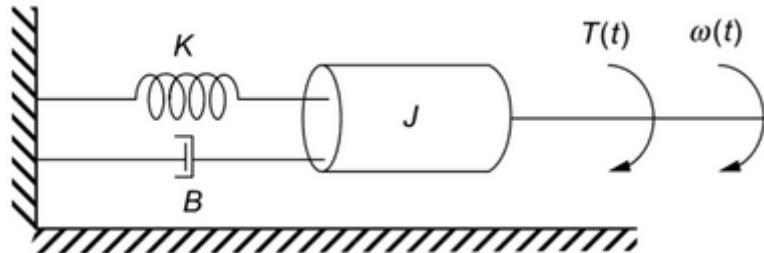

**Figure 1.4.4 Rotational mechanical system**


[Source: "Control Systems Engineering" by S.Salivahanan, R.Rengaraj, G.R.Venkatakrishnan, Page: 1.71]

Using D' Alembert's principle, we have,

Sum of the applied torques = Sum of the opposing torques

$$T(t) = J \frac{d\omega(t)}{dt} + B\omega(t) + K \int \omega(t) dt$$

Consider a series RLC circuit as shown in figure 1.4.5.

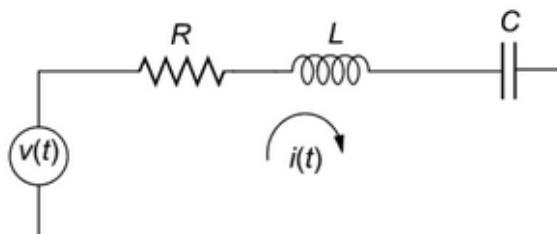

**Figure 1.4.5 Series RLC circuit**

[Source: "Control Systems Engineering" by S.Salivahanan, R.Rengaraj, G.R.Venkatakrishnan, Page: 1.72]

Using KVL, the integro-differential equations can be written as


$$v(t) = L \frac{di(t)}{dt} + Ri(t) + \frac{1}{C} \int i(t) dt$$

On comparing with the mechanical rotational system equation, we get,

Rotational System	Electrical System
Torque (T)	Voltage (v)
Angular velocity ( $\omega$ )	Current (i)
Angular displacement ( $\theta$ )	Charge (q)
Moment of inertia (J)	Inductance (L)
Rotational damping (B)	Resistance (R)
Rotational spring constant (K)	1/Capacitance (C)

## TORQUE-CURRENT ANALOGY

Consider a simple parallel RLC circuit as shown in figure 1.4.6.

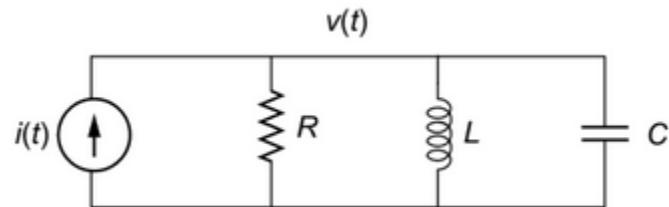

**Figure 1.4.6 Parallel RLC circuit**

[Source: "Control Systems Engineering" by S.Salivahanan, R.Rengaraj, G.R.Venkatakrishnan, Page: 1.73]

Using KCL, the integro-differential equations can be written as follows:

$$i(t) = C \frac{dv(t)}{dt} + G v(t) + \frac{1}{L} \int v(t) dt$$

where, conductance,  $G=1/R$ .

On comparing with the mechanical rotational system equation, we get,

Rotational Mechanical System	T-I Analogous
Torque ( $T$ )	Current ( $i$ )
Angular velocity ( $\omega$ )	Voltage ( $v$ )
Angular displacement ( $\theta$ )	Flux ( $\Phi$ )
Moment of inertia ( $J$ )	Capacitance ( $C$ )
Rotational spring constant ( $K$ )	1/Inductance ( $L$ )
Rotational damping ( $B$ )	Conductance ( $G$ )