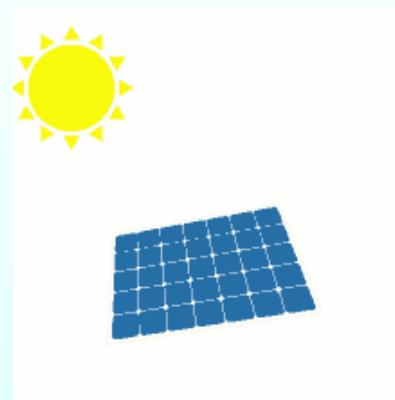



# BALANCED THREE PHASE DELTA CONNECTED LOAD



*Rohini College of Engineering and Technology*



### Delta Connection :

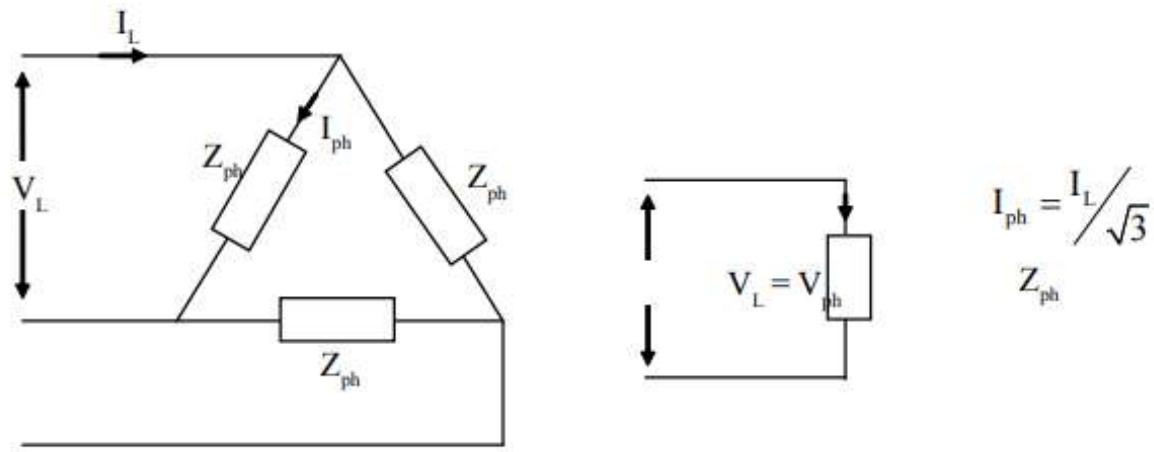

*Fig. 4.30 Balanced Delta Load*

A balanced 3 phase load when connected in delta across a 3 phase balanced supply, the total power in three phase delta connected load is equal to the three times of power in star connected load.

$$\text{Phase voltage, } V_{ph} = V_L$$

$$\text{Phase impedance, } Z_{ph} = R + jX = \sqrt{R^2 + X^2}$$



$$\text{Phase current, } I_{\text{ph}} = \frac{V_{\text{ph}}}{Z_{\text{ph}}}$$

$$\text{Line current, } I_L = \sqrt{3} I_{\text{ph}}$$

$$\text{Power factor, } \cos\phi = \frac{R}{Z}$$

$$\text{per phase power} = V_{\text{ph}} I_{\text{ph}} \cos\phi$$

$$\text{Total power, } P = \sqrt{3} V_L I_L \cos\phi$$

$$\text{Reactive power per phase} = V_{\text{ph}} I_{\text{ph}} \sin\phi$$

$$\text{Total reactive power, } Q = \sqrt{3} V_L I_L \sin\phi$$

$$\text{Apparent power per phase} = V_{\text{ph}} I_{\text{ph}}$$

$$\text{Total apparent power, } S = \sqrt{3} V_L I_L$$



# Thank You

