

1.7 DRIVE SYSTEM AND CONTROL CIRCUITRY FOR STEPPER MOTOR

DRIVE SYSTEM

The stepper motor is a digital device that needs binary (digital) signals for its operation. Depending on the stator construction two or more phases have to be sequentially switched using a master clock pulse input. The clock frequency determines the stepping rate, and hence the speed of the motor. The control circuit generating the sequence is called a translator or logic sequencer.

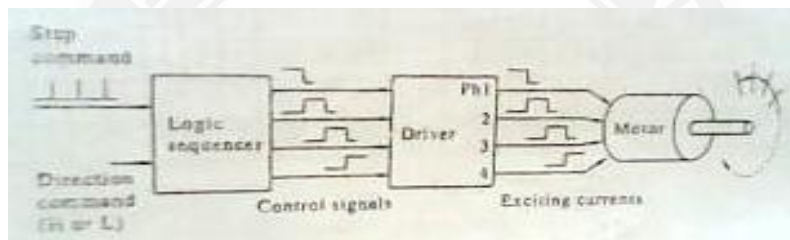


Figure 1.7.1 Block Diagram of the drive system of a stepper motor

[Source: "special electric machines" by R.Srinivasan page:2.63]

The figure shows the block diagram of a typical control circuit for a stepper motor. It consists of a logic sequencer, power driver and essential protective circuits for current and voltage limiting. This control circuit enables the stepper motor to be run at a desired speed in either direction. The power driver is essentially a current amplifier, since the sequence generator can supply only logic but not any power. The controller structure for VR or hybrid types of stepper motor

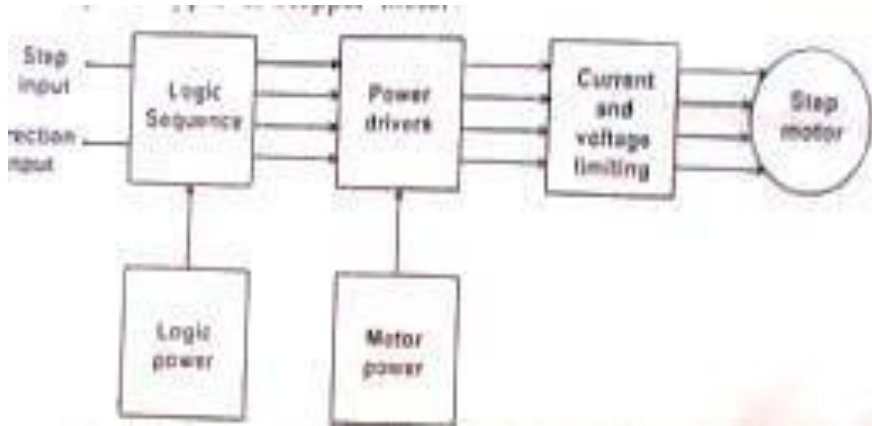


Figure 1.7.2 Block Diagram of a typical step motor control

[Source: "special electric machines" by R.Srinivasan page:2.63]

LOGIC SEQUENCER

The logic sequencer is a logic circuit which control the excitation of the winding sequentially, responding to step command pulses. A logic sequencer is usually composed of a shifter register and logic gates such as NANDs, NORs etc. But one can assemble a logic sequencer for a particular purpose by a proper combination of JK flip flop, IC chips and logic gate chips. Two simple types of sequencer build with only two JK-FFs are shown in figure for unidirectional case. Truth tables for logic sequencer also given for both the directions.

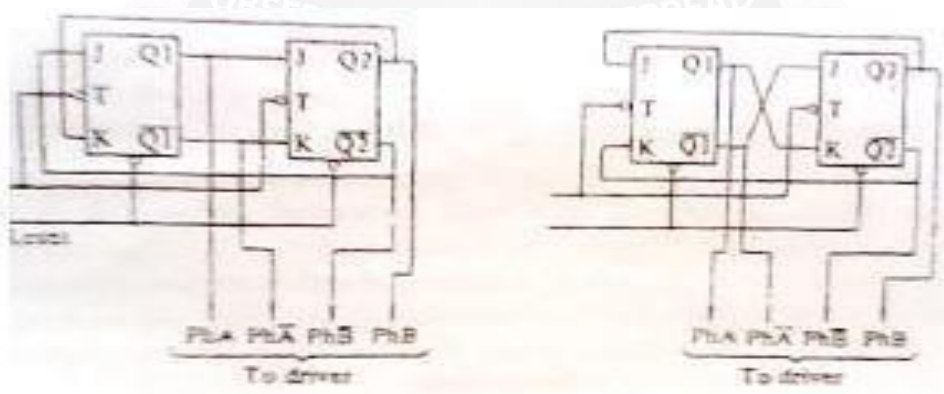


Figure 1.7.3 Logic Sequencer

[Source: "special electric machines" by R.Srinivasan page:2.64]

	R	1	2	3	4	5	6
Ph A,Q1	0	1	1	0	0	1	1
Ph B,Q2	0	0	1	1	0	0	1
Ph A,Q1	1	0	0	1	1	0	0
Ph B,Q2	1	1	0	0	1	1	0

	R	1	2	3	4	5	6
Ph A,Q1	0	0	1	1	0	0	1
Ph B,Q2	0	1	1	0	0	1	1
Ph A,Q1	1	1	0	0	1	1	0
Ph B,Q2	1	0	0	1	1	0	0

A unidirectional logic sequencer for two phases on operation of a two phase hybrid motor. The corresponding between the output terminals of the sequencer and the phase windings to be controlled is as follows. If Q1 is on the H level the winding Ph A is excited and if Q1 is on L level, Ph A is not excited. To reserve the rotational direction, the connection of the sequencer must be interchanged. The direction switching circuits shown in fig 2.40 may be used for this purpose. The essential functions being in the combination of three NAND gates or two AND gates and a NOR gate.

POWER DRIVER CIRCUIT

The number of logic signals discussed above is equal to the number of phases and the power circuitry is identical for all phases. Fig. 2.44(a) shows the simplest possible circuit of one phase consisting of a Darlington pair current amplifier and associated protection circuits. The switching waveform shown in figure is the typical R-L response with an exponential rise followed by decay at the end of the pulses.

In view of the inductive switching operation, certain protective elements are introduced in the driver circuit. These are the inverter gate 7408, the forward biased diode D1 and the freewheeling diode D. The inverter IC provides some sort of isolation between the logic circuit and the power driver. There are some problems with this simple power circuit. They can be understood by considering each phase winding as a R-L circuit

shown in figure. subject to repetitive switching. On application of a positive step voltage, the current rises exponentially as

Where $I=V/R$ – rated current and

$\tau=L/R$ winding time constant.

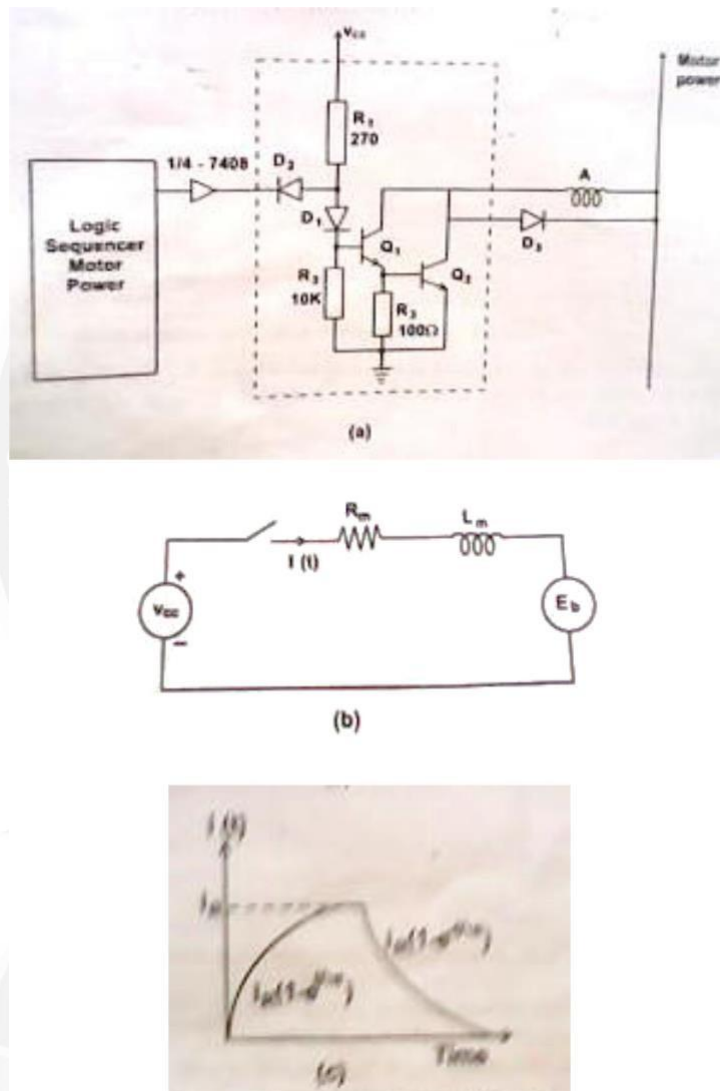


Figure 1.7.4 Power Driver Stage of Stepper Motor Controller

[Source: "special electric machines" by R.Srinivasan page:2.69]

In practice, the time constant τ limits the rise and fall of current in the winding. At low stepping rate the current rises to the rated value in each ON interval and falls to zero value in each OFF interval. However as the switching rate increases, the current is not

able to rise to the steady state, nor fall down to zero value within the on/off time intervals set by the pulse waveform. This in effect, smoothens the winding current reducing the swing as shown in figure. As a result the torque developed by the motor gets reduced considerably and for higher frequencies, the motor just vibrates or oscillates within one step of the current mechanical position.

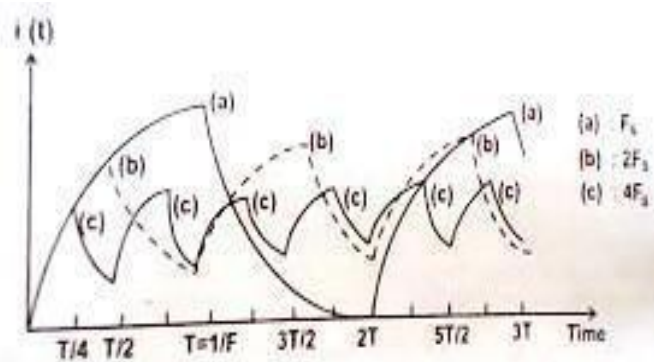


Figure 1.7.5 Effect of increasing Stepping Rate on Current Swing

[Source: "special electric machines" by R.Srinivasan page:2.70]

In order to overcome these problems and to make improvement of current build up several methods of drive circuits have been developed. For example when a transistor is turned on to excite a phase, the power supply must overcome effect of winding inductances has tendency to oppose the current built up. As switching frequency increases the position that the buildup time takes up within the switching cycle becomes large and it results in decreased torque and slow response.

Improvement of current buildup/special driver circuit

(a) Resistance drive (L/R drive)

Here the initial slope of the current waveform is made higher by adding external resistance in each winding and applying a higher voltage proportionally. While this increases the rate of rise of the current, the maximum value remains unchanged as

shown in figure 1.7.5

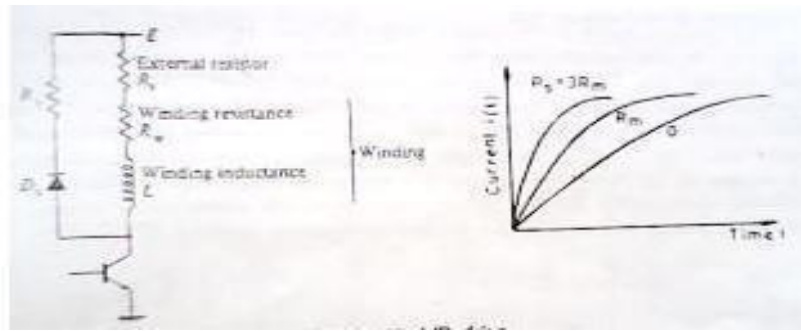


Figure 1.7.5 Resistance L/R drive

[Source: "special electric machines" by R.Srinivasan page:2.71]

The circuit time constant is now reduced and the motor is able to develop normal torque even at high frequencies. The disadvantage of this method is Flow of current through external resistance causes I^2R losses and heating. This denotes wastage of power as far as the motor is concerned. In order to reach the same steady state current I_R as before, the voltage required To be applied is much higher than before. Hence this approach is suitable for small instrument stepper motor with current ratings around 100 mA, and heating is not a major problem.

(b) Dual voltage driver (or) Bi-level driver

To reduce the power dissipation in the driver and increase the performance of a stepping motor, a dual-voltage driver is used. The scheme for one phase T_1 is shown in fig. 1.7.6. When a step command pulse is given to the sequencer, a high level signal will be put out from one of the output terminal to excite a phase winding. On this signal both 1 and 2 are turned on, and the higher voltage E_H will be applied to the winding. The diode D_1 is now reverse biased to isolate the lower voltage supply. The current build up quickly due to the higher voltage E_H . The time constant of the

monostable multivibrator is selected so that transistor 1 is turned off when the winding current exceeds the rated current by a little. After the higher

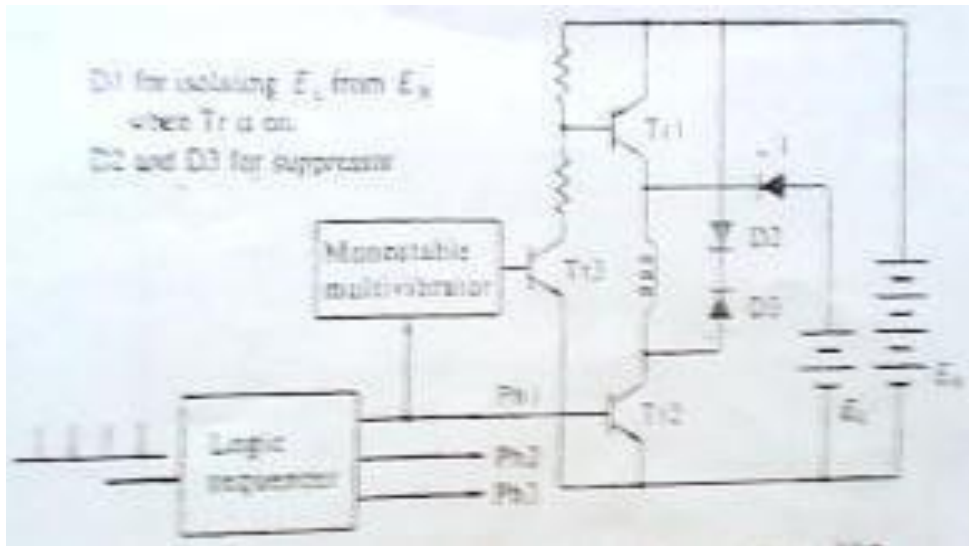


Figure 1.7.6 Dual voltage Drive

[Source: "special electric machines" by R.Srinivasan page:2.72]

Voltage source is cut off the diode is forward biased and the winding current is supplied from the lower voltage supply. A typical current wave form is shown figure

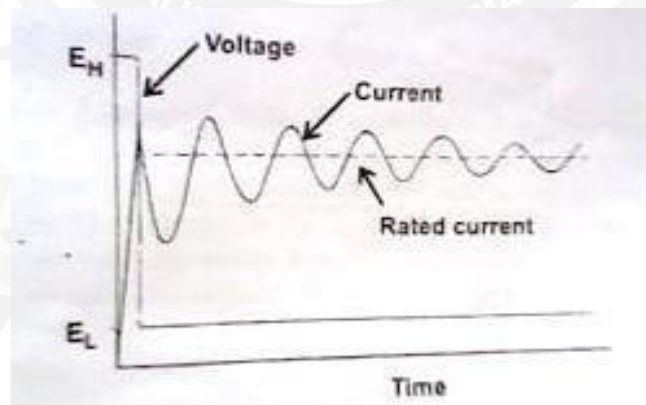


Figure 1.7.6 Voltage and current wave form in dual voltage driver

[Source: "special electric machines" by R.Srinivasan page:2.72]

When the dual voltage method is employed for the two phase on drive of a two phase

T_r

hybrid motor, the circuit scheme will be such as that shown in fig.1.7.7. Two transistors Tr_1 & Tr_2 and two diodes D_1 and D_2 are used for switching the higher voltage. In dual voltage scheme as the stepping rate is increased, the high voltage is turned on for a greater percentage of time.

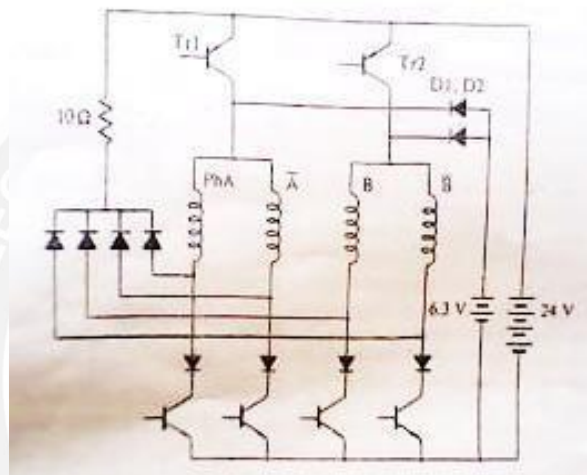


Figure 1.7.7 Dual voltage Driver circuit

[Source: "special electric machines" by R.Srinivasan page:2.72]

It requires two regulated power supplies EH & EL and two power transistor switches Tr_1 & Tr_2 and complex switching logic. Hence it is not very popular.

(c) Chopper drive

Here a higher voltage 5 to 10 times the rated value is applied to the phase winding as shown in fig.2.50(a) and the current is allowed to rise very fast. As soon as the current reaches about 2 to 5% above the rated current, the voltage is cut off, allowing the current to decrease exponentially. Again as the current reaches some 2 to 5% below the rated value, the voltage is applied again. The process is repeated some 5-6 times within

the ON period before the phase is switched off. During this period the current oscillates about the rated value as shown in figure A minor modification is to chop the applied dc voltage at a high frequency of around 1khz, with the desired duty cycle so as to obtain the average on-state current equal to the rated value.

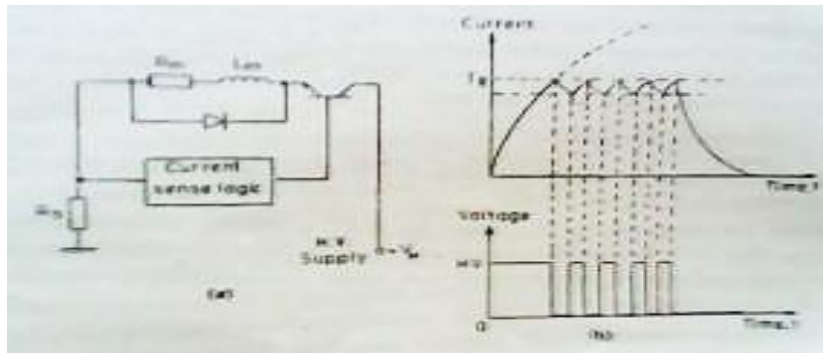


Figure 1.7.8 Oscillation of current in chopper drive

[Source: "special electric machines" by R.Srinivasan page:2.72]

The chopper drive is particularly suitable for high torque stepper motors. It is energy efficient like the bi-level drive but the control circuit is simpler.

(d) Problems with driver circuits

A winding on a stepping motor is inductive and appears as a combination of inductance and resistance in series. In addition, as a motor revolves a counter emf is produced in the winding. The equivalent circuit to a winding is hence, such as that shown for designing a power driver one must take into account necessary factors and behavior of this kind of circuit. Firstly the worst case conditions of the stepping motor, power transistors, and supply voltage must be considered. The motor parameters vary due to manufacturing tolerance and operating conditions. Since stepping motors are designed to deliver the highest power from the smallest size, the case temperature can be as high as about 100°C and the winding resistance therefore increases by 20 to

25 per cent.

Suppressor circuits

These circuits are needed to ensure fast decay of current through the winding when it is turned off. When the transistor in the above fig is turned off a high voltage builds up to $L di/dt$ and this voltage may damage the transistor. There are several methods of suppressing this spike voltage and protecting the transistor as shown in the following.

(a) Diode suppressor

If a diode is put in parallel with the winding in the polarity as shown in fig. a circulating current will flow after the transistor is turned off, and the current will decay with time. In this scheme, no big change in current appears at turn off, and the collector potential is the supply potential E plus the forward potential of the diode. This method is very simple but a drawback is that the circulating current lasts for a considerable length of time and it produces a braking torque.

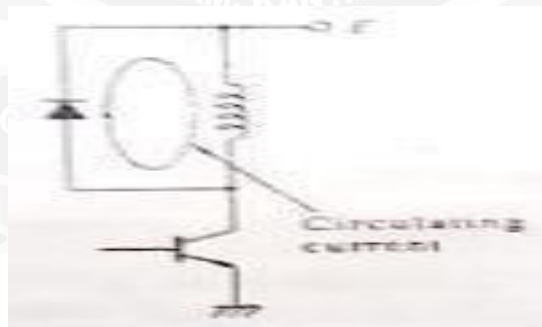


Figure 1.7.9 Diode Resistor suppressor

[Source: "special electric machines" by R.Srinivasan page:2.79]

(b) Diode-Resistor suppressor

A resistor is connected in series with the diode as shown in fig to damp quickly the

circulating current. The voltage VCE applied to the collector at turn-off in this scheme is

$$V_{CE} = E + I R_S + V_D$$

Where E= supply potential

I= Current before turning off

R_S -resistance of suppressor resistor

V_D -forward potential of diode

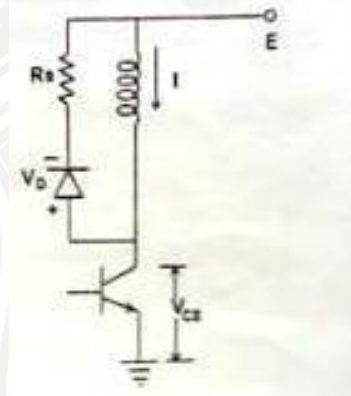


Figure 1.7.10 suppressor based on zener diode

[Source: "special electric machines" by R.Srinivasan page:2.79]

A high resistance R_S is required to achieve a quick current decay, but this also results in a higher collector potential V_{CE} , thus a transistor with a high maximum voltage rating is necessary.

Zener diode suppressor

In this zener diode are often used to connect in series with the ordinary diode as shown in fig. Compared with preceding two cases zener diode which provides negative bias causes the current to decay more quickly after turn off. In addition to this, it is a merit of this method that the potential applied to the collector is the supply potential plus the zener potential, independent of the current. This makes the determination of the rating

of the maximum collector potential easy. However zeners are signal diodes, rather than power diodes. Their power dissipation is limited to 5w. Consequently, this suppressor can be used for very small instrument stepper motors of typical size 8 to 11.

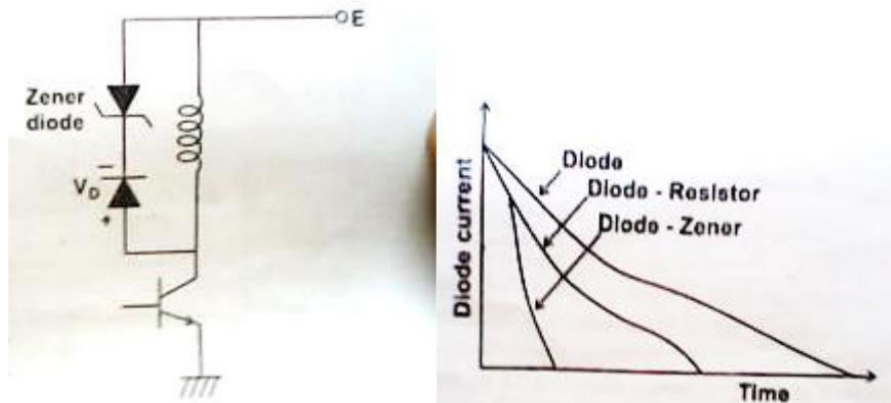


Figure 1.7.11 comparison of suppressor schemes

[Source: "special electric machines" by R.Srinivasan page:2.80]

(d) **Condenser suppressor**

This scheme is often employed for bifilar-wound hybrid motor. An explanation is given for the given for the circuit shown in fig:

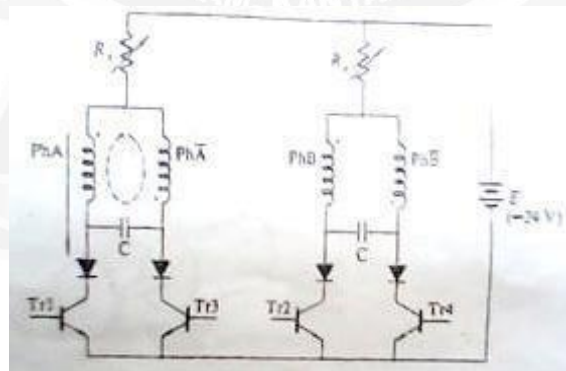


Figure 1.7.12 condenser suppressor

[Source: "special electric machines" by R.Srinivasan page:2.80]

Another utility of condensers is as an electrical damper, a method of damping rotor oscillations is to provide a mechanism to convert kinetic energy to joule heating. If a rotor having a permanent magnet oscillates, an alternating Emf is generated in the winding. However if a current path is not provided or a high resistance is connected, no current will be caused by this Emf. When the condenser is connected between phases an oscillatory current will flow in the closed loop and joule heat is generated in the windings, which means that the condenser works as an electrical damper.

