

MULTISTAGE IMPULSE VOLTAGE GENERATOR

The difficulties encountered with spark gaps for the switching of very high voltages, the increase of the physical size of the circuit elements, the efforts Generation of high voltages 61necessary in obtaining high dace. voltages to charge C1 and, last but not least, the difficulties of suppressing corona discharges from the structure and leads during the charging period make the one-stage circuit inconvenient for higher voltages. In order to overcome these difficulties, in 1923 Marx35 suggested an arrangement where a number of condensers are charged in parallel through high ohmic resistances and then discharged in series through spark gaps. There are many different, although always similar, multistage circuits in use. To demonstrate the principle of operation, a typical circuit is presented in Figure 3.2.1 which shows the connections of a six-stage generator. The dace. Voltage charges the equal stage capacitors C01 in parallel through the high value charging resistors R0 as well as through the discharge (and also charging).

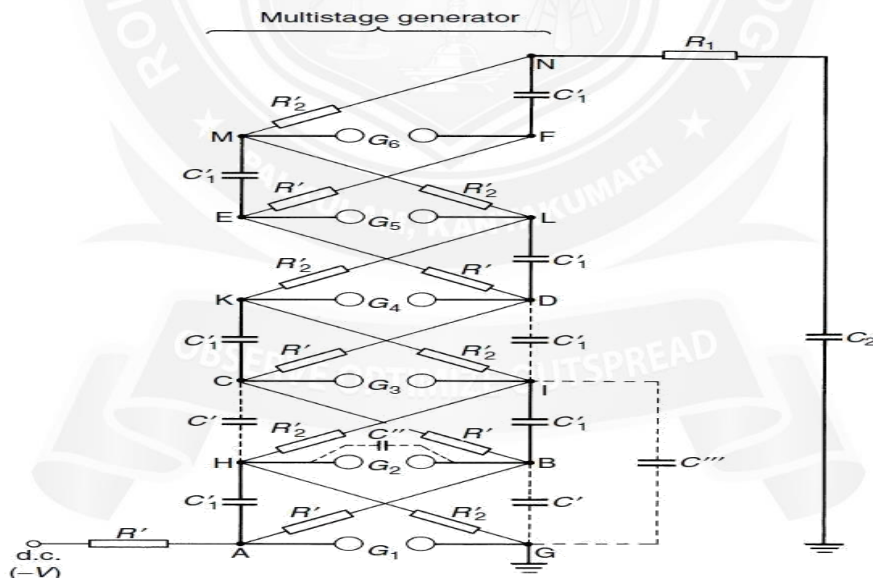


Figure 3.2.1 Basic circuit of a six-stage impulse generator (Marx generator) resistances

[Source: "High Voltage Engineering" by C.L. Wadhwa , Page – 354]

As the point B still would remain at the charging potential, $-V$, thus a voltage of $2V$ would appear across G_2 . This high overvoltage would therefore cause this gap to break down and the potential at point I would rise to C_2V , creating a potential difference of $3V$ across gap G_3 , if again the potential at point C would remain at the charging potential. This traditional interpretation, however, is wrong, since the potentials B and C can – neglecting stray capacitances – also follow the adjacent potentials of the points A and B, as the resistors R_0 are between. We may only see up to now that this circuit will give an output voltage with a polarity opposite to that of the charging voltage. In practice, it has been noted that the gap G_2 must be set to a gap distance only slightly greater than that at which G_1 breaks down; otherwise it does not operate.

According to Edwards and Perry for an adequate explanation one may assume the stray capacitances C_0 , C_{00} and C_{000} within the circuit. The capacitances C_0 are formed by the electrical field between adjacent stages; C_{000} has a similar meaning across two stages. C_{00} is the capacitance of the spark gaps. If we assume now the resistors as open circuits, we may easily see that the potential at point B is more or less fixed by the relative magnitudes of the stray capacitances. Neglecting C_0 between the points Hand C and taking into account that the discharge capacitors C_{01} are large in comparison to the stray capacitances, point B can be assumed as mid-point of a capacitor voltage divider formed by C_{00} and C_0/C_{000} . Thus the voltage rise of point A from $-V$ to zero will cause the potential B to rise from V to a voltage of

$$V_B = -V + V \left(\frac{C''}{C' + C'' + C'''} \right) = -V \left(\frac{C' + C'''}{C' + C'' + C'''} \right)$$

Hence the potential difference across G_2 becomes

$$V_{G_2} = +V - (-V_B) = V \left(1 + \frac{C' + C'''}{C' + C'' + C'''} \right).$$

If C_{00} equals zero, the voltage across G_2 will reach its maximum value $2V$. This gap capacitance, however, cannot be avoided. If the stage capacitances C_0 and C_{00} are both zero, V_{G2} will equal V , and a sparking of G_2 would not be possible. It is apparent, therefore, that these stray capacitances enhance favorable conditions for the operation of the generator. In reality, the conditions set by the above equations are approximate only and are, of course, transient, as the stray capacitances start to discharge via the resistors. As the values of C_0 to C_{00} are normally in the order of some 10 pF only, the time constants for this discharge may be as low as 10^{-7} to 10^{-8} sec. Thus the voltage across G_2 appears for a short time and leads to breakdown within several tens of nanoseconds. Transient over voltages appear across the further gaps, enhanced also by the fact that the output terminal N remains at zero potential mainly, and therefore additional voltages are built up across the resistor R_{02} . So the breakdown continues and finally the terminal N attains a voltage of C_6V , or nV , if n stages are present.

The processes associated with the firing of such generators are even more sophisticated. They have been thoroughly analyzed and investigated experimentally.^{31,36,37} In practice for a consistent operation it is necessary to set the distance for the first gap G_1 only slightly below the second and further gaps for earliest breakdown. It is also necessary to have the axes of the gaps in one vertical plane so that the ultraviolet illumination from the spark in the first gap irradiates the other gaps. This ensures a supply of electrons released from the gap to initiate breakdown during the short period when the gaps are subjected to the overvoltage.

If the first gap is not electronically triggered, the consistency of its firing and stability of breakdown and therefore output voltage is improved by providing ultraviolet illumination for the first gap. These remarks indicate only a small part of the problems involved with the construction of spark gaps and the layout of the generator.

The wave front control resistor R_1 is placed between the generator and the load only. Such a single 'external' front resistor, however, has to withstand for a short time the full rated voltage and therefore is inconveniently long or may occupy much space. This disadvantage can be avoided if either a part of this resistance is distributed or if it is completely distributed within the generator. Such an arrangement is illustrated in Fig. 2.30, in which in addition the series connection of the capacitors C_0 and gaps (as proposed originally by Goodlet_38_) is changed to an equivalent arrangement for which the polarity of the output voltage is the same as the charging voltage. The charging resistors R_0 are always large compared with the distributed resistors R_0 and R_0 , and R_0 is made as small as is necessary to give the required time to halve-value T_2 .

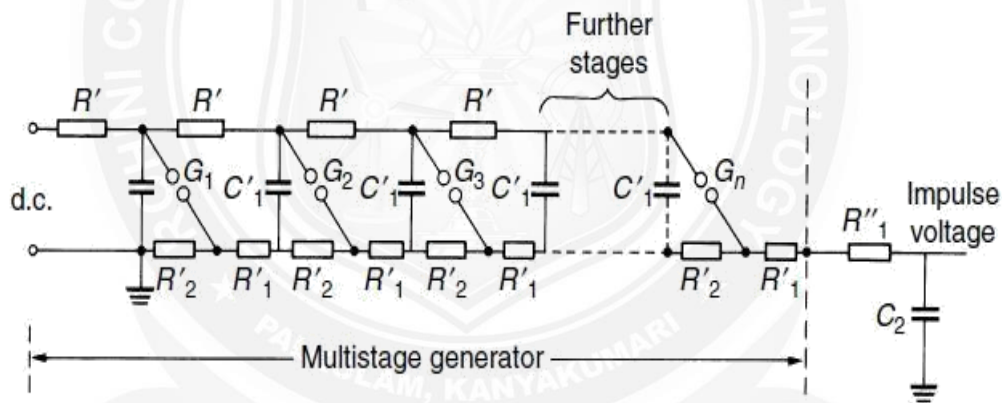


Figure 3.2.2 Multistage impulse generator with distributed discharge and front Resistors

[Source: "High Voltage Engineering" by C.L. Wadhwa, Page – 381]

R_0 : discharge resistors. R_0 : internal front resistors. R_0 : external front resistor excited by the inductance and capacitance of the external leads between the generator and the load, if these leads are long. If the generator has fired, the total is charge capacitance C_1 maybe calculated as where n is the number of stages. The consistent firing of such circuits could be explained as for the generator.