

Common Drain Amplifier

In this circuit shown in figure 3.3.1, input is applied between gate and source and output is taken between source and drain.

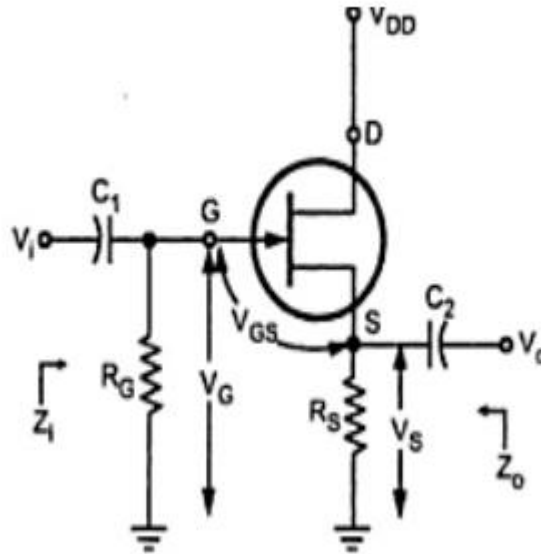


Figure 3.3.1 Common Drain Amplifier

Diagram Source Electronic Tutorials

In this circuit, the source voltage is

$$V_s = V_G + V_{GS}$$

When a signal is applied to the JFET gate via C_1 , V_G varies with the signal. As V_{GS} is fairly constant and $V_s = V_G + V_{GS}$, V_s varies with V_i . The following figure 3.3.2 shows the low frequency equivalent model for common drain circuit.

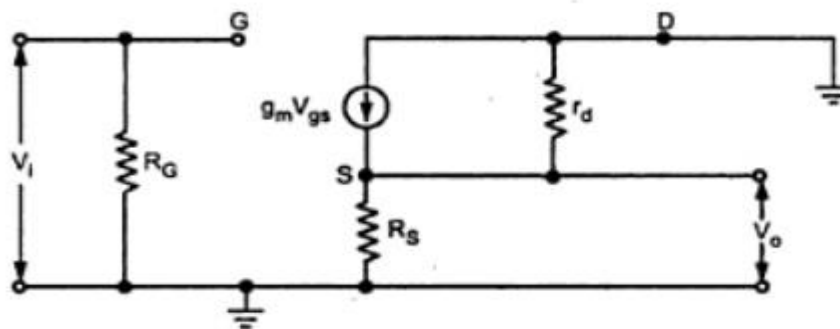


Figure 3.3.2 Small model of common Drain Amplifier

Diagram Source Electronic Tutorials

Input Impedance Z_i

Figure 3.3.3 shows the simplified small model of common Drain Amplifier.

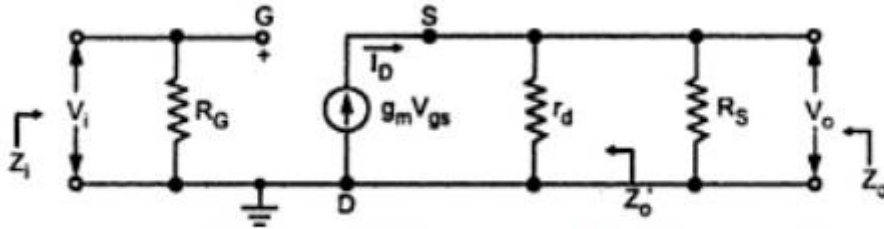


Figure 3.3.3 Simplified small model of common Drain Amplifier

Diagram Source Electronic Tutorials

$$Z_i = R_G$$

Output Impedance Z_o

It is given by

$$Z_o = Z_o' || R_s$$

where
$$Z_o' = \left. \frac{V_o}{I_d} \right|_{V_i=0}$$

Applying KVL to the outer loop we can have,

$$V_i + V_{gs} - V_o = 0$$

As
$$V_i = 0,$$

$$V_{gs} = V_o$$

Looking at Fig. we can write that,

$$g_m V_{gs} = I_d$$

But $V_{gs} = V_o$, so

$$g_m V_o = I_d$$

$$Z_o' = \frac{V_o}{I_d} = \frac{1}{g_m}$$

$$\therefore Z_o = \frac{1}{g_m} || R_s$$

Voltage gain (A_v)

It is given by

$$A_v = \frac{V_o}{V_i}$$

Looking at Fig. we can write that,

$$V_o = -I_d (r_d || R_s)$$

and
$$I_d = g_m V_{gs}$$

$$\therefore V_o = -g_m V_{gs} (r_d || R_s)$$

But

$$\begin{aligned} V_i &= -V_{gs} + V_o \\ &= -V_{gs} + [-g_m V_{gs} (r_d || R_s)] \end{aligned}$$

Substitute the value V_o and V_i . Then

$$A_v = \frac{-g_m V_{gs} (r_d \parallel R_s)}{-V_{gs} (1 + g_m (r_d \parallel R_s))}$$

$$= \frac{g_m (r_d \parallel R_s)}{1 + g_m (r_d \parallel R_s)}$$

if $r_d \gg R_s$

$$A_v = \frac{g_m R_s}{1 + g_m R_s}$$

if $g_m R_s \gg 1$

$A_v \approx 1$, but it is always less than one.

Common drain circuit does not provide voltage gain.& there is no phase shift between input and output voltages.

Table summarizes the performance of common drain amplifier

	Exact	$r_d \gg R_D$
Z_i	R_G	R_G
Z_o	$\frac{1}{g_m} \parallel R_s$	$\frac{1}{g_m} \parallel R_s$
A_v	$\frac{g_m (r_d \parallel R_s)}{1 + g_m (r_d \parallel R_s)}$	$\frac{g_m R_s}{1 + g_m R_s}$